

**Illustration 1**

**Question:** An electrical device sends out 78 coulombs of charge through a conductor in 6 seconds. Find the current flow.

**Solution:** Given that charge flowing  $Q = 78 \text{ C}$ ,  
time of flow  $t = 6 \text{ s}$

$$\text{The current } I = \frac{Q}{t} = \frac{78 \text{ C}}{6 \text{ s}} = 13 \text{ A}$$

**Illustration 2**

**Question:** What is the quantity of electricity required to provide a current of 1 A for one hour?

**Solution:** Given that the current  $I = 1 \text{ A}$ ,  
time of flow  $t = 1 \text{ hour} = 3600 \text{ s}$   
The quantity of electricity = the amount of charge flowing

$$\begin{aligned} Q &= It \\ &= (1 \text{ A})(3600 \text{ s}) = 3600 \text{ C} \end{aligned}$$

**Illustration 3**

**Question:** The current in a conductor is 5 A when the voltage between the ends of the conductor is 12 V. What is the resistance (in  $\text{m}\Omega$ ) of the conductor?

**Solution:** Given that  $I = 5 \text{ A}$ ;  $V = 12 \text{ V}$ ;  $R = ?$

$$R = \frac{V}{I} = \frac{12\text{V}}{5\text{A}} = 2400 \text{ m}\Omega$$

**Illustration 4**

**Question:** A certain rectangular block has dimensions  $100 \text{ cm} \times 1 \text{ cm} \times 1 \text{ cm}$ . Find the resistance (in  $\text{m}\Omega$ ) of the block (across the square faces. The specific resistance of the material is  $40 \times 10^{-8} \text{ ohm-metre}$ ).

**Solution:**

Resistance of the block across the square faces



$$R = \frac{\rho \times L}{A} = \frac{(40 \times 10^{-8} \text{ ohm-m})(1\text{m})}{1 \times 10^{-4} \text{ m}^2} = 4 \text{ m}\Omega$$

**Illustration 5**

**Question:** A metal wire of diameter 2 mm and of length 100 m has a resistance of 0.5475 ohm at  $20^\circ\text{C}$  and 0.805 ohm at  $150^\circ\text{C}$ . Find the value of its resistance at  $0^\circ\text{C}$

**Solution:**

If  $R_{20}$  and  $R_{150}$  be the resistances at temperatures  $20^\circ\text{C}$  and  $150^\circ\text{C}$  respectively and  $\alpha$  be the temperature coefficient of resistance

$$R_{20} = 0.5475 = R_0 (1 + \alpha \times 20) \quad \dots \text{(i)}$$

$$R_{150} = 0.805 = R_0 (1 + \alpha \times 150) \quad \dots \text{(ii)}$$


$$\text{Now, } \alpha = \frac{R_{150} - R_{20}}{R_{20} \times 150 - R_{150} \times 20} = \frac{0.805 - 0.5475}{0.5475 \times 150 - 0.805 \times 20} \quad \text{or } \alpha = 3.9 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$$

Substituting this value of  $\alpha$  in equation (i),  $R_0 = 508 \text{ m}\Omega$

**Illustration 6**

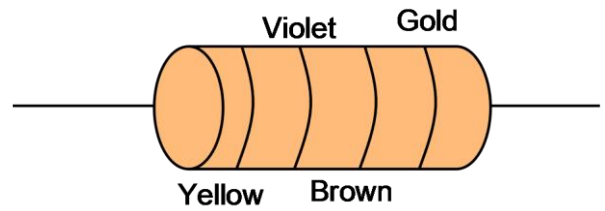**Question:** Figure shows a colour –coded resistor. What is the resistance of this resistor?

**Solution:** The number for yellow colour is 4.  
 The number for violet colour is 7.  
 Brown colour gives a multiplier of  $10^1$ . Gold indicates a tolerance of 5%.  
 So the resistance of the given resistor is  $47 \times 10\Omega \pm 5\%$




(b) In the second code the body of the resistor one, end of a resistor and a dot on the body of the resistor carry specific colours.  
 The colour of the body gives the first significant figure.  
 The colour of the end gives the second significant figure.  
 The colour of the dot on the body of the resistor gives the decimal multiplier i.e., the number of zeros that will follow the two significant figures.  
 The colour of the ring  $R$  indicates the percentage accuracy of resistance or tolerance limits of the value of resistance.

**Illustration 7**

**Question:** Three resistors of values 4 ohm, 6 ohm and 7 ohm are in series and a potential difference of 34 V is applied across the grouping. Find the potential drop across each resistor.

**Solution:**

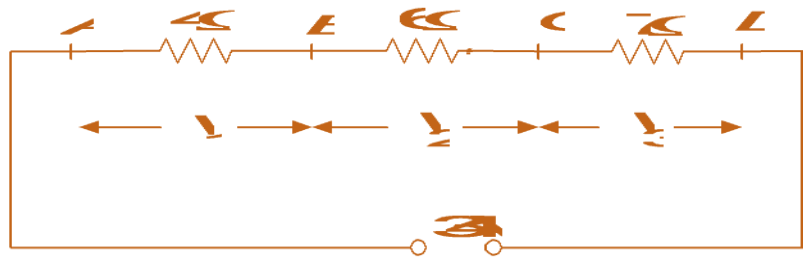


The current through the circuit  $= \frac{34V}{(4+6+7)ohm} = 2 A$   
 Potential difference across 4 ohm resistor  $= IR = 2 A \times 4 ohm = 8 V$   
 Potential difference across 6 ohm resistor  $= 2A \times 6 ohm = 12 V$   
 Potential difference across 7 ohm resistor  $= 2 A \times 7 ohm = 14 V$

**Illustration 8**

**Question:** Two resistances 3 ohm and 2 ohm are in parallel connection and a potential difference of 12 V is applied across them. Find

- (a) the circuit current and
- (b) the branch currents.

**Solution:**

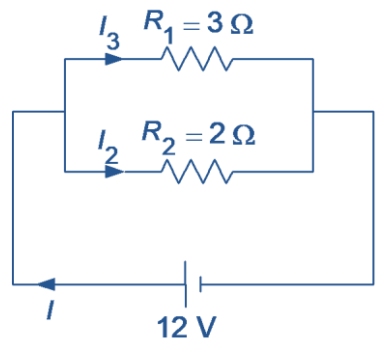

(a) The circuit current  $= \frac{\text{Circuit voltage}}{\text{Circuit resistance}}$

$$= \frac{12V}{1.2\Omega} = 10 \text{ A}$$

(b) The current through 2 ohm resistor

$$I_2 = I \times \frac{3}{2+3} = 10 \times \frac{3}{5} = 6 \text{ A}$$


The current through 3 ohm resistor

$$I_3 = I \times \frac{2}{2+3} = 10 \times \frac{2}{5} = 4 \text{ A}$$

(Also  $I_3 = I - I_2 = 10 \text{ A} - 6 \text{ A} = 4 \text{ A}$ )


### Illustration 9

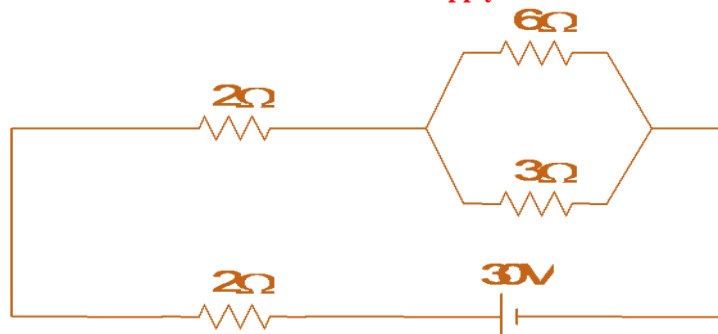**Questions:** Determine the current taken from the 30 V supply.



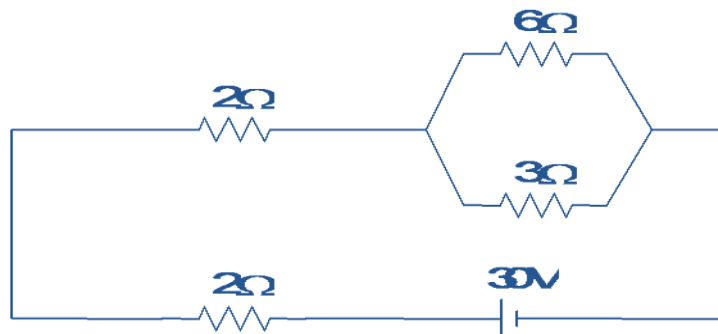**Solution:**

As a first step to solution let us reduce the parallel combination of 6 ohm and 3 ohm into a single resistance.




$$\text{The parallel combination} = \frac{6 \times 3}{6 + 3} \Omega = 2\Omega$$

Now the circuit reduces to three resistors, each 2 ohm, in series to a 30 V supply.

$$\text{Hence the circuit current} = \frac{30V}{6\Omega} = 5 \text{ A}$$


### Illustration 10

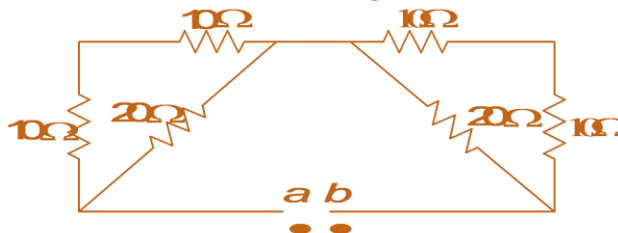**Questions:** Find the equivalent resistance of the circuit given across *ab*.



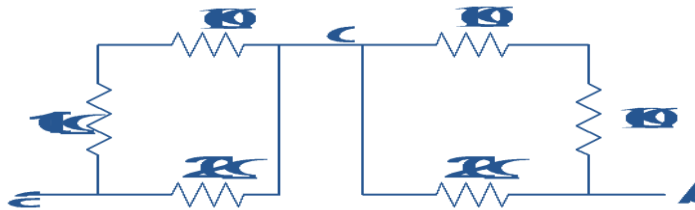**Solution:**

As a first step the circuit may be redrawn as follows.



The left block is equivalent to 20 ohm and 20 ohm in parallel

$$\text{i.e., } \frac{20 \times 20}{20 + 20} = 10 \Omega$$

The right block is equivalent to 20 ohm and 20 ohm in parallel

$$\text{i.e., } \frac{20 \times 20}{20 + 20} = 10 \Omega$$



The circuit now reduces as two resistors in series =  $20 \Omega$

### Illustration 11

**Questions:** Six cells are connected (a) in series, (b) in parallel and (c) in 2 rows each containing 3 cells. The emf of each cell is 1.08 V and its internal resistance is 1 ohm. Calculate the currents (in mA) that would flow through an external resistance of 5 ohm in the three cases.

**Solution:**

(a) The cells in series.

Given that  $\varepsilon = 1.08 \text{ V}$ ,  $n = 6$ ,  $r = 1 \text{ ohm}$ ,  $R = 5 \text{ ohm}$

The total emf =  $n\varepsilon = 6 \times 1.08 \text{ V}$

The total internal resistance  $nr = 6 \times 1 = 6 \text{ ohm}$

$$\text{The current in the circuit } I_S = \frac{n\varepsilon}{R + nr} = \frac{6 \times 1.08}{5 + 6} = 589 \text{ mA}$$

(b) The cells in parallel.

Here  $\varepsilon = 1.08 \text{ V}$ ,  $m = 6$ ,  $r = 1 \text{ ohm}$ ,  $R = 5 \text{ ohm}$

$$I_p = \frac{m\varepsilon}{mR + r} = \frac{6 \times 1.08}{6 \times 5 + 1} = \frac{6.48}{31} = 209 \text{ mA}$$

(c) The cells in multiple arc with  $n = 3$ ,  $m = 2$

$$I = \frac{m n \varepsilon}{m R + n r} = \frac{6 \times 1.08}{(2 \times 5) + (3 \times 1)} = \frac{6.48}{13} = 498 \text{ mA.}$$

### Illustration 12

**Question:** How would you arrange 20 cells each of emf 2 V and internal resistance 1 ohm to give the maximum current through an external resistance of 5 ohm? Also find this current.

**Solution:**

Let  $n$  cells be in series and let there be  $m$  such groups in parallel.

Total number of cells  $mn = 20$

The external resistance  $R = 5 \text{ ohm}$

The internal resistance of each cell  $r = 1 \text{ ohm}$

The condition for maximum current is  $R = \frac{nr}{m}$

$$\text{or, } 5 = \frac{n \times 1}{m} = \frac{n}{m}$$

$$\text{or } n = 5m$$

$$\text{Now } mn = m(5m) = 20$$

$$\text{or } m^2 = 4$$


$$m = 2 \qquad n = 10$$

To get the maximum current the cells have to be arranged in 2 rows, each row consisting of 10 cells in series.

$$\text{The maximum current} = \frac{m\mathcal{E}}{mR+nr} = \frac{20 \times 2}{2 \times 5 + 10 \times 1} = 2 \text{ A}$$


### Illustration 13

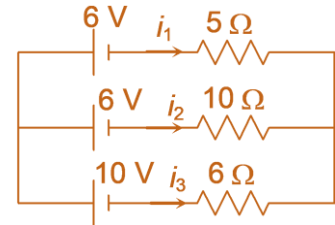**Question:** Show that value of  $i_1 + i_2 + i_3$  in the circuit given is zero. The internal resistances of the batteries are included in the external resistances.



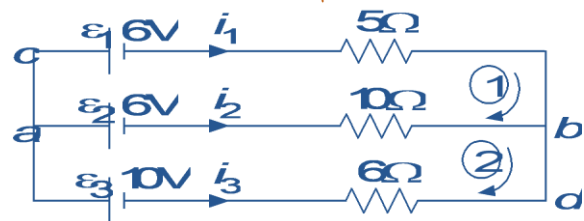**Solution:**

The circuit given can not be simplified further because it contains resistors not in simple series or parallel connection. Hence Kirchoff's rules have to be applied. Since the currents have not been marked we have to do that first. No special care need be taken to indicate the exact current directions since those chosen incorrectly will simplify to give negative numerical values.



Applying the junction rule to junction a

$$i_1 + i_2 + i_3 = 0 \quad \dots \text{(i)}$$

Taking the loop acba

$$IR \text{ drop across } 5 \Omega = +5i_1$$

$$IR \text{ drop across } 10 \Omega = -10i_2$$

$$\text{emf of } \varepsilon_1 = +6 \text{ V}$$

$$\text{emf of } \varepsilon_2 = -6 \text{ V}$$

Applying the loop rule

$$5i_1 - 10i_2 = +6 - 6 = 0 \quad \text{or} \quad i_1 - 2i_2 = 0 \quad \dots \text{(ii)}$$

Considering the loop abda

$$10i_2 - 6i_3 = 10 - 6$$

$$10i_2 - 6i_3 = 4$$

$$5i_2 - 3i_3 = 2 \quad \dots \text{(iii)}$$

To find the unknowns  $i_1$ ,  $i_2$  and  $i_3$ , solve the three equations (i), (ii) and (iii).

We get


$$i_1 = \frac{2}{7} \text{ A}, \quad i_2 = \frac{1}{7} \text{ A}$$

$$i_3 = -\frac{3}{7} \text{ A. The direction of flow of } i_3 \text{ is opposite to that marked in the circuit.}$$

$$\therefore i_1 + i_2 + i_3 = 0$$

### Illustration 14

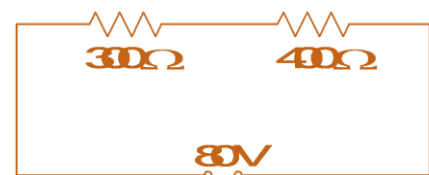**Question:** In the circuit shown a voltmeter reads 30 volt when it is connected across the 400 ohm resistance. Calculate what the same voltmeter would read when it is connected across the 300 ohm resistance.



**Solution:** The voltmeter is in parallel with 400 ohm resistance. Let its resistance be  $R$  ohm.

It is clear that the resistances  $R$  and  $400\ \text{ohm}$  combining in parallel produce equivalent resistance of value of  $300\ \text{ohm}$  so that the potential drop across this equivalent resistance is half of  $60\ \text{V}$ .

$$\therefore \frac{R \times 400}{R + 400} = 300$$

$$400R = 300R + 120000$$

$$100R = 120000$$


$$R = 1200\ \Omega$$

Next the same voltmeter is connected across the  $300\ \text{ohm}$  resistance. Now the equivalent resistance of  $300\ \text{ohm}$  and  $1200\ \text{ohm}$  of voltmeter in parallel connection will be

$$\frac{300 \times 1200}{300 + 1200} = 240\ \Omega$$

$$\text{The total circuit resistance} = 240 + 400 = 640$$
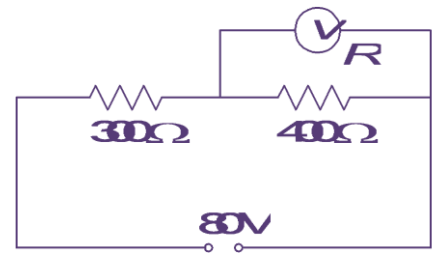
$$\text{Potential drop across } 240\ \text{ohm} = \frac{240}{640} \times 80\ \text{V} = 30\ \text{V}$$



### Illustration 15

**Question:** A battery of emf  $1.4\ \text{V}$  and internal resistance  $2\ \text{ohm}$  is connected to a resistor of  $100\ \text{ohm}$  resistance through an ammeter. The resistance of the ammeter is  $\frac{4}{3}\ \text{ohm}$ . A voltmeter has also been connected to find the potential difference across the resistor.

(i) Draw the circuit diagram.

(ii) The ammeter reads  $0.02\ \text{A}$ . What is the resistance of the voltmeter?

**Solution:**

(i) The circuit diagram is shown.

(ii) Let the resistance of the voltmeter be  $R\ \text{ohm}$ . The equivalent resistance of voltmeter ( $R\ \text{ohm}$ ) and  $100\ \text{ohm}$  in parallel is  $\frac{100 \times R}{100 + R} = \frac{100R}{100 + R}$

$$\text{The resistance of the ammeter} = \frac{4}{3}\ \Omega$$

$$\text{The total resistance of the circuit} = \frac{100R}{100 + R} + \frac{4}{3} + 2\ \Omega$$

The current in the circuit as read by the ammeter =  $0.02\ \text{A}$

$$\text{Now, } 0.02 = \frac{1.4}{\frac{100R}{100 + R} + \frac{4}{3} + 2}$$

$$\text{or, } \frac{100R}{100 + R} + \frac{4}{3} + 2 = \frac{1.4}{0.02} = 70$$


$$\frac{100R}{100 + R} = 70 - \frac{10}{3} = \frac{200}{3}$$

$$300R = 200R + 20000$$

$$100R = 20000$$

$$R = 200\ \Omega$$

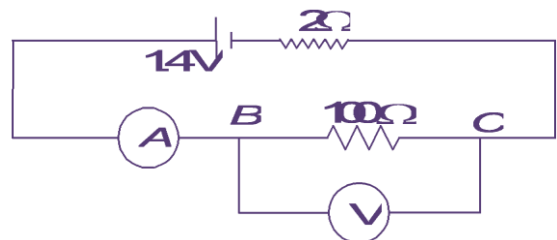Resistance of the voltmeter =  $200\ \Omega$



### Illustration 16

**Question:** What is the resistance of the filament of a bulb rated at (100 W – 250 V)? What is the current (in mA) through it when connected to 250 V line? What will be power if it is connected to a 200 V line?

**Solution:** Power  $P = VI = \frac{V^2}{R}$

$$\text{Resistance } R = \frac{V^2}{P} = \frac{250 \times 250}{100} = 625 \Omega$$

$$\text{The current through the lamp} = \frac{P}{V} = \frac{100 \text{ W}}{250 \text{ V}} = 400 \text{ mA}$$

The power of the lamp when it is connected to a 200 V line is

$$P = \frac{V^2}{R} = \frac{200 \times 200}{625} = 64 \text{ W}$$

### Illustration 17

**Question:** Forty electric bulbs are connected in series across a 220 V supply. After one bulb is fused the remaining 39 are connected again in series across the same supply. In which case will there be more illumination and why?

**Solution:** Let  $r$  be the resistance of each bulb and 40 bulbs in series will have a resistance of  $40r$  ohm. When connected across a supply voltage  $V$ , the power of the system with 40 bulbs will be

$$P_{40} = \frac{V^2}{40r}$$

When one of the bulbs is fused, the resistance of the remaining 39 bulbs in series =  $39r$  and the power of the system when connected to the same supply

$$P_{39} = \frac{V^2}{39r}$$

It is clear that  $\frac{V^2}{39r} > \frac{V^2}{40r}$

$\therefore$  power of 39 bulbs in series is greater.

### Illustration 18

**Question:** Calculate the value of current (in mA) required to deposit 0.72g of chromium in second. If E.C.E of chromium is  $0.00018 \text{ g C}^{-1}$ . 4

**Solution:** Here,  $I = ?$ ,  $m = 0.72 \text{ g}$ ,

$$t = 4, z = 0.00018 \text{ g C}^{-1}$$

As  $m = zIt$

$$\therefore I = \frac{m}{zt} = \frac{0.72}{0.00018 \times 4 \times 60 \times 60} = 1000 \text{ A}$$

### Illustration 19

**Question:** A metal plate of surface area 250 sq.cm is to be coated on both sides with a metal by electrolysis. How long will it take to deposit metal 0.01 cm in thickness if a current of 1.5 A is used. Given ECE of metal is  $0.001 \text{ g C}^{-1}$ , density of metal =  $27 \text{ g cm}^{-3}$ .

**Solution:** Area,  $A = 2 \times 250 \text{ cm}^2 = 500 \text{ cm}^2$ ,  $t = ?$

thickness,  $d = 0.01 \text{ cm}$ ,  $z = 0.00033 \text{ g C}^{-1}$

density,  $\rho = 27 \text{ g cm}^{-3}$ ,  $I = 1.5 \text{ A}$

Mass of metal deposited

$$= \text{volume} \times \text{density} = A \times d \times \rho = 500 \times 0.01 \times 27 = 135 \text{ gram}$$

$$\text{As } t = \frac{m}{zI} = \frac{135}{0.001 \times 60 \times 60 \times 1.5} = 25 \text{ hrs}$$

### Illustration 20

**Question:** The cold junction of thermo couple is kept at  $9^{\circ}\text{C}$ . Calculate the temperature at which thermo emf would be maximum. Given that the thermo emf changes sign at 800 K.

**Solution:** Here,  $\theta_0 = 10^{\circ}\text{C}$ ;  
 $\theta_1 = 800 \text{ K} = 800 - 273 = 527^{\circ}\text{C}$   
 $\theta_n = ?$   
we known,  $\theta_n = \frac{\theta_i + \theta_0}{2} = \frac{527 + 9}{2} = 268^{\circ}\text{C}$

### Illustration 21

**Question:** The e.m.f.  $E$  (in mV) of a certain thermocouple is found to vary with  $\theta$  in accordance with the relation.  $E = 40\theta - \frac{\theta^2}{20}$ . Where  $\theta$  is the temperature of the hot junction, the cold junction being at  $0^{\circ}\text{C}$ . What is the neutral temperature of the thermocouple.


**Solution:** At neutral temperature,  $\theta_n$ , thermo emf becomes maximum.

$$\text{Hence, } \left( \frac{dE}{d\theta} \right)_{\text{at } \theta_n} = 0$$
$$\text{or } \frac{d}{d\theta} \left( \theta - \frac{\theta^2}{20} \right)_{\text{at } \theta_n} = 0$$
$$\text{or } 40 - 2\theta_n / 20 = 0$$
$$\text{or } \theta_n = \frac{40 \times 20}{2} = 400^{\circ}\text{C}$$
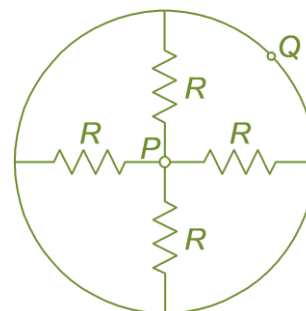
## PROFICIENCY TEST


The following questions deal with the basic concepts of this section. Answer the following briefly. Go to the next section only if your score is at least 80%. Do not consult the Study Material while attempting these questions.

- Two wires, when connected in series, have an equivalent resistance of  $18 \Omega$  and when connected in parallel, have an equivalent resistance of  $4 \Omega$ . Find their resistances.
- If each resistance is  $R$  ohms, what is the resistance across  $PQ$ ? (take  $R = 4\Omega$ )






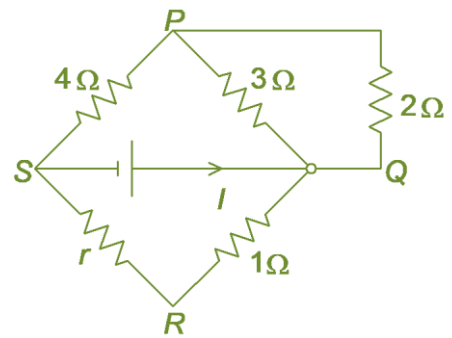3. Find the value of  $r$  if  $I = 1$  A and potential difference across  $PQ$  is 1 V.




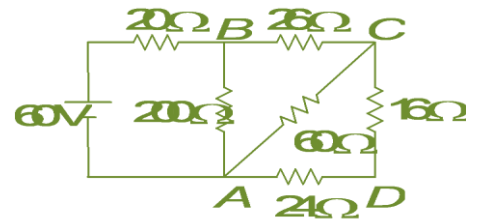4. Find the current drawn from the battery in the circuit.




5. A wire has a resistance of  $2\ \Omega$  at  $25^\circ\text{C}$  and  $2.5\ \Omega$  at  $100^\circ\text{C}$ . The temperature coefficient of resistance of the wire is  $x \times 10^{-6}/^\circ\text{C}$ . Find  $x$
6. A battery of 24 accumulators of emf  $2.5\ \text{V}$  each is charged from  $240\ \text{V}$  d.c at  $3\ \text{A}$  through an external resistance. Assuming nil internal resistance for accumulators, calculate the external resistance.

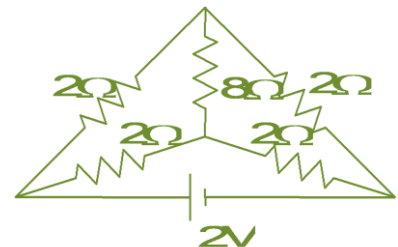7. Find out the current through the cell.




8. Two cells of same emf but differing internal resistances  $r_1 = 4\ \Omega$  and  $r_2 = 2\ \Omega$  are connected in series with an external resistance  $R$ . The potential drop across first cell is zero. Find the value of external resistance  $R$ .

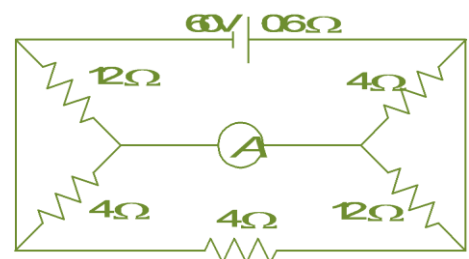9. In the circuit given, find the reading of the ammeter.



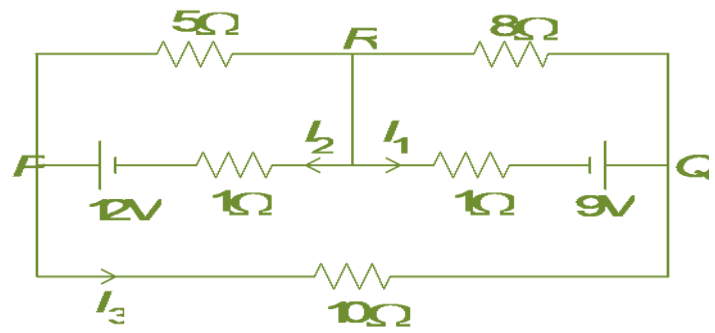10. (a) Calculate the three currents  $I_1$ ,  $I_2$  and  $I_3$  indicated in the following circuit diagram in mA.  
 (b) Also find the potential differences between the points  $P$  and  $R$  and  $R$  and  $Q$  in mV.



## ANSWERS TO PROFICIENCY TEST

1.  $12\ \Omega, 6\ \Omega$
2.  $1\ \Omega$
3.  $25\ \Omega$
4.  $1\ \text{A}$
5.  $3600$
6.  $60\ \Omega$
7.  $1\ \text{A}$
8.  $2\ \Omega$
9.  $8\ \text{A}$
10. (a)  $I_1 = 850\ \text{mA}, I_2 = 2140\ \text{mA}, I_3 = 171\ \text{mA}$   
(b)  $V_{PR} = -9850\ \text{mV}, V_{RQ} = 8170\ \text{Mv}$

## SOLVED OBJECTIVE EXAMPLES

### Example 1:

Three resistors are connected to form the sides of a triangle  $ABC$ . The resistance of the side  $AB$  is  $40 \Omega$ , of side  $BC$  is  $60 \Omega$  and of side  $CA$  is  $100 \Omega$ . The effective resistance between points  $A$  and  $B$  in ohm is


- (a) 32                                      (b) 50                                      (c) 64

### Solution:

Between the junctions  $A$  and  $B$  two resistances  $160$  ohms and  $40$  ohms are in parallel.

$$\frac{160 \times 40}{160 + 40} = 32 \Omega$$


$\therefore$  (a)

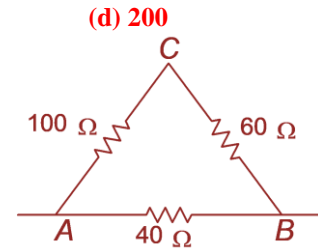

### Example 2:

In the circuit shown in the figure the  $5\text{-}\Omega$  resistor develops heat at the rate of  $13.5$  cal/s. The heat developed per second in the  $2\text{-}\Omega$  resistor is

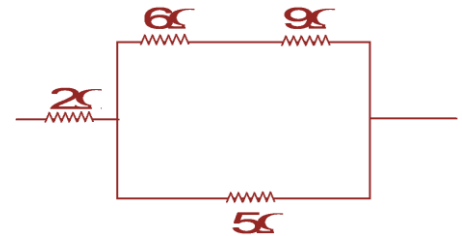- (a) 1.2 Cal                                      (b) 4.8 Cal  
(c) 9.6 Cal                                      (d) 10.8 Cal



### Solution:

If current in  $2\Omega$  is  $I$  then current in the  $5\Omega$  branch =  $\frac{15}{20}i = \frac{3}{4}i$

$$13.5 = \left(\frac{3}{4}i\right)^2 \cdot 5$$

$$i^2 = \frac{16 \times 13.5}{5 \times 9}$$

Heat developed per second in  $2\Omega$  is  $\frac{16 \times 13.5}{5 \times 9} \times 2 = 9.6$  Cal

$\therefore$  (c)

### Example 3:

A cell sends a current through a resistance  $R_1$  for time  $t$  and next the same cell sends a current through another resistance  $R_2$  for the same time  $t$ . If same quantity of heat is developed in both the resistances, then the internal resistance of the cell is

- (a)  $\frac{R_1 + R_2}{2}$                                       (b)  $\frac{R_1 - R_2}{2}$                                       (c)  $\sqrt{R_1 R_2}$                                       (d)  $\frac{\sqrt{R_1 R_2}}{2}$

### Solution:

$$i_1 = \frac{E}{R_1 + r}; i_2 = \frac{E}{R_2 + r}$$

$$H = i_1^2 R_1 t = i_2^2 R_2 t$$

$$\left(\frac{E}{R_1 + r}\right)^2 R_1 t = \left(\frac{E}{R_2 + r}\right)^2 R_2 t, \quad \frac{R_2 + r}{R_1 + r} = \sqrt{\frac{R_2}{R_1}}$$

$$\frac{R_2 - R_1}{R_1 + r} = \frac{\sqrt{R_2} - \sqrt{R_1}}{\sqrt{R_1}}$$

$$R_1 + r = \sqrt{R_1} \frac{(R_2 - R_1)}{\sqrt{R_2} - \sqrt{R_1}} = \sqrt{R_1} (\sqrt{R_2} + \sqrt{R_1})$$

$$R_1 + r = \sqrt{R_1 R_2} + R_1$$


$$r = \sqrt{R_1 R_2}$$

∴ (c)

**Example 4:**

Two identical batteries each of e.m.f 2 V and internal resistance 1 Ω are connected to a resistance  $R = 0.5 \Omega$  as shown in circuit. The maximum power that can be developed across  $R$  is

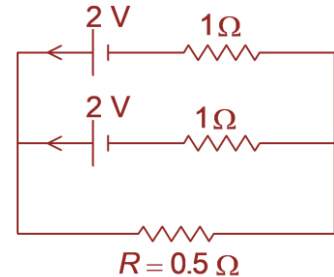- (a) 1.28 W                      (b)  $\frac{8}{9}$  W  
 (c) 2 W                              (d) 3.2 W



**Solution:**

$$2 = (i_1 + i_2) 0.5 + 1i_2$$

$$i_1 = i_2$$

$$2 = 2i_1 (0.5) + i_1$$

$$= 2i_1$$

$$i_1 = 1 \text{ A}, \quad i_2 = 1 \text{ A}$$

∴ the current through 0.5 Ω, resistor  $i = i_1 + i_2 = 2 \text{ A}$

Maximum power developed across  $R = i^2 R = 2^2 (0.5) = 2 \text{ W}$

∴ (c)

**Example 5:**

A current of 2 A is supplied by a cell of emf 1.5 V having internal resistance 0.15 Ω. The potential difference, in volts across the ends of the cell will be

- (a) 1.35                      (b) 1.5                      (c) 1.0                      (d) 1.2

**Solution:**

$$\text{Potential difference across the ends of the cell} = \varepsilon - iR = 1.5 - (2)(0.15) \\ = 1.5 - 0.3 = 1.2 \text{ V}$$

∴ (d)

**Example 6:**

Two electric bulbs whose resistances are in the ratio 1 : 2 are connected in parallel to a constant voltage source. The power dissipated in them have the ratio


- (a) 1 : 2                      (b) 1 : 1                      (c) 2 : 1                      (d) 1 : 4

**Solution:**

$$\frac{R_1}{R_2} = \frac{1}{2}$$

$$\text{Ratio of power dissipated in electric bulbs} \quad \frac{P_1}{P_2} = \frac{V^2}{R_1} \times \frac{R_2}{V^2} = \frac{2}{1}$$

∴ (c)

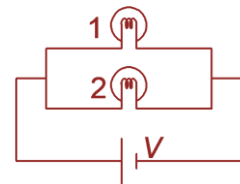

**Example 7:**

A piece of fuse wire is about to melt when the current passing through it is 5 A. When carrying this current it dissipates 2.5 J of energy per sec. What is the resistance of the fuse wire?

- (a) 0.5 Ω                      (b) 10 Ω                      (c) 0.1 Ω                      (d) 2 Ω

**Solution:**

$$\text{When the fuse wire melts energy dissipated, } P = i^2 R \\ = 5^2 R = 2.5 \text{ J}$$

$$\text{Resistance of the fuse wire} \quad R = \frac{2.5}{25} = 0.1 \Omega$$

∴ (c)

**Example 8:**

Two identical heaters produce heat  $H_1$  in time 't' when connected in parallel across the main supply.

They produce heat  $H_2$  in time 't' when connected in series. Then  $\frac{H_1}{H_2}$  is

- (a)  $\frac{1}{4}$                       (b) 4                      (c)  $\frac{1}{2}$                       (d) 2

**Solution:**

When connected in parallel, heat produced  $H_1 = \frac{V^2}{R_{eq}} t = \frac{V^2}{\frac{R}{2}} t = \frac{2V^2}{R} t$

When connected in series, heat produced  $H_2 = I^2 R_{eq} t$

$$= \left( \frac{V}{2R} \right)^2 (2R) t$$

$$\frac{H_1}{H_2} = \left( \frac{2V^2 t}{R} \right) \left( \frac{2R}{V^2 t} \right) = 4$$

∴ (b)

**Example 9:**

The electrical installation in a building is protected by a 15 A fuse. If the supply voltage is 220 V, the maximum number of 60 W bulbs that can be used in the building is

- (a) 44                      (b) 55                      (c) 88                      (d) 66

**Solution:**

Current through each bulb  $I = \frac{60}{220} = \frac{3}{11}$  A

⇒ Number of bulbs,  $n = \frac{15}{\frac{3}{11}} = \frac{15 \times 11}{3} = 55$

∴ (b)

**Example 10:**

Letter A is constructed using a uniform wire of resistance 1 Ω per cm, the sides of the letter being of length 20 cm each, the cross piece of length 10 cm and the angle at the apex being 60°. The effective resistance between two legs of the letter is


- (a)  $\frac{80}{3}$  Ω                      (b) 12 Ω                      (c)  $\frac{13}{3}$  Ω                      (d)  $\frac{70}{3}$  Ω

**Solution:**

The distribution of resistances are as shown.

$$\begin{aligned} \text{Effective resistance } R &= \frac{20 \times 10}{20 + 10} + 10 + 10 \\ &= \frac{20}{3} + 20 = \frac{80}{3} \Omega \end{aligned}$$


∴ (a)

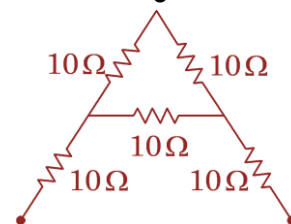

## SOLVED SUBJECTIVE EXAMPLES
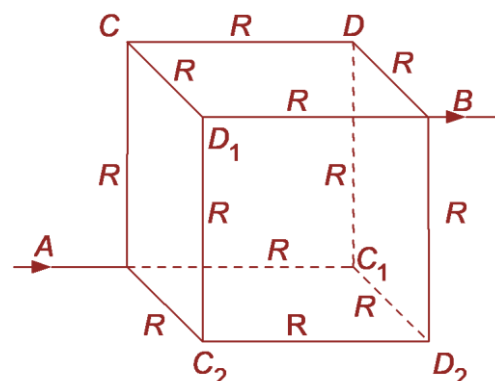
### Example 1:

The Figure shows a cube made of wires each having a resistance  $R = 6\Omega$ . The cube is connected into a circuit across a body diagonal  $AB$  as shown. Find the equivalent resistance of the network in this case.



### Solution:

Let us search the points of same potential. Since the three edges of the cube from  $A$  viz.,  $AC$ ,  $AC_1$  and  $AC_2$  are identical in all respects the circuit points  $C$ ,  $C_1$  and  $C_2$  are at the same potential. Similarly for the point  $B$  the sides  $BD$ ,  $BD_1$  and  $BD_2$  are symmetrical and the points  $D$ ,  $D_1$  and  $D_2$  are at the same potential.

Next let us bring together the points  $C$ ,  $C_1$  and  $C_2$  and also  $D$ ,  $D_1$  and  $D_2$ .

Then the cube will look as follows.

The resistance between  $A$  and  $C = \frac{R}{3}$

The resistance between  $C$  and  $D = \frac{R}{6}$

The resistance between  $D$  and  $B = \frac{R}{3}$

The circuit is equivalent to  $\frac{R}{3}$ ,  $\frac{R}{6}$  and  $\frac{R}{3}$  in series which is equal to  $\frac{5}{6} R = 5\Omega$



### Example 2:

12 cells each of negligible internal resistance and having the same emf are connected in series and are kept in a closed box. Some of the cells are wrongly connected. This box is connected in series with an ammeter and two cells (in series combination) identical with the other cells. The current is 3A when the cells and box aid each other and is 2A when the cells and the box oppose each other. How many cells in the box are wrongly connected?

### Solution:

Let  $x$  cells be connected correctly and  $y$  cells be connected wrongly. According to the given condition

$$x + y = 12 \quad \dots (i)$$

Let  $E$  be the emf of each cell and  $R$  be the external resistance

$$\text{Then, } \frac{(x - y)E + 2E}{R} = 3 \quad \dots (ii)$$

$$\text{And } \frac{(x - y)E - 2E}{R} = 2 \quad \dots (iii)$$


From equation (i), (ii) and (iii),

$$x = 11 \text{ and } y = 1$$

Hence 1 cell is wrongly connected.

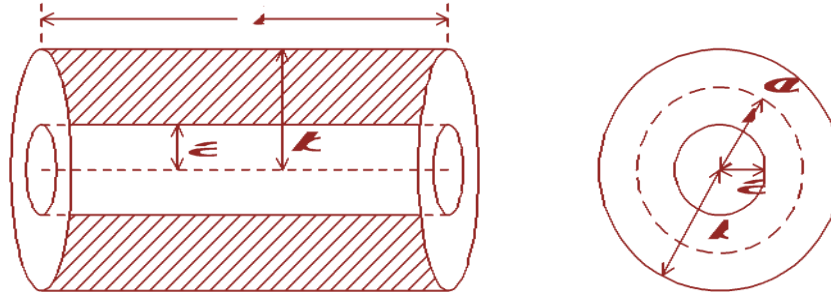**Example 3:**

A homogeneous poorly conducting medium of resistivity  $\rho = 20 \pi$  SI unit fills up the space between two thin coaxial ideally conducting cylinders. The radii of the cylinders are equal to  $a$  and  $b$  with  $a < b$  ( $b = 2a$ ), the length of each cylinder is  $l = 1$  m. Neglecting the edge effects, find the resistance of the medium between the cylinders. ( $\log_e 2 = 0.7$ )



**Solution:**

The current will be conducted radially outwards from the inner conductor to the outer conductor. The area of cross-section for the conduction of the current is therefore the area of an elementary cylindrical shell which varies with radius. The length of the conducting shell is measured radially from radius  $a$  to radius  $b$ . Consider an elementary cylindrical shell of radius  $r$  and thickness  $dr$ . Its area of cross-section (normal to flow of current) =  $(2\pi r l)$  and its length =  $dr$ .


Hence the resistance of the elementary cylindrical shell of the medium is 
$$dR = \frac{\rho dr}{2\pi r l} = \frac{\rho}{2\pi l} \left[ \frac{dr}{r} \right]$$

The resistance of the medium is obtained by integrating for  $r$  from  $a$  to  $b$ .  
Hence required resistance

$$R = \frac{\rho}{2\pi l} \int_a^b \frac{dr}{r} = \frac{\rho}{2\pi l} [\log_e r]_a^b = \left( \frac{\rho}{2\pi l} \right) \log_e \frac{b}{a} = 7 \Omega$$

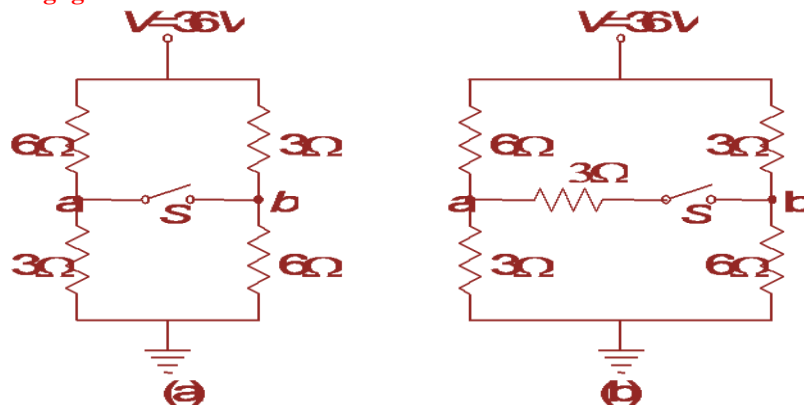**Example 4:**

A convention is often employed in circuit diagrams where the battery (or other power source) is not shown explicitly but the points connected to the source are indicated by voltage and ground respectively. The following two circuit diagrams are drawn on this convention. Assume the battery resistance is negligible.



- (a) In Figure (a), what is the potential difference  $V_{ba}$  when the switch  $S$  is open?
- (b) In Figure (b), what is the potential difference  $V_{ba}$  when switch  $S$  is open?


**Solution:**

The given circuit is equivalent to

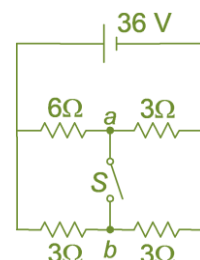(a) Potential at the point  $a = V_a = 36 - \left( \frac{6}{9} \times 36 \right) = 12V$

Potential at the point  $b = V_b = 36 - \left( \frac{3}{9} \times 36 \right) = 24V$

Hence  $V_{ba}$  = Potential difference between  $b$  and  $a$





$$= V_b - V_a = 24 - 12 = 12 \text{ V}$$

(b) In figure (b) we have a resistance of  $3 \Omega$  added to the switch circuit. However this will **NOT** affect the current and potential distributions when the switch  $S$  is open. Hence the potential difference  $V_{ba} = 12 \text{ V}$  (as in the case (a) above).

**Example 5:**

**Find the emfs  $\epsilon_1$  and  $\epsilon_2$  in the circuit of the following diagram and the potential difference between the points  $a$  and  $b$ .**

**Solution:**

(a) It is clear that  $1 \text{ A}$  current flows in the circuit from  $b$  to  $a$ .

Applying Kirchhoff's law to the loop  $PabP$ ,

$$20 - E_1 = 6 + 1 - 4 - 1 = 2$$

Hence  $E_1 = 18 \text{ V}$


Also applying Kirchhoff's law to the loop  $PaQbP$ ,

$$20 - E_2 = 6 + 1 + (1 \times 2) + (2 \times 2) = 13$$

Hence  $E_2 = 7 \text{ V}$

Thus the potential difference between the points  $a$  and  $b$  is


$$V_{ab} = 18 - 1 - 4 = 13 \text{ V}$$

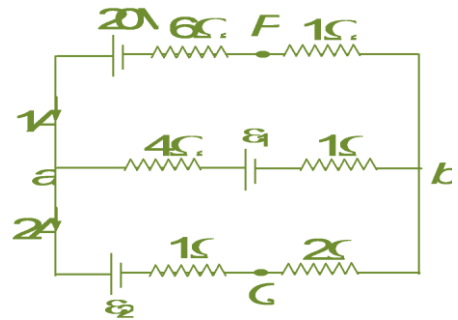

**Example 6:**

**In the circuit  $V_1$  and  $V_2$  are two voltmeters of resistances  $3000 \text{ ohm}$  and  $2000 \text{ ohm}$  respectively. The resistances  $R_1 = 2000 \text{ ohm}$  and  $R_2 = 3000 \text{ ohm}$  and the emf of the battery  $\epsilon = 200 \text{ V}$ . The battery has negligible internal resistance. Find the readings of the voltmeters  $V_1$  and  $V_2$  when**

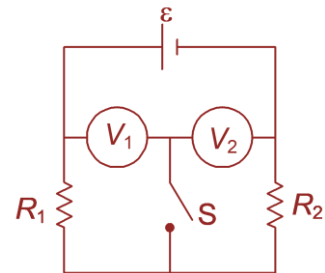- (i) the switch  $S$  is open and**
- (ii) the switch  $S$  is closed.**



**Solution:**

(i) When  $S$  is open

$V_1$  and  $V_2$  in series have a resistance  
 $= 3000 + 2000 = 5000 \Omega$

$R_1$  and  $R_2$  in series have a resistance  
 $= 2000 + 3000 = 5000 \Omega$

$5000 \text{ ohm}$  and  $5000 \text{ ohm}$  in parallel are equivalent to

$$\frac{5000 \times 5000}{10000} = 2500 \Omega$$

$$\text{Circuit current} = \frac{200}{2500} = \frac{2}{25} \text{ A}$$

Current in the branch of  $V_1$  and  $V_2$

$$= \frac{1}{2} \left( \frac{2}{25} \right) = \frac{1}{25} \text{ A}$$

$$\text{p.d. across } V_1 = \left( \frac{1}{25} \text{ A} \right) (3000 \text{ ohm}) = 120 \text{ V}$$

$$\text{p.d. across } V_2 = \left( \frac{1}{25} \text{ A} \right) (2000 \text{ ohm}) = 80 \text{ V}$$


$\therefore$  the voltmeters  $V_1$  and  $V_2$  read  **$120 \text{ V}$  and  $80 \text{ V}$  respectively.**

(ii)  $V_1$  and  $R_1$  are in parallel.

Similarly  $V_2$  and  $R_2$  in parallel have an equivalent resistance of  $1200 \text{ ohm}$ .

As these two equivalent resistances are same

p.d. across  $AS =$  p.d. across  $SB$   
 $\therefore$  p.d. across  $AS = 100 \text{ V}$   
 This is registered by  $V_1$   
 Similarly p.d. across  $SB = 100 \text{ V}$   
 This is registered by  $V_2$   
 Similarly p.d. across  $SB = 100 \text{ V}$   
 This is registered by  $V_2$ .

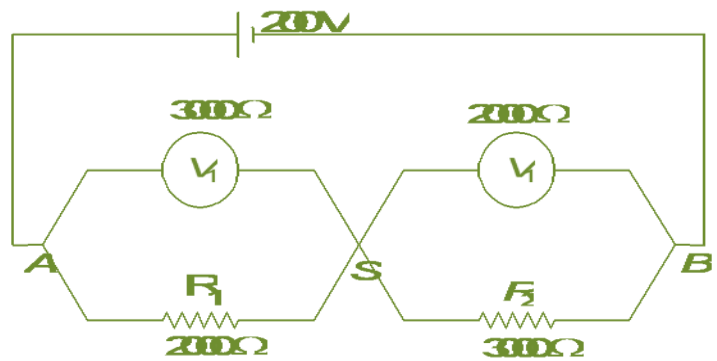

**Example 7:**

A fuse made of lead wire has an area of cross-section  $0.2 \text{ mm}^2$ . On short circuiting, the current in the fuse wire reaches 30 amp. How long (in  $10^{-4} \text{ s}$ ) after the short circuiting will the fuse begin to melt?  
 Specific heat capacity of lead =  $134.4 \text{ J kg}^{-1} \text{ K}^{-1}$ .  
 Melting point of lead =  $327^\circ\text{C}$   
 Density of lead =  $11340 \text{ kg/m}^3$   
 Resistivity of lead =  $22 \times 10^{-8} \text{ ohm-m}$   
 Initial temperature of the wire =  $20^\circ\text{C}$   
 Neglect heat loss.

**Solution:**

If  $L$  be the length of the wire, its resistance

$$R = \frac{\rho L}{A} = \frac{(22 \times 10^{-8})L}{(0.2 \times 10^{-6})m^2}$$

Heat produced in the wire in one second =  $I^2 R = (30)^2 R \text{ J}$

Heat required to raise the temperature of the wire to  $327^\circ\text{C}$

$$Q = ms\Delta T = (LAd)(134.4)(307) \text{ J}$$

Time required to melt the wire

$$\begin{aligned} &= \frac{Q}{I^2 R} = \frac{LAd \times 134.4 \times 307}{I^2 \times \rho L} \times A \\ &= \frac{A^2 d}{I^2 \rho} \times 134.4 \times 307 \\ &= \frac{(0.2 \times 10^{-6})^2}{900} \times \frac{11340}{22 \times 10^{-8}} \times 134.4 \times 307 \\ &= 0.0945 = 945 \times 10^{-4} \text{ s} \end{aligned}$$

**Example 8:**

What amount of heat will be generated in a coil of resistance  $R = 30 \Omega$  due to a charge  $q = 1 \text{ C}$  passing through it if the current in the coil decreases down from maximum to zero uniformly in a time interval of  $t_0 = 10 \text{ s}$ .

**Solution:**

Since current is a uniform function of time, we can write

$$i = \alpha t + \beta \text{ where } \alpha \text{ and } \beta \text{ are constant.}$$

at  $t = 0, i = i_0$  (maximum current) and

at  $t = t_0, i = 0$

$$\therefore \alpha = -\frac{i_0}{t_0}, \beta = i_0$$

$$\Rightarrow i = i_0 - \frac{i_0}{t_0} t$$

Amount of heat generated in the resistor is  $H = \int_0^{t_0} i^2 R dt$

$$= i_0^2 R \int_0^{t_0} dt + \frac{i_0^2}{t_0^2} R \int_0^{t_0} t^2 dt - \frac{2i_0^2}{t_0} R \int_0^{t_0} t dt$$

$$H = \frac{i_0^2 R t_0}{3} \quad \dots (i)$$

Also  $i = \frac{dq}{dt} = i_0 - \frac{i_0}{t_0} t$

$$\int_0^{q_0} dq = i_0 \int_0^{t_0} dt - \frac{i_0}{t_0} \int_0^{t_0} t dt \Rightarrow q_0 = \frac{i_0 t_0}{2}$$


Putting value of  $i_0$  in (i)

$$H = \frac{4q_0^2 R}{3t_0} = 4 \text{ J}$$

### Example 9:

A galvanometer together with an unknown resistance in series is connected across two identical batteries each of 9 V. When the batteries are connected in series the galvanometer records a current of 1 ampere and when the batteries are in parallel the current is 0.6 ampere. What is the internal resistance of the battery?

### Solution:

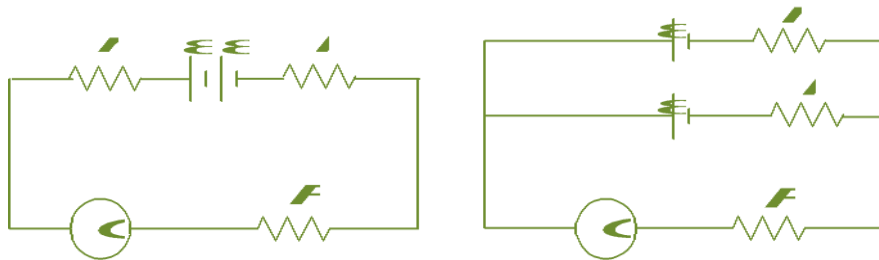

Emf of each cell is  $\varepsilon = 9 \text{ V}$

Let the internal resistance of each cell be  $r$ .

Let the resistance of the galvanometer be  $G$ .

Let the unknown resistance in series with the galvanometer be  $R$ .

(i) Let the cells be in series.

The emf of the circuit =  $2\varepsilon = 18 \text{ V}$

The resistance of the circuit =  $(R + G + 2r) \Omega$

The current in the circuit  $\frac{18}{R+G+2r} = 1 \text{ A}$  (given) ... (i)

(ii) When the cells are in parallel the emf of the circuit =  $\varepsilon = 9 \text{ V}$

The resistance of the circuit =  $R + G + \frac{r \cdot r}{r+r}$

$$= \left( R + G + \frac{r}{2} \right) \Omega$$

The current in the circuit  $\frac{9}{R+G+\frac{r}{2}} = 0.6 \text{ A}$  ... (ii)

From equations (1) and (2), we get

$$R + G + 2r = 18$$

$$\text{and } R + G + \frac{r}{2} = \frac{9}{0.6} = 15$$

Subtracting these two equations, we get

$$\frac{3}{2}r = 3 \quad \Rightarrow r = 2 \Omega$$


Internal resistance of each cell =  $2\Omega$

**Example 10:**

- (i) A galvanometer having a coil of resistance of 100 ohms gives a full scale deflection when a current of one milliampere is passed through it. What is the value of the resistance (in  $m\Omega$ ) which can convert this galvanometer into ammeter giving a full scale deflection for a current of 10 amperes?
- (ii) When this modified galvanometer is connected across the terminals of a battery it shows a current of 4 ampere. The current drops to 1 ampere when a resistance of 1.5 ohm is connected in series with the modified galvanometer. Find the emf of the battery.

**Solution:**

- (i) The value of shunt resistance.

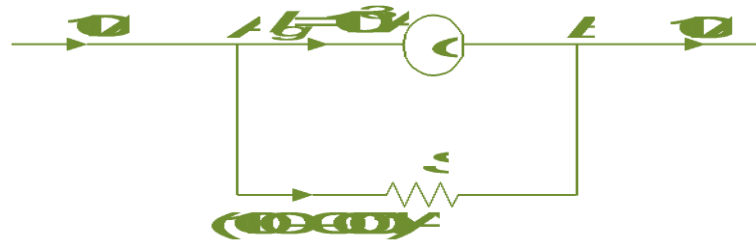

Let the shunt resistance required be  $S \Omega$ . The galvanometer permits the full-scale deflection current of  $I_g = 1 \times 10^{-3} \text{ A}$  through it. When the current is 10 A.

Then,  $(10 - 0.001) S = 0.001 \times 100$

$$S = \frac{0.1}{9999} = \frac{100}{9999} \approx \frac{1}{100} \Omega = 10 \text{ m}\Omega$$

- (ii) Emf of the battery and its internal resistance: The combined resistance of the galvanometer and the shunt

is given by  $\frac{\frac{1}{100} \times 100}{\frac{1}{100} + 100} \Omega \approx \frac{1}{100} \Omega$

This combined resistance and the internal resistance of the battery in series give a total resistance of  $\left(\frac{1}{100} + r\right)$  ohm to the circuit.

If  $\varepsilon$  be the emf of the battery, then

$$\frac{\varepsilon}{r+0.01} = 4A \quad \dots (i)$$

Now with an additional resistance of 1.5  $\Omega$  in series

$$\frac{\varepsilon}{r+0.01+1.5} = 1A \quad \dots (ii)$$

From equations (1) and (2), we get  $\frac{r+1.51}{r+0.01} = 4$

$$3r = 1.47$$

Internal resistance  $r = 0.49 \Omega$

Substituting this value of  $r$  in equation (1),

$$\varepsilon = 4 \times 0.5 = 2 \text{ V}$$

## MIND MAP

### 1. Electric current

$$I = \lim_{\Delta t \rightarrow 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$$

### 2. Ohm's law

$$V = IR$$

where  $R$  is called the resistance

### 3. (i) Resistance

$$R = \rho \frac{l}{A}$$

#### (ii) Effect of temperature

$$R = R_0 (1 + \alpha\theta)$$

#### (iii) Grouping of resistors

(a) When resistors are in series

$$R = R_1 + R_2 + R_3 \dots$$

(b) When resistors are in parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

### 4. Kirchhoff's law

(i) 1st law:

at any junction of circuit elements

$$\sum I = 0$$

(ii) 2nd law:

around any close loop

$$\sum V = 0$$

### 5. (a) When a cell of emf ( $\epsilon$ ) is in a circuit

$$(i) I = \frac{E}{R+r}$$

where  $r$  is internal resistance of the cell

$$(ii) V_{AB} = E - Ir$$

#### (b) Grouping of cells

(i) When cells are in series

$$I = \frac{nE}{R+nr}$$

(ii) When cells are in parallel

$$I = \frac{m\epsilon}{mR+r}$$

(iii) cells are in multiple arc

$$I = \frac{mn\epsilon}{mR+nr}$$

(iv) For maximum current  $mR = nr$

## CURRENT ELECTRICITY

**6. Voltmeter:** is used in parallel in a circuit and should have very high resistance

**7. Ammeter:** is used in series in a circuit and should have very small resistance.

**8. Potentiometer:** is a method of measurement involving a condition of no current flow and e.m.f.s are compared independent of the internal resistance of the source

### 9. Wheatstone bridge

is an arrangement of four resistances used for measuring one of them in terms of others.

For a balanced Wheat stone bridge  $\frac{P}{Q} = \frac{R}{S}$

### 10. Heating effect of current

(i) Joules law

$$H = I^2 R t$$


(ii) Electrical power

$$p = VI = I^2 R = \frac{V^2}{R}$$


## EXERCISE – I

### NEET-SINGLE CHOICE CORRECT

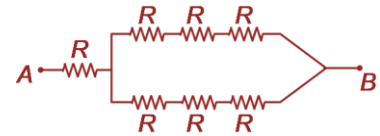
1. The effective resistance of the network between points *A* and *B*
- (a)  $4R$  (b)  $2R$   
 (c)  $10R$  (d)  $5R/2$



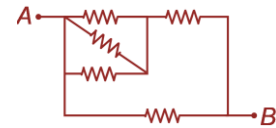
2. Five identical resistances are connected in a network as shown. The resistance measured between *A* and *B* is  $1 \Omega$ . Each resistance is
- (a)  $1/4 \Omega$  (b)  $4/7 \Omega$   
 (c)  $7/4 \Omega$  (d)  $8/7 \Omega$



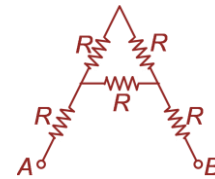
3. What is the effective resistance between *A* and *B*
- (a)  $\frac{2R}{3}$  (b)  $\frac{R}{3}$   
 (c)  $\frac{6R}{3}$  (d)  $\frac{8R}{3}$



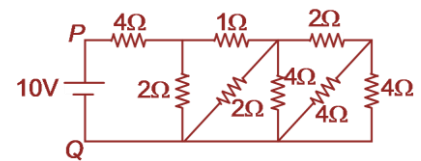
4. Find the equivalent resistance between *P* and *Q*
- (a)  $10 \Omega$  (b)  $5 \Omega$   
 (c)  $15 \Omega$  (d)  $20 \Omega$



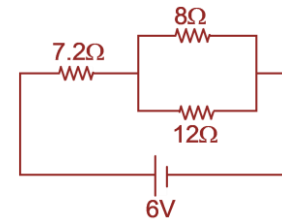5. In the circuit shown,
- (a) the pd across  $8 \Omega$  is  $3.6 \text{ V}$   
 (b) the pd across  $12 \Omega$  is  $2.4 \text{ V}$   
 (c) the pd across  $7.2 \Omega$  is  $5.6 \text{ V}$   
 (d) the current drawn from the battery is  $1.5 \text{ A}$



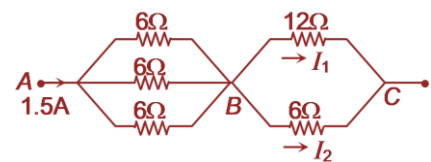6. In the network shown,
- (a)  $V_{AB} = +3.0 \text{ V}$  (b)  $V_{CB} = +6.0 \text{ V}$   
 (c)  $I_1 = 1.5 \text{ A}$  (d)  $I_2 = 0.5 \text{ A}$




7. In the network shown,
- (a)  $V_{AB} = +2 \text{ V}$  (b)  $V_{DA} = +3 \text{ V}$   
 (c)  $V_{BD} = +2 \text{ V}$  (d)  $V_{CD} = -3 \text{ V}$




8. EMF represents
- (a) potential energy (b) a force  
 (c) work done per unit charge (d) potential difference
9. When a cell is undergoing charging process
- (a) there is no voltage drop in its internal resistance  
 (b) its terminal potential is less than its EMF  
 (c) its terminal potential is more than its EMF  
 (d) its terminal potential is zero

10. The specific resistance of a wire  
 (a) varies with its length  
 (b) varies with its cross-section  
 (c) varies with its mass  
 (d) does not depend on its length, cross-section and mass

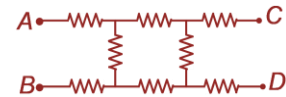
11. In the given circuit, each resistance is  $10\Omega$ . The equivalent resistance between  $A$  and  $D$  is  
 (a)  $40\Omega$  (b)  $30\Omega$   
 (c)  $20\Omega$  (d)  $10\Omega$



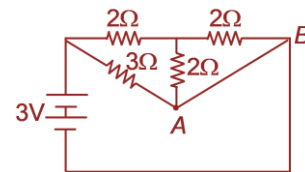12. The current in branch  $AB$  is  
 (a)  $1.5\text{ A}$  (b)  $2\text{ A}$   
 (c)  $1.33\text{ A}$  (d) infinite



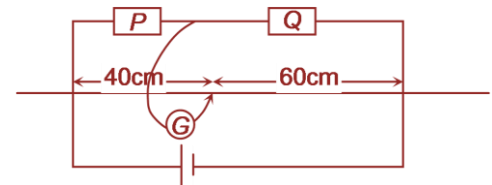
13. In a metre bridge, the gaps are closed by two resistances  $P$  and  $Q$  and the balance point is obtained at  $40\text{ cm}$ . When  $Q$  is shunted by a resistance of  $10\Omega$ , the balance point shifts to  $50\text{ cm}$ . The values of  $P$  and  $Q$  are



- (a)  $\frac{10}{3}\Omega, 5\Omega$  (b)  $20\Omega, 30\Omega$  (c)  $10\Omega, 15\Omega$  (d)  $5\Omega, \frac{15}{2}\Omega$


14. Three bulbs  $B_1$ ,  $B_2$  and  $B_3$  are connected to the mains as shown in figure. How will the incandescence of the bulb  $B_1$  be affected, if one of the bulbs  $B_2$  or  $B_3$  is disconnected from the circuit?

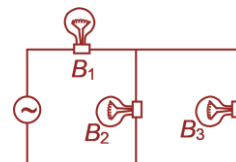- (a) no change in the incandescence  
 (b) bulb  $B_1$  will become brighter  
 (c) bulb  $B_1$  will become less brighter  
 (d) the bulb  $B_1$  may become brighter or dimmer depending upon wattage of the bulb which is disconnected.



15. The effective resistance between the terminals  $P$  and  $Q$  in following circuit is

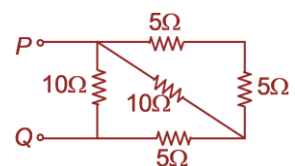- (a)  $5\Omega$  (b)  $10\Omega$   
 (c)  $25\Omega$  (d)  $30\Omega$



16. Five resistances are connected as shown in figure. The effective resistance between the points  $A$  and  $B$  is


- (a)  $\frac{10}{3}\Omega$  (b)  $\frac{20}{3}\Omega$   
 (c)  $15\Omega$  (d)  $6\Omega$




17. There are  $n$  exactly identical resistors each having resistance  $R$ . The resultant resistance when joined in parallel is  $\lambda$ , then on connecting them in series the resistance will come out be

- (a)  $\frac{\lambda}{n^2}$  (b)  $n^2\lambda$   
 (c)  $\frac{\lambda}{n^3}$  (d)  $n^3\lambda$

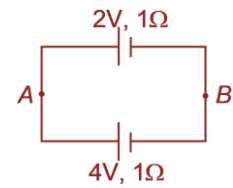18. Find the potential difference between  $A$  and  $B$   
 (a) 6V (b) 2 V  
 (c) 3 V (d) 1 V




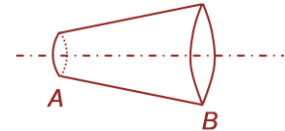19. A wire has a nonuniform cross-section as shown. A steady current is flowing through it. Then the drift speed of the electrons




- (a) is constant throughout the wire (b) decreases from  $A$  to  $B$   
 (c) increases from  $A$  to  $B$  (d) varies randomly
20. 24 identical cells, each of internal resistance  $0.5 \Omega$ , are arranged in a parallel combination of  $n$  rows, each row containing  $m$  cells in series. The combination is connected across resistor of  $3\Omega$ . In order to send maximum current through the resistor, we should have  
 (a)  $m = 12, n = 2$  (b)  $m = 8, n = 3$   
 (c)  $m = 2, n = 12$  (d)  $m = 3, n = 8$

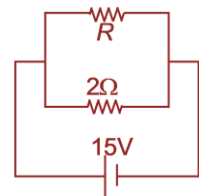21. If in the circuit power dissipation is 150 W. Then  $R$  is  
 (a)  $2\Omega$  (b)  $6\Omega$   
 (c)  $5\Omega$  (d)  $4\Omega$



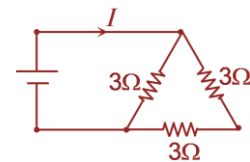22. A 3 volt battery with negligible internal resistance is connected in circuit as shown in the figure. The current  $I$  in the circuit will be  
 (a) 1.5 A (b) 2 A  
 (c)  $1/3$  A (d) 1 A



23. The total current supplied to the circuit by the battery is  
 (a) 1 A (b) 2 A  
 (c) 4 A (d) 6 A



24. The resistance of the series combination of two resistances is  $S$ . When they are joined in parallel the total resistance is  $P$ . If  $S = nP$  then the minimum possible value of  $n$  is  
 (a) 4 (b) 3  
 (c) 2 (d) 1

25. In a meter bridge experiment null point is obtained at 20 cm from one end of the wire when resistance  $X$  is balanced against another resistance  $Y$ . If  $X < Y$ , then where will be the new position of the null point from the same end, if one decides to balance a resistance of  $4X$  against  $Y$ ?  
 (a) 50 cm (b) 80 cm  
 (c) 40 cm (d) 70 cm




## EXERCISE – II

### IIT-JEE- SINGLE CHOICE CORRECT

1. In the network shown, the current  $I$  is equal to  $\frac{2}{3}$  A.


Neglecting the internal resistance of the cell, the value of  $R$  is

- (a) 3.75 (b) 10  
(c) 15 (d) 19.5

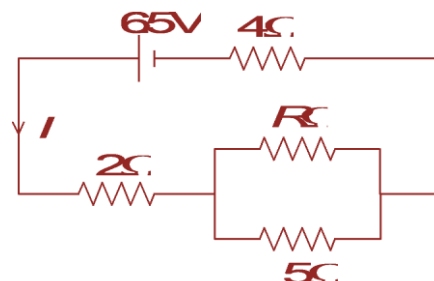

2. In the figure shown, the potentiometer wire of length  $l = 100$  cm and resistance  $9\Omega$  is joined to a cell of emf  $E_1 = 10$  V and internal resistance  $r_1 = 1\Omega$ . Another cell of emf  $E_2 = 5$  V and internal resistance  $r_2 = 2\Omega$  is connected as shown. The galvanometer  $G$  will show no deflection when the length  $AC$  is

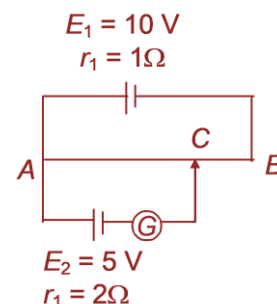- (a) 50 cm (b) 55.55 cm  
(c) 52.67 cm (d) 54.33 cm




3. There are two concentric spheres of radius  $a$  and  $b$  respectively. If the space between them is filled with medium of resistivity  $\rho$ , then the resistance of the inter gap between the two spheres will be

- (a)  $\frac{\rho}{4\pi(b+a)}$  (b)  $\frac{\rho}{4\pi}\left(\frac{1}{b} + \frac{1}{a}\right)$  (c)  $\frac{\rho}{4\pi}\left(\frac{1}{a^2} - \frac{1}{b^2}\right)$  (d)  $\frac{\rho}{4\pi}\left(\frac{1}{a} - \frac{1}{b}\right)$


4. In a group of  $N$  cells, emf of each varies directly with its internal resistance as per the equation  $E_N = 1.5 r_N$ . They are connected as shown in the figure. The current  $I$  in the circuit is

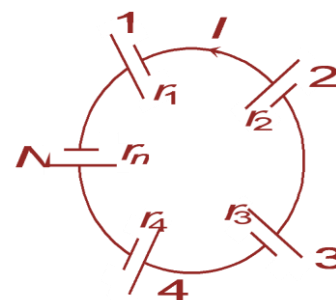- (a) 0.51 amp (b) 5.1 amp  
(c) 0.15 amp (d) 1.5 amp



5. In the circuit shown in the figure, the value of resistance  $X$ , when the potential difference between the points  $B$  and  $D$  is zero, will be

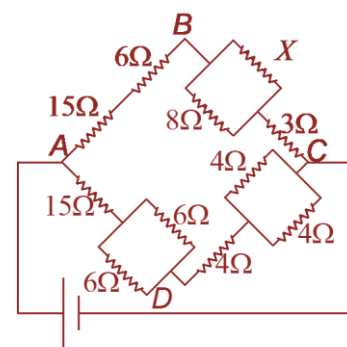- (a)  $9\Omega$  (b)  $8\Omega$   
(c)  $6\Omega$  (d)  $4\Omega$




6. An electron in the potentiometer wire experiences a force of  $2.4 \times 10^{-19}$  N. The length of the potentiometer wire is 4m. The emf of the battery connected across the wire is

- (a) 6.0 V (b) 4.8 V (c) 4.0 V (d) 2.4 V

7. In the network shown in figure, each resistance is  $R$ . The equivalent resistance between  $A$  and  $B$  is

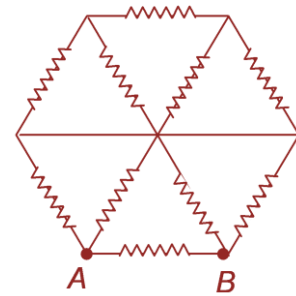- (a)  $\frac{20}{11}R$                       (b)  $\frac{19}{20}R$   
 (c)  $\frac{8}{15}R$                         (d)  $\frac{R}{2}$



8. An ammeter and a voltmeter are joined in series to a cell. Their readings are  $A$  and  $V$  respectively. If a resistance is now joined in parallel with the voltmeter, then

- (a) both  $A$  and  $V$  will increase                      (b) both  $A$  and  $V$  will decrease  
 (c)  $A$  will decrease,  $V$  will increase                      (d)  $A$  Will increase,  $V$  will decrease


9. Value of each resistance in the circuit is  $r$ . The equivalent resistance between  $A$  and  $B$  is

- (a)  $\frac{r}{4}$                               (b)  $4r$                               (c)  $\frac{2r}{5}$                               (d) 0



10. In the circuit shown, the ammeter reads 2 A. The resistance of ammeter is negligible. What is the value of  $R$ ?

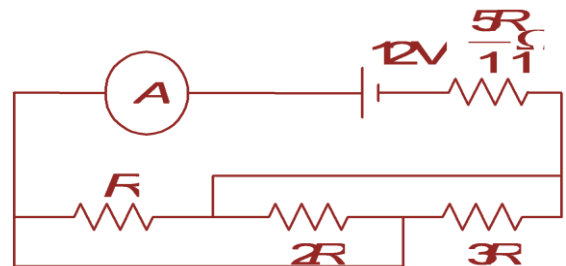- (a)  $2\ \Omega$                               (b)  $3\ \Omega$   
 (c)  $5\ \Omega$                               (d)  $6\ \Omega$




11. A galvanometer together with unknown resistance in series is connected to two identical batteries each of emf 1.5 V. When the batteries are in series the galvanometer registers a current of 1 ampere. When the batteries are in parallel the current is 0.6 ampere. What is the internal resistance of the battery?

- (a)  $5\ \Omega$                               (b)  $\frac{1}{3}\ \Omega$                               (c)  $0.2\ \Omega$                               (d)  $0.8\ \Omega$


12. The resistance across  $AB$  is

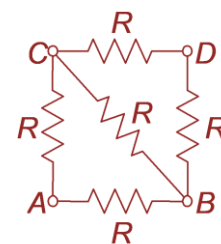- (a)  $\frac{5}{8}R$                               (b)  $\frac{7}{8}R$   
 (c)  $1R$                                 (d)  $2R$




13. In the circuit shown in figure, the current in  $2\ \Omega$  resistor is

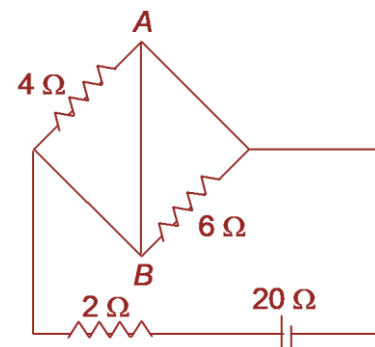- (a) 4 A                                (b) 10 A  
 (c) 5 A                                (d) none




14. The effective resistance between point  $P$  and  $Q$  of the electrical circuit shown in the figure is

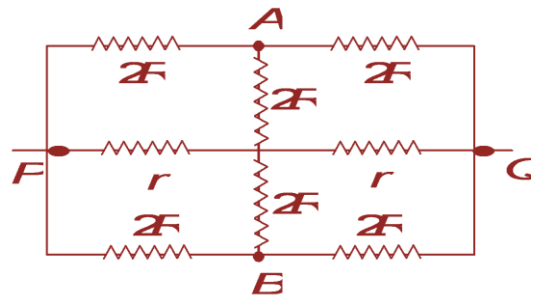- (a)  $2Rr / (R + r)$   
 (b)  $8R(R + r) / (3R + r)$   
 (c)  $2r + 4R$   
 (d)  $5R / 2R + 2r$




15. The equivalent resistance between point  $A$  and  $B$  is

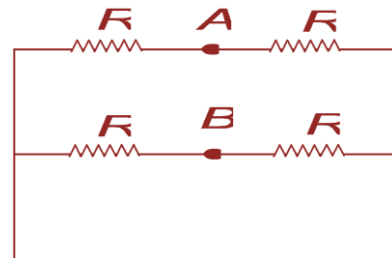- (a)  $R$   
 (b)  $R/4$   
 (c)  $4R$   
 (d)  $\frac{2R}{3}$




16. All resistance shown in circuit are  $2\Omega$  each. The current in the resistance between  $D$  and  $E$  is

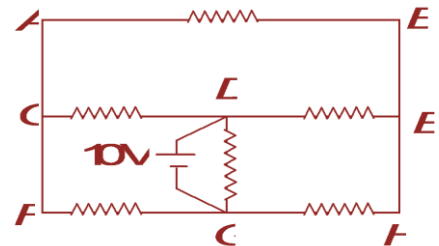- (a)  $5\text{ A}$   
 (b)  $2.5\text{ A}$   
 (c)  $1\text{ A}$   
 (d)  $7.5\text{ A}$



17. In the circuit shown in figure, power supplied by the battery is

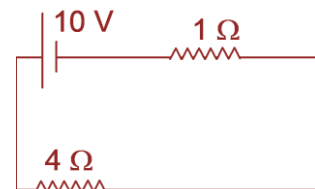- (a)  $16\text{ W}$   
 (b)  $20\text{ W}$   
 (c)  $4\text{ W}$   
 (d)  $18\text{ W}$




18. A millimeter of range  $10\text{ mA}$  has a coil of resistance  $1\Omega$ . To use it as an ammeter of range  $1\text{ A}$ , the required shunt must have a resistance of

- (a)  $\frac{1}{101}\Omega$   
 (b)  $\frac{1}{100}\Omega$   
 (c)  $\frac{1}{99}\Omega$   
 (d)  $\frac{1}{9}\Omega$

19. Two cells with emfs  $\epsilon_1 = 1.3\text{ V}$  and  $\epsilon_2 = 1.5\text{ V}$  are connected as shown. The voltmeter reads  $1.45\text{ V}$ . If  $r_1$  and  $r_2$  be the internal resistance of the cells, then


the ratio  $\frac{r_1}{r_2}$  is

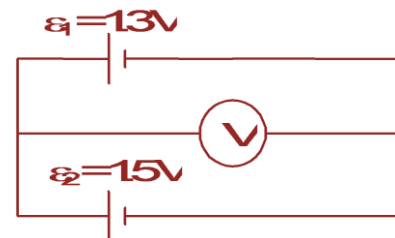- (a)  $1:1$   
 (b)  $3:1$   
 (c)  $1:2$   
 (d) none




20. An infinite ladder network consisting of  $1\Omega$  and  $2\Omega$  resistors is shown in the figure. The effective resistance of the network across  $AB$  is

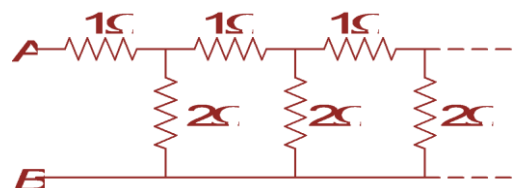- (a)  $5\Omega$   
 (b)  $3.5\Omega$   
 (c)  $2\Omega$   
 (d) none




**MORE THAN ONE CHOICE CORRECT**

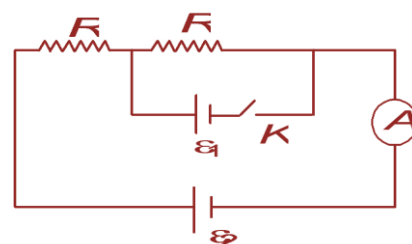
1. In the given circuit, when key  $K$  is open, reading of ammeter is  $I$ . Now key  $K$  is closed. Then the correct statement is:
- If  $\varepsilon_1 = IR$ , reading of the ammeter is  $I$ .
  - If  $IR < \varepsilon_1 < 2IR$ , reading of the ammeter is greater than  $I$ .
  - If  $\varepsilon_1 = 2IR$ , reading of the ammeter will be zero.
  - Reading of ammeter will not change.



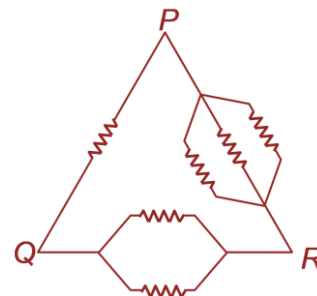2. Six equal resistances are connected between points  $P$ ,  $Q$ , and  $R$  as shown in the figure. Then the net resistance will be
- maximum between  $P$  and  $Q$
  - maximum between  $P$  and  $R$
  - minimum between  $P$  and  $Q$
  - minimum between  $P$  and  $R$



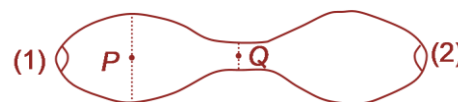3. A metallic conductor of irregular cross-section is as shown in the figure. A constant potential difference is applied across the ends (1) and (2). Then



- the current at the cross-section  $P$  equals to the current at the cross-section  $Q$ .
  - the electric field intensity at  $P$  is less than that at  $Q$ .
  - the rate of heat generated at  $Q$  is greater than that at  $P$ .
  - the number of electrons crossing per unit area of cross-section at  $P$  is less than that of  $Q$ .
4. When no current is passed through a conductor, then
- the free electrons do not move.
  - the average speed of a free electron over a large period of time is zero.
  - the average velocity of a free electron over a large period of time is zero.
  - the average of the velocities of all the free electrons at an instant is zero.
5. When the terminals of a cell of e.m.f.  $1.5\text{ V}$  are connected to an ammeter of resistance  $4\Omega$ . The ammeter reads  $0.30\text{ amp}$ . Which of the following statements is/are correct?
- The cell is non-ideal.
  - If a  $4\Omega$  resistor is also connected across terminals of the cell, the ammeter will read  $0.50\text{ amp}$
  - If a  $4\Omega$  resistor is also connected across the terminals of the cell, one-third of the electrical power generated will dissipate as heat within the cell.
  - If a voltmeter of resistance  $4\Omega$  is used after removing ammeter from circuit to measure potential difference between terminals of the cell, it will read  $1.2\text{V}$ .
6. The charge flowing in a conductor varies with time as  $q = at - bt^2$ , where  $a$  and  $b$  are positive constants. The current in the conductor
- decreases linearly with time
  - increases linearly with time
  - changes at the rate of  $-2b$
  - becomes zero after time  $= a/b$
7. Two bulbs have same specified voltage but different power ratings. When they are connected individually across a source of voltage  $V$ , both produce  $H$  amount of heat in time  $t_1$  and  $t_2$  respectively. When used together across the same source, they produce  $H$  amount of heat in time  $t$ . Then
- if they are in series,  $t = t_1 + t_2$
  - if they are in series,  $t = 2(t_1 + t_2)$
  - if they are in parallel,  $t = \frac{t_1 t_2}{t_1 + t_2}$
  - if they are in parallel,  $t = \frac{t_1 t_2}{2(t_1 + t_2)}$

8. A galvanometer has a resistance of  $100 \Omega$  and a full scale range of  $50 \mu\text{A}$ . If a resistance is added to it, it can be used as a voltmeter or as a high range ammeter. Then
- (a) If  $10 \text{ k}\Omega$  resistance is added in series, it can be used as a voltmeter of range  $50 \text{ V}$
  - (b) If  $200 \text{ k}\Omega$  resistance is added in series, it can be used as a voltmeter of range  $10 \text{ V}$
  - (c) If  $1 \Omega$  resistance is added in parallel, it can be used as a ammeter of range  $5 \text{ mA}$
  - (d) If  $1 \Omega$  resistance is added in parallel, it can be used as a ammeter of range  $10 \text{ mA}$
9. A uniform wire is shaped into a regular  $n$ -sided polygon ( $n$  is even). The resistance of total wire is  $R$ . Then
- (a) The maximum resistance of the polygon between any two corners is  $R/4$
  - (b) The maximum resistance of the polygon between any two corners is  $R/n$
  - (c) The minimum resistance of the polygon between any two corners is  $\frac{R(n-1)}{n^2}$
  - (d) The minimum resistance of the polygon between any two corners is  $R/n$
10. A wire of non-uniform cross-section is connected through a potential source. The quantities that will remain independent of area of cross section are
- (a) the charge flowing per unit time
  - (b) current density
  - (c) drift speed
  - (d) free electron density

### EXERCISE – III

#### MATCH THE FOLLOWING

**Note:** Each statement in column – I has one or more than one match in column –II.

1. Match the following

Column -I	Column -II
<b>I.</b> Electric conductivity of a conductor depends on	<b>A.</b> length of conductor.
<b>II.</b> Conductance of a conductor depends on	<b>B.</b> Temperature
<b>III.</b> For a given conductor and at a given temperature, current density depends on	<b>C.</b> Nature of conductor
<b>IV.</b> For a given potential difference applied across a conductor, current in it will depend on	<b>D.</b> Electric field strength
	<b>E.</b> Area of cross section of conductor

#### REASONING TYPE


**Directions:** Read the following questions and choose

- (A) If both the statements are true and statement-2 is the correct explanation of statement-1.
- (B) If both the statements are true but statement-2 is not the correct explanation of statement-1.
- (C) If statement-1 is True and statement-2 is False.
- (D) If statement-1 is False and statement-2 is True.

1. **Statement-1:** There is no current in the metals in the absence of electric field.  
**Statement-2:** Motion of free electrons are random.  
(a) (A)                      (b) (B)                      (c) (C)                      (d) (D)
2. **Statement-1:** In meter bridge experiment, a high resistance is always connected in series with a galvanometer.  
**Statement-2:** As resistance increases current through the circuit increases.  
(a) (A)                      (b) (B)                      (c) (C)                      (d) (D)
3. **Statement-1:** A potentiometer of longer length is used for accurate measurement.  
**Statement-2:** The potential gradient for a potentiometer of longer length with a given source of emf becomes small.  
(a) (A)                      (b) (B)                      (c) (C)                      (d) (D)
4. **Statement-1:** Potential difference across the battery is always equal to emf of the battery.  
**Statement-2:** Work done by the battery per unit charge is the emf of the battery.  
(a) A                      (b) B                      (c) C                      (d) D
5. **Statement-1:** In a simple battery circuit the point at the lowest potential is positive terminal of the battery.  
**Statement-2:** The current flows towards the point of the lower potential in the circuit, but it does not flow in a cell from positive to the negative terminal.  
(a) (A)                      (b) (B)                      (c) (C)                      (d) (D)
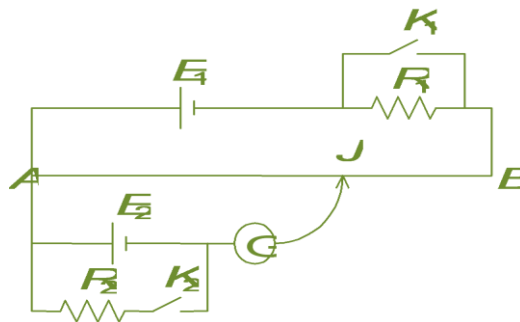
### LINKED COMPREHENSION TYPE

In the circuit shown  $AB$  is a  $10\ \Omega$  uniform slide wire  $50\ \text{cm}$  long.  $E_1$  is  $2\ \text{V}$  accumulator of negligible internal resistance.  $R_1$  and  $R_2$  are  $15\ \Omega$  and  $5\ \Omega$  respectively. When  $K_1$  and  $K_2$  are both open, the galvanometer shows no deflection when  $AJ = 31.25\ \text{cm}$ . When  $K_1$  and  $K_2$  are both closed the balance length  $AJ = 5\ \text{cm}$ .




1. The emf of the cell  $E_2$ ,  
(a)  $0.5\ \text{V}$  (b)  $1\ \text{V}$   
(c)  $1.5\ \text{V}$  (d)  $2\ \text{V}$
2. The internal resistance of the cell  $E_2$ ,  
(a)  $7.5\ \Omega$  (b)  $8\ \Omega$   
(c)  $10\ \Omega$  (d)  $2\ \Omega$
3. The balance length  $AJ$  when  $K_2$  is open and  $K_1$  is closed  
(a)  $12.5\ \text{cm}$  (b)  $13.5\ \text{cm}$   
(c)  $14.5\ \text{cm}$  (d)  $15.5\ \text{cm}$


## EXERCISE – IV

### SUBJECTIVE PROBLEMS

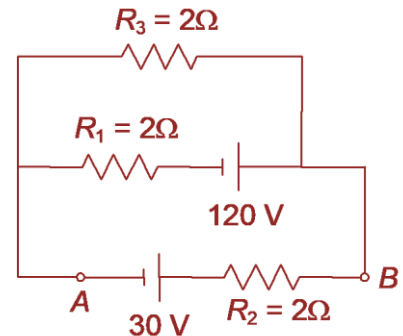1. In the circuit shown find the potential difference ( $V_B - V_A$ ) and the rate of production of heat across  $R_1$ .



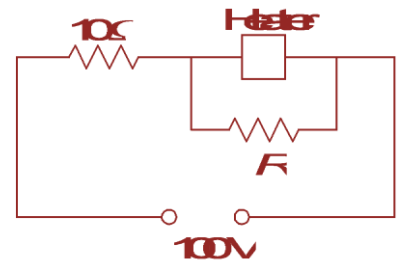2. A heater is designed to operate with a power of 1000 W in a 100 V line. It is connected in combination with a resistance of 10 ohm and a resistance  $R$  to a 100 volt mains as shown in the circuit. What should be the value of  $R$  so that the heater operates with a power of 62.5 watt?




3. A wire of resistance 0.1 ohm/cm is bent to form a square  $ABCD$  of side 10 cm. A similar wire is connected between the corners  $B$  and  $D$  to form the diagonal  $BD$ . If 2 volt battery of negligible internal resistance is connected across  $A$  and  $C$ , calculate the total power dissipated.
4. The current  $i$  through a rod of a certain metallic oxide is given by  $i = 0.2V^{1/2}$ , where  $V$  is potential difference across it. The rod is connected in series with a resistance to a 6 volt battery of negligible internal resistance. What should be series resistance in  $\Omega$  so that power dissipated in the resistance is twice that of rod. ( $\sqrt{2} = 1.4$ )

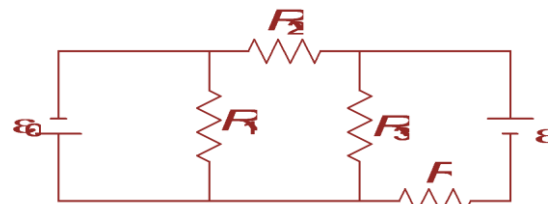
5. Find the current flowing in the resistor  $R$  in the circuit shown.

The internal resistance of the batteries are negligible.

(given  $\epsilon_0 = 20$  V,  $\epsilon = 60$  V,  $R_2 = 10 \Omega$ ,  $R_3 = 5 \Omega$  and  $R = 10 \Omega$ )




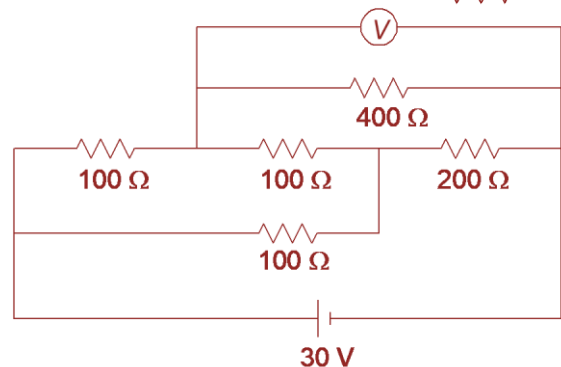6. An electrical circuit is as shown in the Figure. Calculate the potential difference across the resistor of 400 ohm, as will be measured by the voltmeter  $V$  of resistance 400 ohm, either by applying Kirchhoff's rules or otherwise.






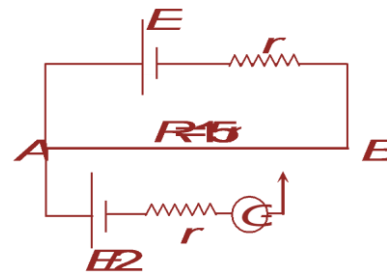
7. Consider the potentiometer circuit arranged as in figure. The potentiometer wire is 600 cm long. At what distance (in cm) from the point A should the jockey touch the wire to get zero deflection in the galvanometer?



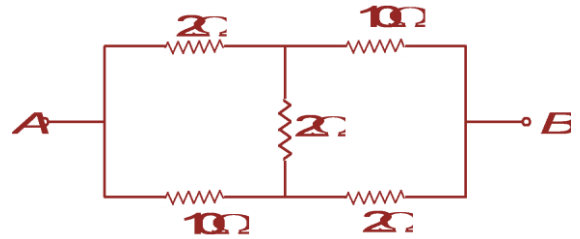
8. Find the effective resistance between the points A and B of the following network.



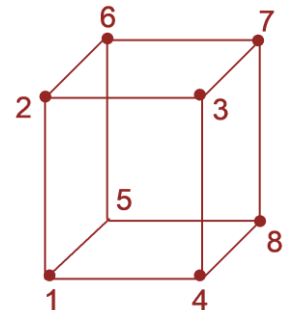9. Find the resistance of a wire frame shaped as a cube as in figure when measured between points  
(a) 1-2; (b) 1-3  
The resistance of each edge of the frame is  $12\ \Omega$



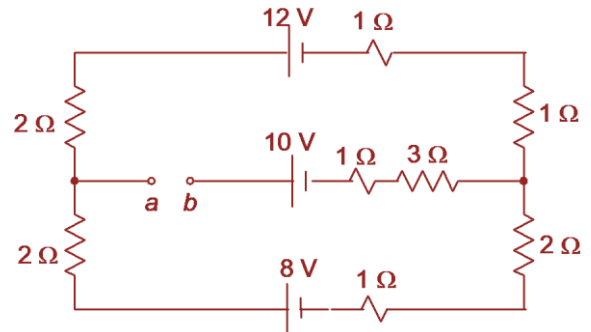10. If  $a$  and  $b$  are connected, find the current (in mA) in the 12 V cell in the given circuit.



## ANSWERS

### EXERCISE – I

#### NEET-SINGLE CHOICE CORRECT

1. (d)	2. (c)	3. (d)	4. (b)	5. (b)
6. (a)	7. (a)	8. (c)	9. (c)	10. (d)
11. (b)	12. (a)	13. (a)	14. (c)	15. (a)
16. (a)	17. (b)	18. (c)	19. (b)	20. (a)
21. (b)	22. (a)	23. (c)	24. (a)	25. (a)

### EXERCISE – II

#### IIT-JEE-SINGLE CHOICE CORRECT

1. (c)	2. (b)	3. (d)	4. (d)	5. (b)
6. (a)	7. (d)	8. (d)	9. (c)	10. (d)
11. (b)	12. (a)	13. (b)	14. (a)	15. (a)
16. (b)	17. (b)	18. (c)	19. (b)	20. (c)

#### MORE THAN ONE CHOICE CORRECT

1. (a,c)	2. (a,d)	3.(a,b,c,d)	4. (c,d)	5. (a,c,d)
6. (a,c)	7. (a,c)	8. (b,c)	9. (a,c)	10. (a,d)

### EXERCISE – III

#### MATCH THE FOLLOWING

1. I – B, C; II – A, B, C, E; III – D; IV – A, B, C, E

#### REASONING TYPE

1. (a)	2. (c)	3. (a)	4. (d)	5. (d)
--------	--------	--------	--------	--------

#### LINKED COMPREHENSION TYPE

1. (a)	2. (a)	3. (a)
--------	--------	--------

## EXERCISE – IV

### SUBJECTIVE PROBLEMS

1. 50 V, 2450 W
2. 5 ohm
3. 4 W
4. 14  $\Omega$
5. 5 A
6. 20 V
7. 320 cm
8. 4  $\Omega$
9. (i) 7 $\Omega$  (ii) 9  $\Omega$
10. 464 mA

## IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 1

- Q.1** A current of 5 Amp exist on a 10 ohm resistance for 4 min. How much charge pass through any cross-section of the resistor in this time ?  
(1) 12 coulombs (2) 120 coulombs  
(3) 1200 coulombs (4) 12000 coulombs
- Q.2** The electric current in a liquid is due to the flow of -  
(1) electron only  
(2) positive ions only  
(3) negative and positive ions both  
(4) electrons and positive ions both
- Q.3** The electric current in a discharge tube containing a gas is due to -  
(1) electron only  
(2) positive ions only  
(3) negative ion and positive ions both  
(4) electrons and positive ions both
- Q.4** A steady current is passing through a linear conductor of non-uniform cross-section. The net quantity of charge crossing any cross-section per second is -  
(1) independent of area of cross-section  
(2) directly proportional to the length of conductor  
(3) directly proportional to the area of cross-section  
(4) inversely proportional to the lengths of conductor
- Q.5** A current (I) flows through a uniform wire of diameter (d) when the mean drift velocity is v. The same current will flow through a wire of diameter d/2 made of the same material if the mean drift velocity of the electron is -  
(1) v/4 (2) v/2 (3) 4v (4) 2v
- Q.6** A wire of non-uniform cross-section is carrying a steady current. Along the wire -  
(1) current and current density are constant  
(2) only current is constant  
(3) only current density is constant  
(4) neither current nor current density is a constant
- Q.7** When a potential difference (V) is applied across a conductor , the thermal speed of electrons is -  
(1) zero (2) proportional to  $\sqrt{T}$   
(3) proportional to (T) (4) proportional to V
- Q.8** Specific resistance of a wire depends on the  
(1) length of the wire  
(2) area of cross-section of the wire  
(3) resistance of the wire  
(4) material of the wire
- Q.9** A cross-sectional area of a copper wire is  $3 \times 10^{-6} \text{ m}^2$ . The current of 4.2 amp is flowing through it. The current density in amp/m<sup>2</sup> through the wire is –  
(1)  $1.4 \times 10^3$  (2)  $1.4 \times 10^4$   
(3)  $1.4 \times 10^5$  (4)  $1.4 \times 10^6$
- Q.10** The resistance of some substances become zero at very low temperature , then these substances are called –  
(1) good conductors (2) super conductors  
(3) bad conductors (4) semi conductors

**Q.11** The resistance of wire is  $20\Omega$ . The wire is stretched to three times its length. Then the resistance will now be –  
 (1)  $6.67\Omega$  (2)  $60\Omega$   
 (3)  $120\Omega$  (4)  $180\Omega$


**Q.12** The dimensions of a mangnin block are  $1\text{ cm} \times 1\text{ cm} \times 100\text{ cm}$ . The electrical resistivity of mangnin is  $4.4 \times 10^{-7}\text{ ohm-meter}$ . The resistance between the opposite rectangular faces is –  
 (1)  $4.4 \times 10^{-7}\text{ ohm}$  (2)  $4.4 \times 10^{-3}\text{ ohm}$   
 (3)  $4.4 \times 10^{-5}\text{ ohm}$  (4)  $4.4 \times 10^{-1}\text{ ohm}$

**Q.13** If the temperatures of iron and silicon wires are increased from  $30^\circ\text{C}$  to  $50^\circ\text{C}$ , the correct statement is–  
 (1) resistance of both wires increase  
 (2) resistance of both wires decrease  
 (3) resistance of iron wire increases and the resistance of silicon wire decreases  
 (4) resistance of iron wire decreases and the resistance of silicon wire increases

**Q.14** When the resistance of copper wire is  $0.1\Omega$  and the radius is  $1\text{ mm}$ , then the length of the wire is (specific resistance of copper is  $3.14 \times 10^{-8}\text{ ohm} \times \text{m}$ ) -  
 (1)  $10\text{ cm}$  (2)  $10\text{ m}$  (3)  $100\text{ m}$  (4)  $100\text{ cm}$

**Q.15** When the resistance wire is passed through a die the cross-section area decreases by  $1\%$ , the change in resistance of the wire is -  
 (1)  $1\%$  decrease (2)  $1\%$  increase  
 (3)  $2\%$  decrease (4)  $2\%$  increase

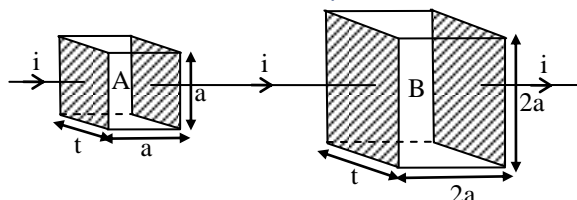**Q.16** In the following diagram two parallelopiped A and B are of the same thickness. The arm of B is double that of A. Compare these resistances and find out the value of  $R_A/R_B$  is –



(1) 1 (2) 2 (3)  $\frac{1}{2}$  (4) 4

**Q.17** When the temperature of a metallic conductor is increased its resistance -  
 (1) always decreases  
 (2) always increases  
 (3) may increase or decrease  
 (4) remains the same

**Q.18** The resistance of a semi-conductors -  
 (1) increases with increase of temperature  
 (2) decreases with increase of temperature  
 (3) does not change with change of temperature  
 (4) first decreases and then increases with increase of temperature

**Q.19** Ohm's law is valid when the temperature of the conductor is -  
 (1) constant (2) very high  
 (3) very low (4) varying


**Q.20** A certain piece of copper is to be shared into a conductor of minimum resistance . Its length and diameter should be respectively -  
 (1)  $\ell, d$  (2)  $2\ell, d$  (3)  $\ell/2, 2d$  (4)  $2\ell, d/2$

**Q.21** A wire has a resistance of  $10\Omega$ . A second wire of the same material is having length double and radius of cross-section half that of the wire. The resistance of the second wire is -  
 (1)  $20\Omega$  (2)  $40\Omega$  (3)  $80\Omega$  (4)  $10\Omega$

**Q.22** A cylindrical copper rod is reformed to twice its original length with no change in volume. The resistance between its ends before the change was  $(R)$ . Now its resistance -  
 (1)  $8R$  (2)  $6R$  (3)  $4R$  (4)  $2R$


**Q.23** The length of a conductor is halved. Its conductance will be -  
 (1) halved (2) unchanged  
 (3) doubled (4) quadrupled

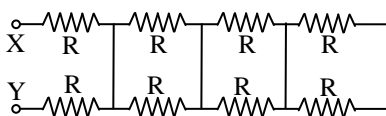**Q.24** Net resistance between X and Y is -




(1)  $R$  (2)  $2R$  (3)  $\frac{R}{2}$  (4)  $4R$

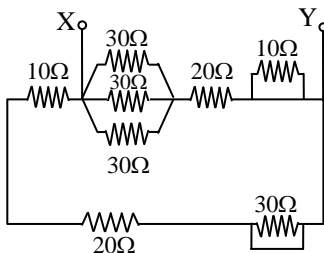**Q.25** Net resistance between X and Y is -




(1)  $5\Omega$  (2)  $10\Omega$  (3)  $15\Omega$  (4)  $60\Omega$

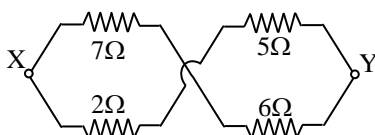**Q.26** Net resistance between X and Y is -



(1)  $4\Omega$  (2)  $4.55\Omega$  (3)  $2\Omega$  (4)  $20\Omega$

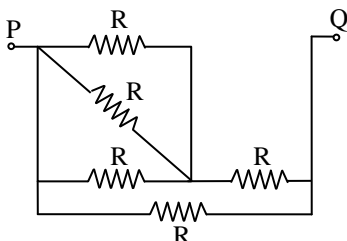**Q.27** The equivalent resistance between the terminal point P and Q is  $4\Omega$  in the given circuit, then find out the resistance of  $R$  in ohms -




(1) 7 (2) 4 (3) 2 (4) 5

**Q.28** At a point  $\Sigma i = 0$  in a circuit with one emf source, then-


- (1) the resistance of the circuit is zero
- (2) the point is the junction point
- (3) the emf of the source is infinity
- (4) this is not possible

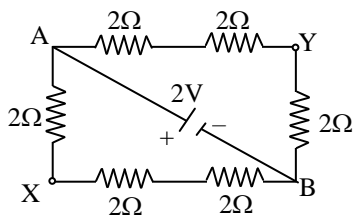**Q.29** For the following circuits, the potential difference between X and Y in volt is –



- (1)  $\frac{2}{3}$       (2)  $\frac{4}{3}$       (3)  $\frac{8}{9}$       (4)  $\frac{5}{3}$

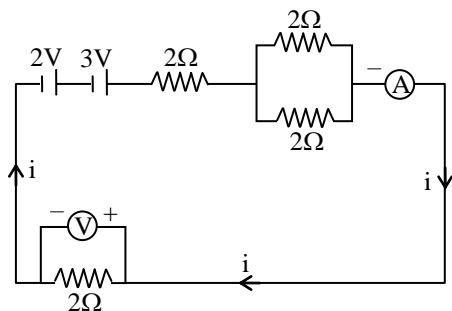**Q.30** Reading of ideal ammeter in ampere for the following circuit is –




- (1) 1      (2) 2      (3) 3      (4) 4

**Q.31** In a closed circuit the sum of total emf is equal to the sum of the –


- (1) currents  
 (2) resistances  
 (3) products of current and the resistances  
 (4) none of the above

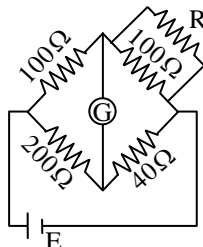**Q.32** For following diagram the galvanometer shows zero deflection, then the value of R is -



- (1)  $52 \Omega$       (2)  $50 \Omega$       (3)  $100 \Omega$       (4)  $25 \Omega$

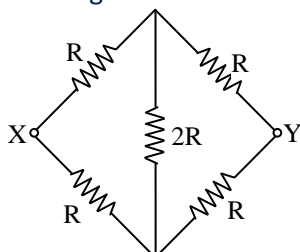**Q.33** For following circuit the value of total resistance between X and Y in ohm is -



- (1) R      (2) 4 R      (3) 5 R      (4) 6 R


**Q.34** The equivalent resistance in series combination is-

- (1) smaller than the largest resistance  
 (2) larger than the largest resistance  
 (3) smaller than the smallest resistance  
 (4) larger than the smallest resistance

- Q.35** The equivalent resistance of resistors in parallel is always -  
 (1) higher than the highest of component resistor  
 (2) less than the lowest of component resistors  
 (3) in between the lowest and the highest of component resistors  
 (4) equal to the sum of the component resistors


- Q.36** When  $n$  identical resistances of value ' $r$ ' each are connected in parallel, the equivalent resistance is  $x$ . The resultant resistance when they are connected in series is -  
 (1)  $n x$     (2)  $n^2 x$     (3)  $r n x$     (4)  $r^2 x/n$

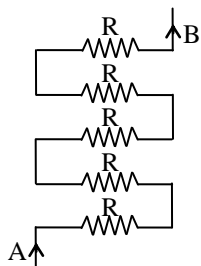- Q.37** Five identical resistance are connected as shown in fig. The equivalent resistance between point (A) and (B) is -




- (1)  $R$     (2)  $5R$     (3)  $R/5$     (4)  $2R/5$

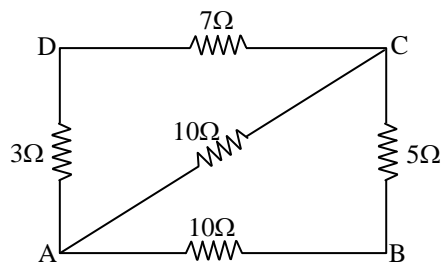- Q.38** Five resistance are connected as shown in the adjoining figure. The equivalent resistance between A and B is -



- (1)  $35\Omega$     (2)  $5\Omega$   
 (3)  $15/4\Omega$     (4)  $25\Omega$

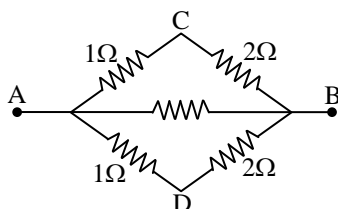- Q.39** The equivalent resistance between points (A) and (B) in the adjoining fig. is one ohm. What is the value of middle resistance -




- (1)  $9\Omega$     (2)  $1\Omega$     (3)  $6\Omega$     (4)  $3\Omega$

- Q.40** Four wires of equal length and of resistance 5 ohm each are connected in the form of a square. The equivalent resistance between the diagonally opposite corners of the square is -  
 (1) 5 ohm    (2) 10 ohm  
 (3) 20 ohm    (4)  $5/4$  ohm




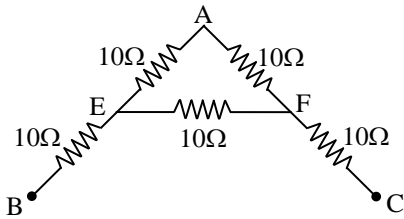**Q.41** The effective resistance (in  $\Omega$ ) between (B) and (C) of letter (A), containing resistance as shown in fig. as



- (1) 60                      (2) 40  
 (3)  $80/3$                 (4)  $160/9$

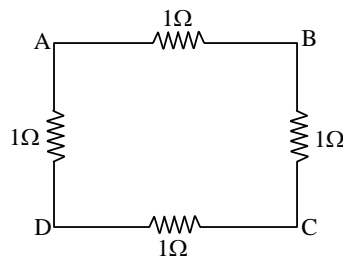**Q.42** Four identical resistances are joined as shown in fig. The equivalent resistance between points (A) and (B) is  $R_1$ . The equivalent resistance between points A and C is  $R_2$  then ratio of  $R_1/R_2$  is -



- (1) 1 : 1    (2) 4 : 3    (3) 3 : 4                      (4) 1 : 2


**Q.43** Kirchoff's first law is  $\Sigma i = 0$  at a junction deals with -

- (1) conservation of charge  
 (2) conservation of energy  
 (3) conservation of momentum  
 (4) conservation of angular momentum

**Q.44** Kirchoff's second law is based on law of conservation of -


- (1) charge  
 (2) energy  
 (3) momentum  
 (4) sum of mass and energy

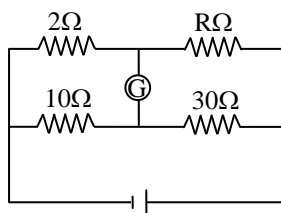**Q.45** In the adjoining fig. there is no deflection in the galvanometer . Then R is equal to -




- (1)  $2\Omega$     (2)  $30\Omega$     (3)  $6\Omega$                       (4)  $(2/3)\Omega$

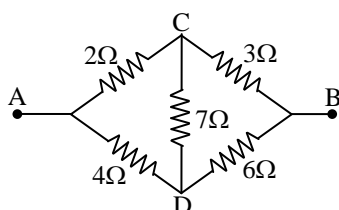**Q.46** Five resistances are connected as shown in fig. The effective resistance between the points A and B is -




- (1)  $10/3\Omega$     (2)  $20/3\Omega$     (3)  $15\Omega$                       (4)  $6\Omega$

**Q.47** Reading of ammeter is -

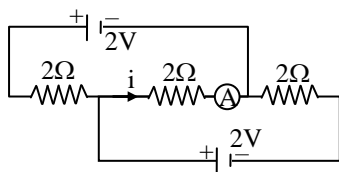


- (1) 1      (2) 2      (3)  $\frac{2}{3}$       (4) 3

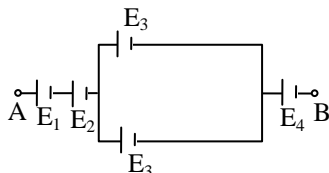**Q.48** In the following circuit the resultant emf between AB is -



- (1)  $E_1 + E_2 + E_3 + E_4$   
 (2)  $E_1 + E_2 + 2E_3 + E_4$   
 (3)  $E_1 + E_2 + (E_3/2) + E_4$   
 (4)  $E_1 + E_2 + (E_3/4) + E_4$

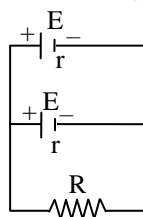**Q.49** Two cells of same emf  $E$  and internal resistance  $r$  are connected in parallel with a resistance of  $R$ . To get maximum power in the external circuit, the value of  $R$  is -



- (1)  $R = \frac{r}{2}$       (2)  $R = r$   
 (3)  $R = 2r$       (4)  $R = 4r$

**Q.50** A cell of e.m.f ( $E$ ) and internal resistance ( $r$ ) is connected in series with an external resistance ( $nr$ ) then the ratio of the terminal p.d. to E.M.F is -

- (1)  $1/n$       (2)  $1/(n+1)$   
 (3)  $n/(n+1)$       (4)  $(n+1)/n$

**Q.51** The terminal potential difference of a cell, when short circuited is -

- (1)  $E$       (2)  $E/2$   
 (3) zero      (4)  $E/3$

**Q.52** Five dry cell each of e.m.f 1.5V are connected in parallel. The e.m.f of the combination is -

- (1) 7.5 V      (2) 0.3 V  
 (3) 3V      (4) 1.5 V


**Q.53** Two bulbs , one of 50 watt and another of 25 watt are connected in series to the mains , the ratio of the current through them is -

- (1) 2 : 1  
 (2) 1 : 2  
 (3) 1 : 1  
 (4) can't be determined without the p.d. of the main supply


- Q.54** Constant voltage is applied between the two ends of a uniform metallic wire. The heat developed is doubled if -  
 (1) both the length and radius of the wire are halved  
 (2) both the length and radius of the wire are doubled  
 (3) the radius of wire is doubled  
 (4) the length of the wire is doubled
- Q.55** Two electric bulbs rated  $P_1$  watt  $V$  volt and  $P_2$  watt  $V$  volt are connected in parallel across  $V$  volt mains then the total power is -  
 (1)  $P_1 + P_2$                       (2)  $\sqrt{P_1 P_2}$   
 (3)  $\frac{P_1 P_2}{(P_1 + P_2)}$                       (4)  $\frac{(P_1 + P_2)}{P_1 P_2}$
- Q.56** Lamps used for the house lightening are connected in -  
 (1) series                      (2) parallel  
 (3) mixed grouping                      (4) arbitrary manner
- Q.57** Two electric bulbs whose resistances are in the ratio of 1 : 2 are connected in parallel to a constant voltage source. The power's dissipated in them have the ratio -  
 (1) 1 : 2    (2) 1 : 1    (3) 2 : 1    (4) 1 : 4
- Q.58** An electric bulb is rated 220 volt and 100 watt. The resistance of the filament of the electric bulb is -  
 (1)  $2.2 \Omega$                       (2)  $2.2 \times 10^4 \Omega$   
 (3)  $484 \Omega$                       (4)  $100 \Omega$
- Q.59** Three electric bulbs 40W , 60W and 100W are designed to work on a 220V mains. Which bulb will burn most brightly if they are connected in series across 220V mains -  
 (1) 100W bulb  
 (2) 60W bulb  
 (3) 40 W bulb  
 (4) all bulbs will burn equally brightly
- Q.60** If the current in a electric bulb drops by 2% then the power decreases by -  
 (1) 1%    (2) 2%    (3) 4%    (4) 16%
- Q.61** If the current in an electric bulb decreases by 0.5 percent, then the power in the bulb decreases approximately by -  
 (1) 0.5 percent                      (2) 1 percent  
 (3) 2 percent                      (4) 0.25 percent

## IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 2

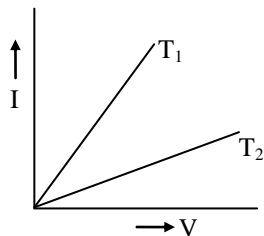- Q.1** The current (I) and voltage (V) graphs for a given metallic wire at two different temperature ( $T_1$ ) and ( $T_2$ ) are shown in fig. It is concluded that -



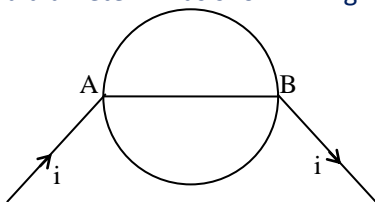
- (1)  $T_1 > T_2$                       (2)  $T_1 < T_2$   
 (3)  $T_1 = T_2$                       (4)  $T_1 = 2T_2$
- Q.2** A  $3^\circ\text{C}$  rise in temperature is observed in a conductor by passing a certain current. When the current is doubled, the rise in temp -  
 (1)  $15^\circ\text{C}$     (2)  $12^\circ\text{C}$     (3)  $9^\circ\text{C}$     (4)  $3^\circ\text{C}$
- Q.3** A wire of resistance  $0.5\Omega \text{ m}^{-1}$  is bent into a circle of radius 1m. The same wire is connected across a diameter AB as shown in fig. The equivalent resistance is -




- (1)  $\pi \Omega$                       (2)  $\frac{\pi}{\pi+2} \Omega$   
 (3)  $\frac{\pi}{\pi+4} \Omega$                       (4)  $(\pi + 1) \Omega$
- Q.4** You have three equal resistance. How many different combination can you have with these resistances -  
 (1) 2            (2) 3            (3) 4            (4) 6
- Q.5** An electron charge (e) is revolving in a circular orbit of radius (r) round a nucleus of charge (Ze) with speed (v). The equivalent current is -  
 (1) zero                      (2)  $e.v/2\pi r$   
 (3)  $Ze . v/2\pi r$                       (4)  $e . 2\pi r/v$
- Q.6** In Wheat stone's bridge  $P = 9 \text{ ohm}$  ,  $Q = 11 \text{ ohms}$ ,  $R = 4 \text{ ohm}$  and  $S = 6 \text{ ohms}$ . How much resistance must be put in parallel to the resistance (S) to balance the bridge  
 (1) 24 ohms                      (2)  $(44/9) \text{ ohm}$   
 (3) 26.4 ohms                      (4) 18.7 ohms
- Q.7** A wire of resistance  $2\Omega$  is redrawn so that its length becomes four times. The resistance of the redrawn wire is -  
 (1)  $2\Omega$     (2)  $8\Omega$     (3)  $16\Omega$     (4)  $32\Omega$
- Q.8** Two wires of equal lengths and of material (x) and (y) have same resistance. The ratio of the radii of two wires is 1 : 2. The ratio of the specific resistance of the two materials is -  
 (1) 1 : 1    (2) 1 : 2    (3) 1 : 4    (4) 4 : 1

- Q.9** A wire is cut into 4 pieces, which are put together side by side to obtain one conductor. If the original resistance of the wire was (R). The resistance of the bundle will be -  
 (1)  $R/4$  (2)  $R/8$   
 (3)  $R/16$  (4)  $R/32$

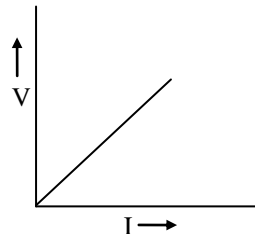- Q.10** The current -voltage variation for a wire of copper of length (L) and area (A) is shown in fig. The slope of the line will be -




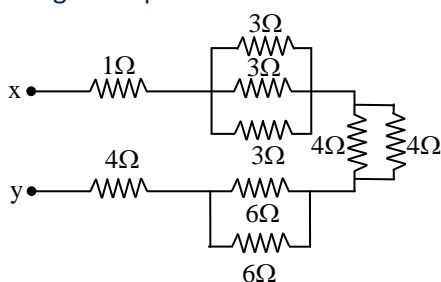- (1) less if experiment is done at a higher temperature  
 (2) more if a wire of silver of same dimensions is used  
 (3) will be doubled if the lengths of the wire is doubled  
 (4) will be halved if the length is doubled
- Q.11** The internal resistance of cell is  $0.1\Omega$  and its emf is 2V. When a current of 2A is being drawn from it, the potential difference across its terminals will be -  
 (1) more than 2V (2) 2V  
 (3) 1.8V (4) none of the above
- Q.12** A dry cell has an e.m.f of 1.5V and internal resistance  $0.5\Omega$ . If the cell sends a current of 1A through an external resistance the p.d. of the cell will be -  
 (1) 1.5V (2) 1V  
 (3) 0.5V (4) 0V
- Q.13** Twelve wires of equal resistance (R) are connected to form a cube. The effective resistance between two diagonal ends will be -  
 (1)  $5/6 R$  (2)  $6/5 R$   
 (3)  $3R$  (4)  $12 R$
- Q.14** A wire has resistance 12 ohms. It is bent in the form of a circle. The effective resistance between the two points on any diameter of the circle is -  
 (1)  $12\Omega$  (2)  $24\Omega$  (3)  $6\Omega$  (4)  $3\Omega$
- Q.15** Five cells each of e.m.f (E) and internal resistance (r) are connected in series. If due to oversight one cell is connected wrongly ,then the equivalent e.m.f and internal resistance of the combination is -  
 (1)  $5E$  and  $5r$  (2)  $3E$  and  $3r$   
 (3)  $3E$  and  $5r$  (4)  $5E$  and  $4r$
- Q.16** In fig the equivalent resistance between points (x) and (y) -




- (1)  $16\Omega$  (2)  $14\Omega$  (3)  $11\Omega$  (4)  $18\Omega$

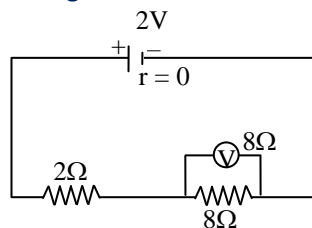**Q.17** In the circuit shown in fig, the reading of voltmeter is -




- (1) 1.33 V                      (2) 0.8 V  
 (3) 2.0 V                        (4) 1.6V

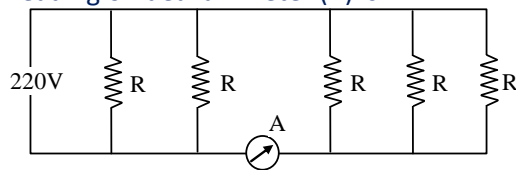**Q.18** Five identical lamps each resistance  $R = 1100\Omega$  are connected to 220V as shown in fig. The reading of ideal ammeter (A) is -




- (1)  $1/5$  A                                      (2)  $2/5$  A  
 (3)  $3/5$  A                                      (4) 1 A

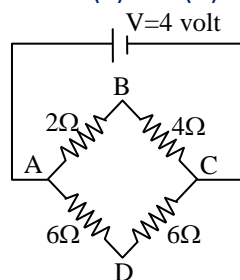**Q.19** In fig. the difference of potential between (B) and (D) is -




- (1) + 0.67V                      (2) -0.67V  
 (3) 2V                                (4) 1.33V

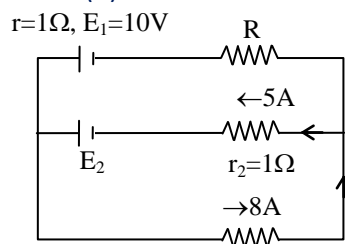**Q.20** In fig the current through resistance (R) is -




- (1) 3A                                      (2) 13A  
 (3) 6.5 A                                (4) 9A

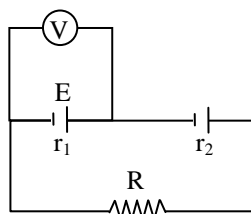**Q.21** In the adjoining figure, the reading of an ideal voltmeter (V) is zero. Then the relation between  $R$ ,  $r_1$ , and  $r_2$  is -




- (1)  $R = r_2 - r_1$                       (2)  $R = r_1 - r_2$   
 (3)  $R = r_1 + r_2$                       (4)  $R = \frac{r_1 \cdot r_2}{r_1 + r_2}$

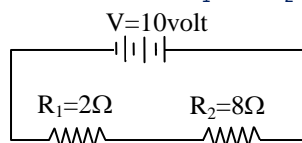**Q.22** In fig the ratio of power dissipated in resistors  $R_1$  and  $R_2$  is -




- (1) 1 : 4                      (2) 4 : 1  
 (3) 1 : 2                      (4) 2 : 1

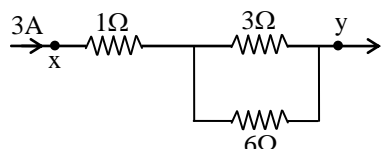**Q.23** In fig the ratio of current in  $3\Omega$  and  $1\Omega$  resistance is -




- (1) 1                              (2) 1/3  
 (3) 2/3                          (4) 3

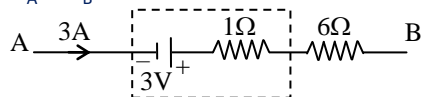**Q.24** Fig represents a part of a closed circuit. The potential difference between (A) and (B) i.e.  $V_A - V_B$  is -




- (1) 24 V                          (2) 0V  
 (3) 6V                            (4) 18 V

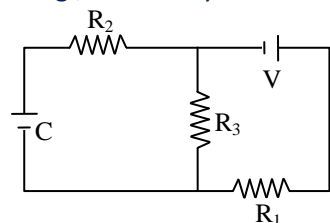**Q.25** In fig., the steady state voltage drop across capacitor (C) is -




- (1) V                              (2)  $\frac{VR_1}{R_3 \left( \frac{R_1 R_3}{R_1 + R_3} \right)}$   
 (3)  $\frac{VR_3}{R_1 + R_3}$                       (4)  $\frac{VR_1}{R_1 + R_3}$

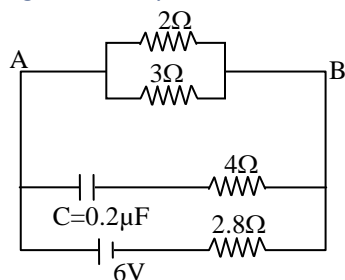**Q.26** In fig the steady state current in  $2\Omega$  resistance is-



- (1) 1.5 A                          (2) 0.9 A  
 (3) 0.6 A                          (4) zero

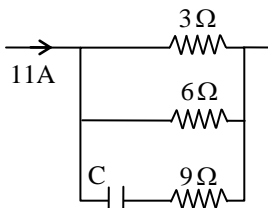**Q.27** In fig the current in  $3\Omega$  and  $6\Omega$  resistance are respectively-



- (1) 7.33 A , 3.067A    (2) 3.67A , 7.33 A  
 (3) 6A , 3A            (4) 3A , 6A

**Q.28** A battery of 20 cells (each having e.m.f 1.8V and internal resistance 0.1ohm ) is charged by 220 volts and the charging current is 15A. The resistance to be put in the circuit is -

- (1) 10.27 ohm            (2) 12.27 ohm  
 (3) 8.62 ohms            (4) 16.24 ohms

**Q.29** A battery is connected in series with an external resistance. The current in circuit is 1amp. and 0.7 amp When external resistance equals  $5\Omega$  and  $8\Omega$  respectively the internal resistance of the battery is -

- (1)  $0.2\Omega$                 (2)  $0.5\Omega$   
 (3)  $2\Omega$                  (4)  $0.6\Omega$

**Q.30** In the above question the maximum current is -

- (1) 8 amp                 (2) 4 amp  
 (3) 3.5 amp.             (4) 1 amp

**Q.31** A house is served by a 220V supply line . In a circuit protected by a fuse marked 9A. The maximum number of 60W lamps in parallel that can be turned on is -

- (1) 44            (2) 20            (3) 22            (4) 33


**Q.32** The two head lamps of a car are in parallel and they together consume 48 watts with the help of a 6V battery. The resistance of each bulb is -

- (1) 0.67 ohm            (2) 3.0 ohms  
 (3) 4.0 ohms            (4) 1.5 ohms

**Q.33** A 25 watt , 220 volt bulb and a 100 watt, 220 volt bulb are connected in series across a 440 volt line -

- (1) only 100 watt bulb will fuse  
 (2) only 25 watt bulb will fuse  
 (3) both bulbs will fuse  
 (4) none of the bulb will fuse

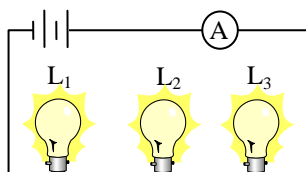
**Q.34** In the circuit below, ammeter (A) reads 0.5A. Bulbs  $L_1$  and  $L_2$  are brightly lit, but  $L_3$  is not lit. What is the reason for  $L_3$  not being lit ?



- (1) the ammeter is faulty  
 (2) the filament of  $L_3$  is broken  
 (3) the resistance of  $L_3$  is much lower than that of  $L_1$  and  $L_2$   
 (4) there is a break in the connecting wire between  $L_2$  and  $L_3$



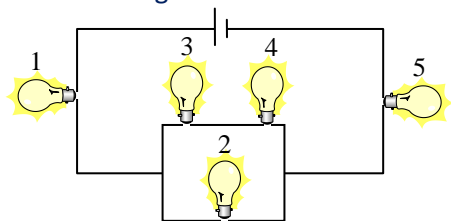**Q.35** All bulbs in figure below are identical which, bulbs light most brightly -



- (1) 1 only                      (2) 2 only  
 (3) 3 and 4 only              (4) 1 and 5

**Q.36** A cell of e.m.f (E) volt and internal resistance (r) ohms is connected to an external resistance of (r) ohms. The potential difference across the terminals of the cell will be

- (1) E volt                      (2) E/2 Volt  
 (3) E/4 volt                      (4) 2E volt

**Q.37** When a cell is connected to 1 ohm resistance, 1 ampere current flows through the circuit. When 3 ohm resistance issued then 0.5 amp current flows, then internal resistance of the cell is -

- (1) 1Ω      (2) 1.5 Ω (3) 2 Ω                      (4) 2.5 Ω

**Q.38** An electric kettle has two coils. When one of these is switched on, the water in the kettle boils in 6 minutes. When the other coil is switched on, the water boils in 3 minutes. If the two coils are connected in series, the time taken to boil the water in the kettle is-

- (1) 2 min.                      (2) 3 min.  
 (3) 6 min.                      (4) 9 min.

**Q.39** In question 39, if the two coils are connected in parallel, then the total time taken to boil the water in kettle is -

- (1) 2 minutes                      (2) 3 minutes  
 (3) 6 minutes                      (4) 9 minutes.


**Q.40** A resistance coil of 60 Ω is immersed in 42 kg of water. A current of 7 A is passed through it. The rise in temperature of water per minutes is -

- (1) 4°C                      (2) 8°C  
 (3) 1°C                      (4) 12°C

**Q.41** A coil of wire of resistance 50Ω is embedded in a block of ice and a potential difference of 210 V is applied across it. the amount of ice which melts in 1 second is -

- (1) 0.262 g                      (2) 2.62 g  
 (3) 26.2 g                      (4) 0.0262 g

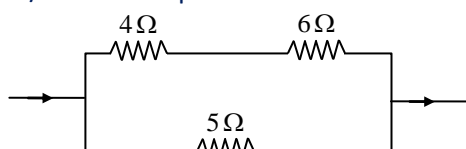**Q.42** In the circuit shown in fig. the heat produced in 5 Ω resistor due to a current flowing in it is 10 cal/s. The heat produced in 4 Ω resistor is -




- (1) 4 cal/s                      (2) 1 cal/s  
 (3) 2 cal/s                      (4) 3 cal/s


**Q.43** 'N' equal resistors connected in series across a source of e.m.f together dissipate 4 watts of power. The power dissipated when the same resistors are connected in parallel across the same source of e.m.f is 64 watts. The number of resistors 'N' is equal to -

- (1) 8                      (2) 4  
 (3) 16                      (4) 2

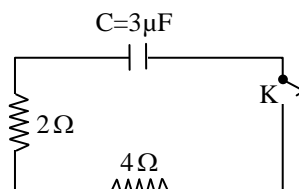- Q.44** The same mass of copper is drawn into two wires 1 mm thick and 2 mm thick. If the two wires are connected in series and the current is passed, the heat produced in the wires will be in the ratio -  
 (1) 2 : 1                      (2) 4 : 1  
 (3) 1 : 16                     (4) 16 : 1
- Q.45** Forty electric bulbs are connected in series across a 220 V supply. After one bulb is fused the remaining 39 are connected again in series across the same supply. The percentage with which the illumination of the bulbs will change will be -  
 (1) 10.25%                    (2) 7%  
 (3) 5%                         (4) 2.5%
- Q.46** A cell of e.m.f.  $E$  and internal resistance  $r$  supplies currents for the same time  $t$  through external resistance  $R_1 = 100 \Omega$  and  $R_2 = 40 \Omega$  separately. If the heat developed in both the cases is the same, then the internal resistance of the cell is given by -  
 (1)  $28.6 \Omega$                     (2)  $70 \Omega$   
 (3)  $63.3 \Omega$                     (4)  $140 \Omega$
- Q.47** Two bulbs of 500 watt and 200 watt are manufactured to operate on 220 volt line. The ratio of heat produced in 500 watt and 200 watt, in two cases, when first they are joined in series and secondly in parallel, will be -  
 (1)  $\frac{5}{2}, \frac{2}{5}$                     (2)  $\frac{5}{2}, \frac{5}{2}$   
 (3)  $\frac{2}{5}, \frac{5}{2}$                     (4)  $\frac{2}{5}, \frac{2}{5}$
- Q.48** A capacitor of capacitance  $3\mu\text{F}$  is first charged by connecting across a 10 V battery, then it is allowed to get discharged through  $2\Omega$  and  $4\Omega$  resistor by closing the key K fig. The total energy dissipated in  $2\Omega$  resistor is equal to -




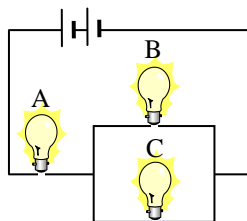- (1) 0.15 mJ                    (2) 0.5 mJ  
 (3) 0.05 mJ                    (4) 1.0 mJ
- Q.49** The bulbs A, B and C are connected as shown in fig. The bulbs B and C are identical. If the bulb C is fused -



- (1) both A and B will glow more brightly  
 (2) both A and B will glow less brightly  
 (3) A will glow less brightly and B will glow more brightly  
 (4) A will glow more brightly and B will glow less brightly.
- Q.50** How much electrical energy in kilo-watt hour is consumed in operating ten 50 watt bulbs for 10 hours per day in a month of 30 days ?  
 (1) 1500                    (2) 15000                    (3) 15                    (4) 150

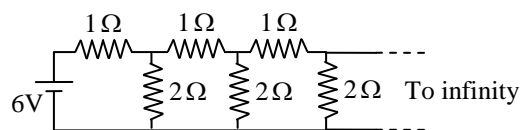- Q.51** A charge of  $2 \times 10^{-2}$  C moves at 30 revolution per second in a circle of diameter 0.80 m. The current linked with the circuit will be -  
 (1) 0.1 A (2) 0.2 A  
 (3) 0.4 A (4) 0.6 A
- Q.52** The current in a copper wire is increased by increasing the potential difference between its end. Which one of the following statements regarding  $n$ , the number of charge carriers per unit volume in the wire and  $v$  the drift velocity of the charge carriers is correct -  
 (1)  $n$  is unaltered but  $v$  is decreased  
 (2)  $n$  is unaltered but  $v$  is increased  
 (3)  $n$  is increased but  $v$  is decreased  
 (4)  $n$  is increased but  $v$  is unaltered
- Q.53** A wire of resistance  $32 \Omega$  is melted and drawn into a wire of half of its original length. The resistance of new wire and percentage decrease in resistance -  
 (1)  $8\Omega$ , 75% (2)  $8\Omega$ , 50%  
 (3)  $16\Omega$ , 75% (4)  $16\Omega$ , 50%
- Q.54** Consider two conducting wires of same length and material, one wire is solid with radius  $r$ . The other is a hollow tube of outer radius  $2r$  while inner  $r$ . The ratio of resistance of the two wires will be -  
 (1) 1 : 1 (2) 1 : 2 (3) 1 : 3 (4) 1 : 4
- Q.55** A carbon and an aluminium wire connected in series. If the combination has resistance of 30 ohm at  $0^\circ\text{C}$ , what is the resistance of carbon and aluminium wire at  $0^\circ\text{C}$  so that the resistance of the combination does not change with temperature - [ $\alpha_c = -0.5 \times 10^{-3} (\text{C}^\circ)^{-1}$  and  $\alpha_{Al} = 4 \times 10^{-3} (\text{C}^\circ)^{-1}$ ]  
 (1)  $\frac{10}{3}\Omega$ ,  $\frac{80}{3}\Omega$  (2)  $\frac{80}{3}\Omega$ ,  $\frac{10}{3}\Omega$   
 (3)  $10 \Omega$ ,  $80 \Omega$  (4)  $80 \Omega$ ,  $10 \Omega$
- Q.56** A resistance  $R_2$  is connected in parallel with a resistance  $R_1$  what resistance  $R_3$  must be connected in series with the combination of  $R_1$  and  $R_2$  so that the equivalent resistance is equal to the resistance  $R_1$  -  
 (1)  $\frac{R_1^2}{R_1 + R_2}$  (2)  $\frac{(R_1 + R_2)^2}{R_1}$   
 (3)  $\frac{R_2^2}{R_1 + R_2}$  (4)  $\frac{R_1^2}{R_2}$
- Q.57** An infinite ladder network of resistance is constructed with  $1\Omega$  and  $2\Omega$  resistance. The 6V battery between A and B has negligible internal resistance. The current that passes through  $2\Omega$  resistance nearest to the battery is -




- (1) 1A (2) 1.5 A  
 (3) 2 A (4) 2.5 A

**Q.58** A potential difference of 200 V is applied to a coil at a temperature of 15°C and the current is 10A. What will be the mean temperature of the coil when the current has fallen to 5A, the applied voltage being the same as before -

(Given  $\alpha = \frac{1}{234} \text{ C}^{-1}$  at 0°C)


- (1) 254°                      (2) 256°  
 (3) 258°                      (4) 264°

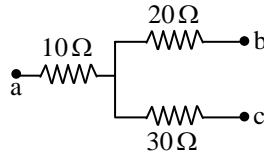**Q.59** In a given electric circuit the potentials at the points a, b and c are 30 V, 12 V and 2 V respectively. The current through resistors 10 Ω, 20 Ω and 30 Ω are -




- (1) 1, 0.4, 0.6              (2) 2, 0.8, 1.2  
 (3) 0.6 A, 0.4 A, 1A      (4) None of these

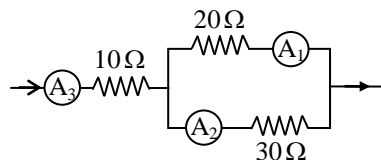**Q.60** If the reading of ammeter  $A_1$ , in figure is 2.4 A, what will the ammeter  $A_2$  and  $A_3$  read ? (Neglecting the resistances of ammeters) -




- (1) 1.6 A, 2.3 A              (2) 1.6 A, 4.0 A  
 (3) 4.0 A, 1.6 A              (4) 2.3 A, 1.6 A

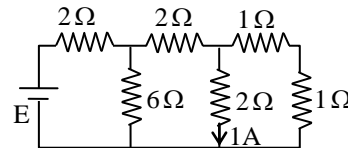**Q.61** The emf of the battery shown in the figure is given by -




- (1) 6 V      (2) 12 V      (3) 18 V      (4) 8 V

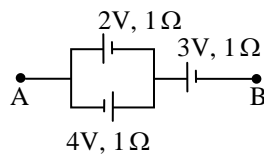**Q.62** The potential difference between points A and B is -



- (1) 2 V      (2) 6 V      (3) 4 V      (4) 3 V

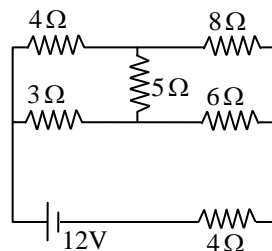
**Q.63** In the given figure the ratio of current in 8Ω and 3Ω will be -



- (1)  $\frac{8}{3}$       (2)  $\frac{3}{8}$       (3)  $\frac{4}{3}$       (4)  $\frac{3}{4}$


- Q.64** Through an electrolyte, an electric current is due to drift of -  
 (1) Free electrons  
 (2) Free electrons and holes  
 (3) Positive and negative ions  
 (4) Protons
- Q.65** A current flows in a wire of circular cross-section with the free electrons travelling with a mean drift velocity  $\bar{v}$ . If an equal current flows in a wire of twice the radius, new mean drift velocity is -  
 (1)  $\bar{v}$  (2)  $\bar{v}/2$   
 (3)  $\bar{v}/4$  (4) None of these
- Q.66** If a copper wire is stretched to make its radius decrease by 0.1%, then the percentage increase in resistance is approximately -  
 (1) 0.1% (2) 0.2%  
 (3) 0.4% (4) 0.8%
- Q.67** There is a current of 1.344 amp in a copper wire whose area of cross-section normal to the length of the wire is  $1\text{mm}^2$ . If the number of free electrons per  $\text{cm}^3$  is  $8.4 \times 10^{22}$ , then the drift velocity would be -  
 (1) 1.0 mm per sec (2) 1.0 metre per sec  
 (3) 0.1 mm per sec (4) 0.01 mm per sec

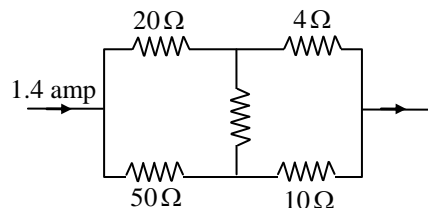- Q.68** In the following figure the current through 4 ohm resistor is -



- (1) 1.4 amp (2) 0.4 amp  
 (3) 1.0 amp (4) 0.7 amp

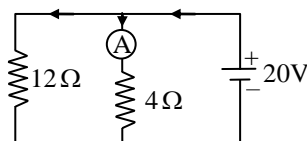
- Q.69** In the following figure, the reading of the ammeter A when the internal resistance of the battery is zero, is -



- (1)  $\frac{20}{3}$  amp (2)  $\frac{20}{12}$  amp  
 (3)  $\frac{20}{4}$  amp (4)  $\left(\frac{20}{3} + \frac{20}{12}\right)$  amp


- Q.70** The number of dry cells, each of e.m.f. 1.5 volt and internal resistance  $0.5 \Omega$  that must be joined in series with a resistance of 20 ohm so as to send a current of 0.6 ampere through the circuit is -  
 (1) 2 (2) 8 (3) 10 (4) 12
- Q.71** Two batteries of different e.m.f. and internal resistance are connected in series with each other and with an external load resistor. The current is 3.0 amp. When the polarity of one battery is reversed, the current becomes 1.0 amp. The ratio of the e.m.f. of the two batteries is -  
 (1) 2.5 (2) 2.0 (3) 1.5 (4) 1.0

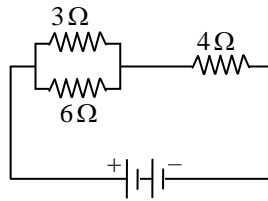- Q.72** In the following figure, current through  $3\Omega$  resistor is 0.8 amp; then the potential drop through  $4\Omega$  resistor is -



- (1) 9.6 V                      (2) 2.6 V  
 (3) 4.8 V                      (4) 1.2 V
- Q.73** A cell supplies a current  $I_1$  through a resistor of resistance  $R_1$  and a current  $I_2$  through a resistor of resistance  $R_2$ , then internal resistance of the cell is -
- (1)  $R_1 - R_2$                       (2)  $R_1 + R_2$   
 (3)  $\frac{I_1 R_2 + I_2 R_1}{I_1 + I_2}$                       (4)  $\frac{I_2 R_2 - I_1 R_1}{I_1 - I_2}$
- Q.74** The sides of a rectangular block are 2cm, 3cm and 4 cm. The ratio of maximum to minimum resistance between its parallel faces is -
- (1) 4              (2) 3              (3) 2              (4) 1
- Q.75** The current in a conductor varies with time  $t$  is  $I = 2t + 3t^2$  where  $I$  is in ampere and  $t$  in seconds. Electric charge flowing through a section of conductor during  $t = 2$  sec to  $t = 3$  sec. is -
- (1) 10 C              (2) 24 C              (3) 33 C              (4) 44 C
- Q.76** Two wires of resistance  $R_1$  and  $R_2$  have temperature coefficient of resistance  $\alpha_1$  and  $\alpha_2$ , respectively. These are joined in series. The effective temperature coefficient of resistance is -
- (1)  $\frac{\alpha_1 + \alpha_2}{2}$                       (2)  $\sqrt{\alpha_1 \alpha_2}$   
 (3)  $\frac{\alpha_1 R_1 + \alpha_2 R_2}{R_1 + R_2}$                       (4)  $\frac{\sqrt{R_1 R_2 \alpha_1 \alpha_2}}{\sqrt{R_1^2 + R_2^2}}$
- Q.77** A long resistance wire is divided into  $2n$  parts. Then  $n$  parts are connected in series and the other  $n$  parts in parallel separately. Both combinations are connected to identical supplies. Then the ratio of heat produced in series to parallel combinations will be -
- (1) 1 : 1                      (2) 1 :  $n^2$   
 (3) 1 :  $n^4$                       (4)  $n^2$  : 1
- Q.78** Two bulbs 100 W, 250 V and 200 W, 250 V are connected in parallel across a 500 V line. Then-
- (1) 100 W bulb will fused  
 (2) 200 W bulb will fused  
 (3) Both bulbs will be fused  
 (4) No bulb will fused
- Q.79** A bulb rated 220 V, 100 W is connected across 160 V line. The power dissipated will be -
- (1) 100 W              (2) 75 W              (3) 52 W              (4) 26 W
- Q.80** A uniform wire connected across a supply produces heat  $H$  per second. If the wire is cut into  $n$  equal parts and all the parts are connected in parallel across the same supply, the heat produced per second will be -
- (1)  $\frac{H}{n}$               (2)  $nH$               (3)  $n^2H$               (4)  $\frac{H}{n^2}$

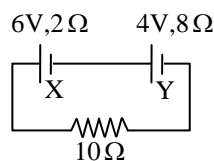- Q.81** Two electric bulbs 40 W, 200 V and 100 W, 200 V are connected in series. Then the maximum voltage that can be applied across the combination, without fusing either bulb is -  
 (1) 280V (2) 400V (3) 3000V (4) 200V
- Q.82** The resistance of  $3\Omega$  and  $6\Omega$  are joined in series and connected across a battery of emf 10 V and internal resistance  $1\Omega$ . The power dissipated by battery is -  
 (1) 3 W (2) 8 W (3) 9 W (4) 10 W
- Q.83** A 24 V battery of internal resistance  $4\Omega$  is connected to a variable resistor. The rate of heat production in the resistor is maximum when the current in the circuit is -  
 (1) 2 A (2) 3 A (3) 4 A (4) 6 A
- Q.84** In the Bohr's model of hydrogen atom, the electron moves around the nucleus in a circular orbit of radius  $5 \times 10^{-11}$  m. Its time period is  $1.5 \times 10^{-16}$  s. The current associated with the electron motion is -  
 (1) zero (2)  $1.6 \times 10^{-19}$  A  
 (3) 0.17 A (4)  $1.07 \times 10^{-3}$  A
- Q.85** Three copper wire of lengths and cross-sectional areas are  $(\ell, A)$  ;  $\left(2\ell, \frac{A}{2}\right)$  and  $\left(\frac{\ell}{2}, 2A\right)$ . Resistance is minimum is-  
 (1) wire of cross-sectional area  $\frac{A}{2}$   
 (2) wire of cross-sectional area A  
 (3) wire of cross-sectional area 2A  
 (4) same is all the three cases
- Q.86** When a piece of aluminium wire of finite length is drawn through a series of dies to reduce its diameter to half its original value, its resistance will become-  
 (1) two times (2) four times  
 (3) eight times (4) sixteen times
- Q.87** Assume that each atom of copper contributes one free electron. The density of copper is  $9\text{gcm}^{-3}$  and atomic weight of copper is 63. If the current flowing through a copper wire of 1mm diameter is 1.1 ampere, the drift velocity of electrons will be-  
 (1) 0.01 mm/s (2) 0.02 mm/s  
 (3) 0.2 mm/s (4) 0.1 mm/s
- Q.88** A metal wire of resistance R is cut into three equal pieces that are then connected side by side to form a new wire, the length of which is equal to one third of the original length. The resistance of this new wire is-  
 (1) R (2) 3R (3)  $\frac{R}{9}$  (4)  $\frac{R}{3}$
- Q.89** Two cells X and Y are connected to a resistance of  $10\Omega$  as shown in the figure. The terminal voltage of cell Y is-




- (1) zero (2) 2V (3) 4V (4) 10V

- Q.90** Masses of three wires of same metal are in the ratio 1 : 2 : 3 and their lengths in the ratio 3 : 2 : 1. Electrical resistance of these wires will be in the ratio of -  
 (1) 1 : 1 : 1                      (2) 1 : 2 : 3  
 (3) 9 : 4 : 1                      (4) 27 : 6 : 1


- Q.91** As the temperature of a metallic resistor is increased, the product of resistivity and conductivity-  
 (1) increases  
 (2) decreases  
 (3) may increase or decrease  
 (4) remains constant

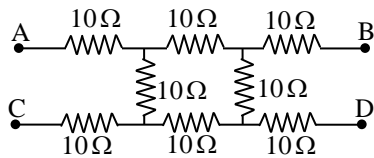- Q.92** What will be the equivalent resistance between the A and D ?



- (1) 10 Ω    (2) 20 Ω    (3) 30 Ω    (4) 40 Ω

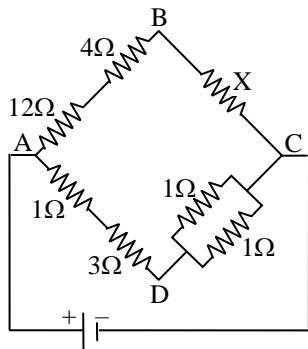- Q.93** In the arrangement of resistances shown in the circuit, the potential difference between points B and D will be zero, when the unknown resistance X is –




- (1) 4Ω    (2) 3Ω    (3) 2Ω    (4) 1Ω

- Q.94** It is observed in a potentiometer experiment that no current passes through the galvanometer, when the terminals of the cell are connected across a certain length of the potentiometer wire. On shunting the cell by a 2Ω resistance, the balancing length is reduced to half. The internal resistance of the cell is-

- (1) 4Ω    (2) 2Ω    (3) 9Ω    (4) 18Ω

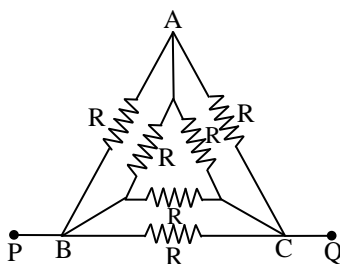- Q.95** The resistance across P and Q in the given figure is-




- (1)  $\frac{R}{3}$                       (2)  $\frac{R}{2}$   
 (3) 2R                      (4) 6R



- Q.96** When no current, is passed through conductor-
- (1) the free electrons do not move
  - (2) the average speed of a free electron over a large period of time is zero
  - (3) the average velocity of a free electron over a large period of time is zero
  - (4) the average of square of velocities of all the free electrons at an instant is zero

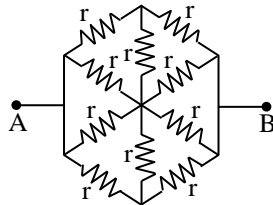- Q.97** The resistance of the circuit between A and B is-




- (1)  $r$       (2)  $0.5 r$       (3)  $2r$       (4)  $3r$
- Q.98** The number of free electrons per 10 mm of an ordinary copper wire is about  $2 \times 10^{21}$ . The average drift speed of the electrons is 0.25 mm/sec. The current flowing is-
- (1) 0.8 A                      (2) 8 A
  - (3) 80 A                        (4) 5 A
- Q.99** The potential difference between the terminals of a cells is found to be 3 volts when it is connected to a resistance equal to its internal resistance. The e.m.f. of the cell is-
- (1) 3V                            (2) 6V
  - (3) 1.5V                        (4) 4.5V

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 3**


**Q.1** Resistance of a galvanometer coil is  $8\Omega$  and  $2\Omega$  shunt resistance is connected with it. If main current is 1A then the current flow through  $2\Omega$  resistance will be-  
 (1) 0.2 A (2) 0.8 A (3) 0.1 A (4) 0.4 A

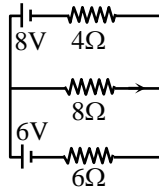**Q.2** The current in  $8\Omega$  resistance is- (as per given circuit)



- (1) 0.69 A (2) 0.92 A  
 (3) 1.30 A (4) 1.6 A

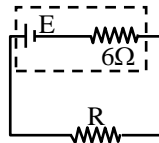**Q.3** The value of R for which power in it is maximum -



- (1)  $3\Omega$  (2)  $6\Omega$  (3)  $12\Omega$  (4)  $9\Omega$

**Q.4** The current conduction in a discharge tube is due to-

- (1) electrons only  
 (2) + ve ions and - ve ions  
 (3) (- ve) ions and electrons  
 (4) (+ ve) ions and electrons

**Q.5** A car battery of e.m.f. 12V and internal resistance  $5 \times 10^{-2}\Omega$ , receives a current of 60 A from an external source, then terminal potential difference of battery is -  
 (1) 32 V (2) 10 V (3) 15 V (4) 50 V

**Q.6** If specific resistance of a potentiometer wire is  $10^{-7}\Omega\text{m}$  and current flow through it is 0.1 amp., cross-sectional area of wire is  $10^{-6}\text{m}^2$  then potential gradient will be -  
 (1)  $10^{-2}$  volt/m (2)  $10^{-4}$  volt/m  
 (3)  $10^{-6}$  volt/m (4)  $10^{-8}$  volt/m

**Q.7** The resistance of each arm of the wheat stone bridge is  $10\Omega$ . A resistance of  $10\Omega$  is connected in series with galvanometer then the equivalent resistance across the battery will be -  
 (1)  $10\Omega$  (2)  $15\Omega$   
 (3)  $20\Omega$  (4)  $40\Omega$

**Q.8** Copper and silicon are cooled from 300 K to 60K, the specific resistance -  
 (1) decrease in copper but increase in silicon  
 (2) increase in copper but decrease in silicon  
 (3) increase in both  
 (4) decrease in both

**Q.9** Specific resistance of a conductor increases with-  
 (1) increase in temperature  
 (2) increase in cross-section area  
 (3) increase in cross-section and decrease in length.  
 (4) decrease in cross-section area.

**Q.10** For a cell terminal potential difference is 2.2 V when circuit is open and reduces to 1.8 V when cell is connected to a resistance of  $R = 5\Omega$  then determine internal resistance of cell is -

- (1)  $\frac{10}{9}\Omega$                       (2)  $\frac{9}{10}\Omega$   
 (3)  $\frac{11}{9}\Omega$                       (4)  $\frac{5}{9}\Omega$

**Q.11** To convert a galvanometer into a voltmeter one should connect a -

- (1) high resistance in series with galvanometer.  
 (2) low resistance in series with galvanometer.  
 (3) high resistance in parallel with galvanometer.  
 (4) low resistance in parallel with galvanometer

**Q.12** The electric resistance of a certain wire of iron is R. If its length and radius both are doubled, then-

- (1) the resistance will be halved and the specific resistance will remain unchanged  
 (2) the resistance will be halved and the specific resistance will be doubled  
 (3) the resistance and the specific resistance, will both remain unchanged  
 (4) the resistance will be doubled and the specific resistance will be halved

**Q.13** A galvanometer acting as a voltmeter will have-

- (1) a high resistance in series with its coil  
 (2) a low resistance in parallel with its coil  
 (3) a low resistance in series with its coil  
 (4) a high resistance in parallel with its coil


**Q.14** A bullet of mass 2 g. is having a charge of  $2\mu\text{C}$ . Through what potential difference must it be accelerated, starting from rest, to acquire a speed of 10 m/s ?

- (1) 50 kV    (2) 5 V    (3) 50 V                      (4) 5 kV

**Q.15** A battery is charged at a potential of 15V for 8 hours when the current flowing is 10A. The battery on discharge supplies a current of 5 A for 15 hours. The mean terminal voltage during discharge is 14 V. The "Watt hour" efficiency of the battery is -

- (1) 80%    (2) 90%    (3) 87.5%    (4) 82.5%

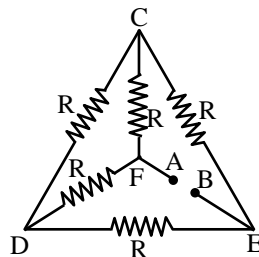**Q.16** Five equal resistances each of resistance R are connected as shown in the figure. A battery of V volts is connected between A and B. The current flowing in AFCEB will be -




- (1)  $V/R$     (2)  $V/2R$     (3)  $2V/R$     (4)  $3V/R$

**Q.17** A galvanometer of 50 ohm resistance has 25 divisions. A current of  $4 \times 10^{-4}$  ampere gives a deflection of one division. To convert this galvanometer into a voltmeter having a range of 25 volts, it should be connected with a resistance of -

- (1)  $245\Omega$  in parallel    (2)  $2550\Omega$  in series  
 (3)  $2450\Omega$  in series    (4)  $2500\Omega$  in parallel


- Q.18** A 6 volt battery is connected to the terminals of a three metre long wire of uniform thickness and resistance of 100 ohm. The difference of potential between two points on the wire separated by a distance of 50 cm will be -
- (1) 3 volt                      (2) 1 volt  
 (3) 1.5 volt                    (4) 2 volt

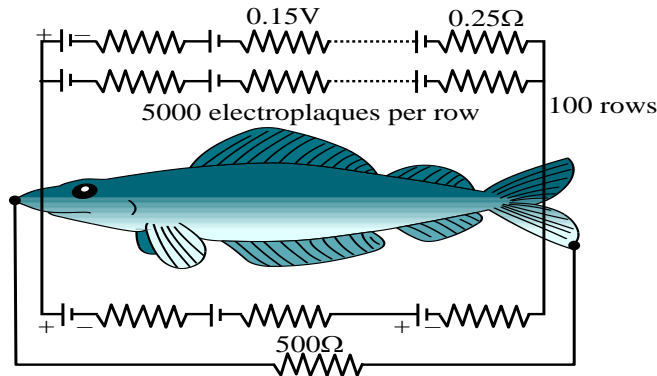- Q.19** Eels are able to generate current with biological cells called electroplaques. The electroplaques in an Eel are arranged in 100 rows, each row stretching horizontally along the body of the fish containing 5000 electroplaques. The arrangement is suggestively shown below. Each electroplaques has an emf of 0.15 V and internal resistance of  $0.25\Omega$ . The water surrounding the Eel completes a circuit between the head and its tail. If the water surrounding it has a resistance of  $500\Omega$ , the current an Eel can produce in water is about -



- (1) 1.5 A                      (2) 3.0 A  
 (3) 15 A                      (4) 30 A

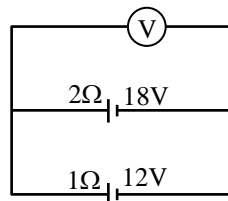
- Q.20** Two batteries, one of emf 18 volts and internal resistance  $2\Omega$  and the other of emf 12 volt and internal resistance  $1\Omega$ , are connected as shown. The voltmeter V will record a reading of -



- (1) 18 V    (2) 30 V    (3) 14 V    (4) 15 V


- Q.21** When a wire of uniform cross-section  $a$ , length  $\ell$  and resistance  $R$  is bent into a complete circle, resistance between any two of diametrically opposite points will be -
- (1)  $R/2$     (2)  $R/4$     (3)  $R/8$     (4)  $4R$

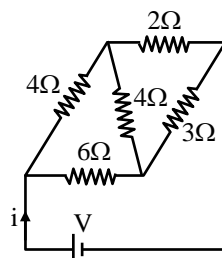- Q.22** For the network shown in the figure the value of the current  $i$  is -




- (1)  $18V/5$                       (2)  $5V/9$   
 (3)  $9V/35$                       (4)  $5V/18$

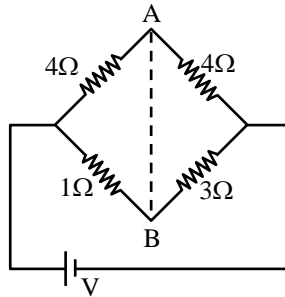
- Q.23** In the circuit shown, if a conducting wire is connected between points A and B, the current in this wire will -



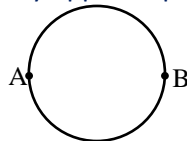- (1) flow from A to B  
 (2) flow in the direction which will be decided by the value of V  
 (3) be zero  
 (4) flow from B to A
- Q.24** The resistance of an ammeter is  $13\Omega$  and its scale is graduated for a current upto 100 amps. After an additional shunt has been connected to this ammeter it becomes possible to measure currents upto 750 amperes by this meter. The value of shunt resistance is -  
 (1)  $2\text{ k}\Omega$  (2)  $20\Omega$  (3)  $2\Omega$  (4)  $0.2\Omega$
- Q.25** A wire of resistance 12 ohms per meter is bent to form a complete circle of radius 10 cm. The resistance between its two diametrically opposite points, A and B as shown in the figure, is -



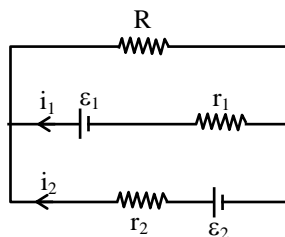- (1)  $6\Omega$  (2)  $0.6\pi\Omega$  (3)  $3\Omega$  (4)  $6\pi\Omega$
- Q.26** See the electrical circuit shown in this figure. Which of the following equations is a correct equation for it ?




- (1)  $\varepsilon_1 - (i_1 + i_2)R + i_1 r_1 = 0$   
 (2)  $\varepsilon_1 - (i_1 + i_2)R - i_1 r_1 = 0$   
 (3)  $\varepsilon_2 - i_2 r_2 - \varepsilon_1 - i_1 r_1 = 0$   
 (4)  $-\varepsilon_2 - (i_1 + i_2)R + i_2 r_2 = 0$
- Q.27** A galvanometer having a coil resistance of  $60\Omega$  shows full scale deflection when a current of 1.0 amp passes through it. It can be converted into an ammeter to read currents upto 5.0 amp by -  
 (1) putting in parallel a resistance of  $15\Omega$   
 (2) putting in parallel a resistance of  $240\Omega$   
 (3) putting in series a resistance of  $15\Omega$   
 (4) putting in series a resistance of  $240\Omega$

**Q.28** A student measures the terminal potential difference ( $V$ ) of a cell (of emf  $\varepsilon$  and internal resistance  $r$ ) as a function of the current ( $I$ ) flowing through it. The slope, and intercept, of the graph between  $V$  and  $I$ , then respectively, equal -

- (1)  $-\varepsilon$  and  $r$                       (2)  $\varepsilon$  and  $-r$   
 (3)  $-r$  and  $\varepsilon$                       (4)  $r$  and  $-\varepsilon$

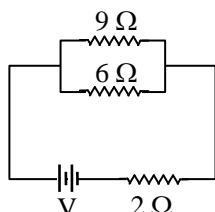**Q.29** If power dissipated in the  $9\Omega$  resistor in the circuit shown is 36 Watt, the potential difference across the  $2\Omega$  resistor is :



- (1) 2 Volt                                  (2) 4 Volt  
 (3) 8 Volt                                  (4) 10 Volt


**Q.30** A current of 2 A flows through a  $2\Omega$  resistor when connected across a battery. The same battery supplies a current of 0.5 A when connected across a  $9\Omega$  resistor. The internal resistance of the battery is :

- (1)  $1\Omega$                                     (2)  $0.5\Omega$   
 (3)  $1/3\Omega$                                 (4)  $1/4\Omega$

**Q.31** The rate of increase of thermo-e.m.f. with temperature at the neutral temperature of a thermocouple :

- (1) is negative  
 (2) is positive  
 (3) is zero  
 (4) depends upon the choice of the two materials of the thermocouple.

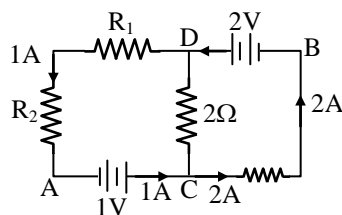**Q.32** In the circuit shown in the figure, if the potential at point A is taken to be zero, the potential at point B is



- (1) +1 V                                    (2) - 1 V  
 (3) +2 V                                    (4) - 2 V


**Q.33** A galvanometer of resistance,  $G$ , is shunted by a resistance  $S$  ohm. To keep the main current in the circuit unchanged the resistance to be put in series with the galvanometer is

- (1)  $\frac{G}{(S+G)}$                               (2)  $\frac{S^2}{(S+G)}$   
 (3)  $\frac{SG}{(S+G)}$                             (4)  $\frac{G^2}{(S+G)}$

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 4**


- Q.1** There are eight resistances of  $R$  ohm each. Two-two resistances are connected in parallel to form couples and these couples are connected in series, then the total resistance of this combination is  
 (1)  $R/2$                                       (2)  $2R$   
 (3)  $4R$                                          (4)  $8R$

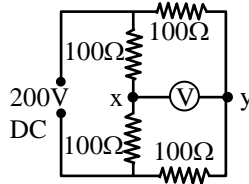- Q.2** For the following circuit the potential difference between  $x$  and  $y$  in volt is -




- (1) 10    (2) 50  
 (3) 100    (4) 0

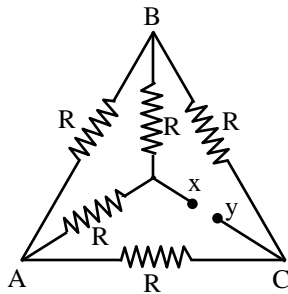- Q.3** The value of total resistance between  $x$  and  $y$  in ohm is -



- (1)  $R$     (2)  $3R$   
 (3)  $4R$     (4)  $5R$

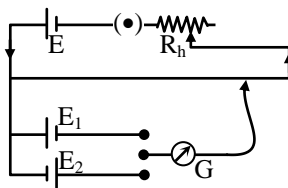
- Q.4** The following diagram shows the circuit for the comparison of e.m.f. of the cells. The circuit can be corrected by -



- (1) Reversing the terminals of  $E$   
 (2) Reversing the terminals of  $E_1$   
 (3) Reversing the terminals of  $E_2$   
 (4) Reversing the current in  $R_h$ .

- Q.5** Two similar cells are connected first in series and then in parallel, the ratio of balancing length on the potentiometer wire will be -  
 (1) 1 : 2    (2) 2 : 1  
 (3) 1 : 4    (4) 4 : 1

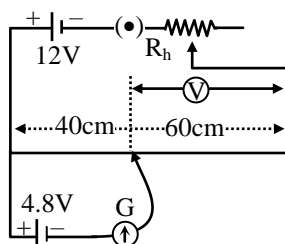**Q.6** In the following circuit, the reading of the voltmeter will be - (in volt)



- (1) 7.2                      (2) 4.8  
 (3) 6                         (4) 4


**Q.7** The resistance of a wire is 50 ohm. Then the graph between log V and log I is -

- (1) straight line              (2) parabola  
 (3) hyperbola                (4) circle

**Q.8** The resistance of wire is 20 ohm. The wire is stretched to three times of its length. Then the resistance will be-


- (1) 6.67  $\Omega$                       (2) 60  $\Omega$   
 (3) 120  $\Omega$                       (4) 180  $\Omega$

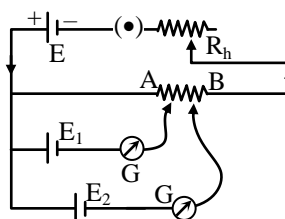**Q.9** In the following diagram, the deflection in the galvanometer in a potentiometer circuit is zero, then -




- (1)  $E_1 > E_2$                       (2)  $E_2 > E_1$   
 (3)  $E_1 = E_2$                       (4)  $E_1 + E_2 = E$

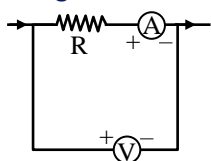**Q.10** In the following circuit, the resistance of a voltmeter is 10,000  $\Omega$  and that of an ammeter is 20 $\Omega$ . If the reading of an ammeter is 0.1 amp. and that of voltmeter is 12 volt, then the value of R is -



- (1) 122  $\Omega$                       (2) 100  $\Omega$   
 (3) 118  $\Omega$                       (4) 116  $\Omega$

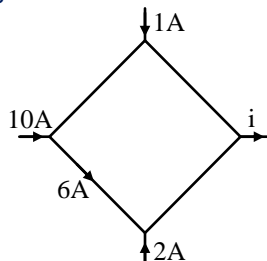**Q.11** Value of current i in the following circuit is -




- (1) 13 A  
 (2) 12 A  
 (3) 9 A  
 (4) none of the above



- Q.12** Which of the following wires of the same material will have higher resistance-
- (1) radius is 1 mm and the length is 40 m.
  - (2) radius is 2 mm and the length is 40 m.
  - (3) radius is 1 mm and the length is 80 m.
  - (4) radius is 2 mm and the length is 80 m.


- Q.13** The resistance of galvanometer is  $G$  ohm and the range is 1 volt. The value of resistance used to convert it into a voltmeter of range 10 volt is-
- (1)  $9G$
  - (2)  $G$
  - (3)  $\frac{1}{9}G$
  - (4)  $10G$

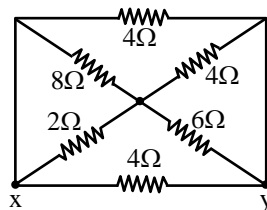- Q.14** The total resistance between x and y in ohm is -



- (1)  $1\Omega$
- (2)  $4\Omega$
- (3)  $\frac{4}{3}\Omega$
- (4)  $\frac{2}{3}\Omega$

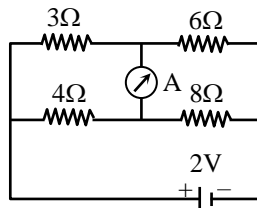- Q.15** The reading of Ammeter in ampere for following circuit is -



- (1) 1
- (2) 1.5
- (3) zero
- (4) 2

- Q.16** The emf of a standard cell is balanced at 150 cm length of a potentiometer wire. When this cell is shunted by a 2 ohm resistance, the null point is obtained at 100 cm. The value of internal resistance of the cell is -

- (1) 0.1 ohm
- (2) 1 ohm
- (3) 2 ohm
- (4) 0.5 ohm

- Q.17** There are two wires of same material but length and diameter of first wire are double of the second wire. Then the resistance of first wire will be -

- (1) double of the resistance of the second wire.
- (2) half of the resistance of the second wire.
- (3) equal to the resistance of the second wire.
- (4) fourth times the resistance of the second wire.

- Q.18** If the length of the wire is doubled, then the specific resistance will be -

- (1) two times
- (2)  $\frac{1}{2}$  times
- (3) four times
- (4) same

- Q.19** The resultant resistance of  $n$  resistance wires each of  $r$  ohm is  $R$ , when they are connected in parallel. When these  $n$  resistance are connected in series, the resultant resistance will be -


- (1)  $\frac{R}{n}$
- (2)  $\frac{R}{n^2}$
- (3)  $nR$
- (4)  $n^2R$

- Q.20** A galvanometer of resistance  $100\Omega$  gives full deflection for a current  $10^{-5}\text{A}$ . The value of shunt required to convert it into an ammeter of range 1 ampere, is -  
 (1)  $1\Omega$  (2)  $10^{-3}\Omega$   
 (3)  $10^{-5}\Omega$  (4)  $100\Omega$

- Q.21** 20% of the main current passes through the galvanometer. If the resistance of the galvanometer is  $G$ , then the resistance of the shunt will be -  
 (1)  $G/50$  (2)  $G/4$  (3)  $50G$  (4)  $9G$


- Q.22** Kirchoff's first and second law shows the conservation of -  
 (1) linear momentum and angular momentum.  
 (2) charge and energy.  
 (3) mass and energy.  
 (4) charge and linear momentum.

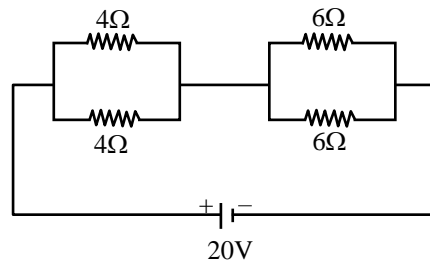- Q.23** Four resistances are connected in a circuit as shown in the following diagram. The value of the current in ampere in 4 ohm and 6 ohm resistance are -



- (1) 2 and 4 (2) 1 and 2  
 (3) 1 and 1 (4) 2 and 2

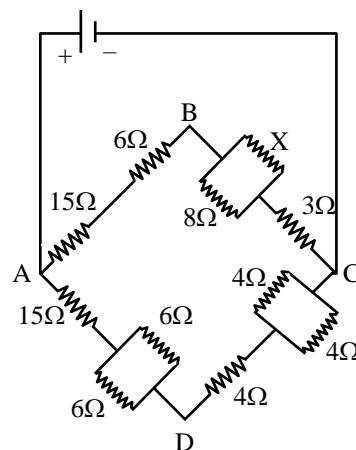
- Q.24** In the following circuit diagram the value of resistance  $X$  for the potential difference between  $B$  and  $D$  is zero -



- (1) 4 ohm (2) 6 ohm  
 (3) 8 ohm (4) 9 ohm

- Q.25** The e.m.f. of a cell is 2.0 volt and the internal resistance is 0.1 ohm. It is connected with a resistance of 3.9 ohm. Then potential difference across the cell is -  
 (1) 0.20 V (2) 1.90 V  
 (3) 1.95 V (4) 2.00 V

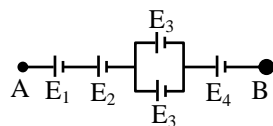**Q.26** In the following circuit the resultant e.m.f. between AB is -



- (1)  $E_1 + E_2 + E_3 + E_4$   
 (2)  $E_1 + E_2 + 2E_3 + E_4$   
 (3)  $E_1 + E_2 + \frac{E_3}{2} + E_4$   
 (4)  $E_1 + E_2 + \frac{E_3}{4} + E_4$
- Q.27** The sensitivity of a potentiometer is increased by -  
 (1) increasing the emf of the cell.  
 (2) increasing the length of the potentiometer wire.  
 (3) decreasing the length of potentiometer wire.  
 (4) none of the above.
- Q.28** A potential gradient is created in the wire by a standard cell for the comparison of emf's of two cells in a potentiometer experiment. Which possibility of the following will cause failure of the experiment ?  
 (1) the emf of the standard cell is higher than that of the other cells.  
 (2) the diameter of the wires is equal and similar.  
 (3) the number of wires is ten.  
 (4) the emf of the standard cell is less than those of both the cells.
- Q.29** A voltmeter of 998 ohm resistance is connected to a cell of emf 2 volt, having internal resistance of 2 ohms. The error in measuring emf will be -  
 (1)  $4 \times 10^{-1}V$  (2)  $2 \times 10^{-3}V$   
 (3)  $4 \times 10^{-3} V$  (4)  $2 \times 10^{-1} V$
- Q.30** The specific resistance of a metal wire is  $64 \times 10^{-6} \Omega \times \text{cm.}$ , the length is 198 cm and the resistance is  $7\Omega$ . The radius of wire is  
 (1) 2.4 cm (2) 0.24 cm  
 (3) 0.024 cm (4) 24 cm
- Q.31** Which of the following statement is wrong -  
 (1) the resistance of a voltmeter is high.  
 (2) the resistance of an ammeter is low.  
 (3) an ammeter is connected in parallel with a conductor in the circuit.  
 (4) a voltmeter is connected in parallel with a resistance in the circuit.
- Q.32** The resistance of the galvanometer is  $25\Omega$  it gives a full scale deflection when a current of 10mA is passed through it. The value of resistance R used in series to convert it into voltmeter of range 100 volt is -  
 (1) 10,000  $\Omega$  (2) 10025  $\Omega$   
 (3) 975  $\Omega$  (4) 9975  $\Omega$
- Q.33** Which of the statement is wrong -  
 (1) when all resistance are equal, then the sensitivity of Wheatstone bridge is maximum.  
 (2) when the galvanometer and the cell are interchanged, then the balancing of wheat stone bridge will be effected.  
 (3) Kirchoff's first law for the currents meeting at the Junctions in an electric circuit shows the conservation of charge.  
 (4) Rheostat can be used as potential divider.

**Q.34** In a meter bridge the null point is obtained at the middle point of the wire. If in one gap the resistance is  $10\Omega$ , then the value of resistance in the other gap is -

- (1)  $10\Omega$  (2)  $5\Omega$   
 (3)  $\frac{1}{5}\Omega$  (4)  $500\Omega$

**Q.35** A new electric store house of  $1.5$  emf of a flash gives a current of  $15A$ , when it is connected with an electric ammeter of  $0.04\Omega$ , then the value of internal resistance of the electric store house is -

- (1)  $0.04\Omega$  (2)  $0.06\Omega$   
 (3)  $0.10\Omega$  (4)  $10\Omega$

**Q.36** In a torch there are two cells each of  $1.45$  volt and  $0.15\Omega$ . Each cell gives a current to filament of a lamp of  $1.5\Omega$ , then the value of current in ampere is -

- (1)  $16.11$  (2)  $1.611$   
 (3)  $0.1611$  (4)  $2.6$


**Q.37** In a potentiometer experiment a voltage source is balanced at  $60$  cm length where as a  $3$  volt battery is balanced at  $45$ cm length. What is the voltage of unknown voltage source-

- (1)  $3V$  (2)  $4V$   
 (3)  $4.5V$  (4)  $6V$

**Q.38** A potential difference  $V$  is applied across a copper wire of diameter  $d$  and length  $L$ . When only  $d$  is doubled, the drift velocity -


- (1) increases two times  
 (2) decreases  $\frac{1}{2}$  times  
 (3) does not change  
 (4) decreases  $\frac{1}{4}$  times

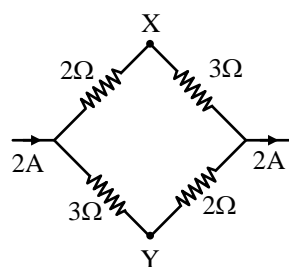**Q.39** Find the potential difference between  $X$  and  $Y$  in volt is -



- (1)  $1$  (2)  $-1$  (3)  $2$  (4)  $-2$

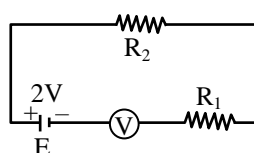**Q.40** A cell of e.m.f.  $2V$  and negligible internal resistance is connected to resistor  $R_1$  and  $R_2$  as shown in the figure. The resistance of the voltmeter,  $R_1$  and  $R_2$  are  $80\Omega$ ,  $40\Omega$  and  $80\Omega$  respectively. The reading of the voltmeter is -



- (1)  $1.78V$  (2)  $1.60V$   
 (3)  $0.80V$  (4)  $1.33V$


**Q.41** Potentiometer wire length is 10 m, having a total resistance of  $10\Omega$ . If a battery of emf 2 volt (negligible internal resistance) and a rheostat is connected to it then potential gradient is  $20\text{mV/m}$  find the resistance applied through rheostat -

- (1)  $90\Omega$  (2)  $990\Omega$   
 (3)  $40\Omega$  (4)  $190\Omega$

**Q.42** In a potentiometer, a standard cell of 1.1V is balanced through a length of 7.04m For calibration of ammeter the resistance of  $1\Omega$  is balanced through a length of 0.64m if the reading of ammeter is 0.11 amp. Then error in measurement is -

- (1) 0.01 A (2)  $-0.01$  A  
 (3) 1.0 A (4)  $-1.0$  A

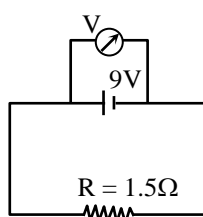**Q.43** When a voltmeter is connected across the terminals of a cell, it measure 9 volt. If a resistance of  $1.5\Omega$  is connected across the terminals of a cell as shown in figure. Then current flowing through this resistance is



- (1) 1.3 A (2) 6 A  
 (3) 9 A (4) 12 A


**Q.44** The resistance of a coil in a platinum resistance thermometer at  $0^\circ\text{C}$  is 5 ohm and at  $100^\circ\text{C}$  it is 5.75 ohm. Its resistance at an unknown temperature is 5.15 ohm. Then the unknown temperature will be -

- (1)  $40^\circ\text{C}$  (2)  $10^\circ\text{C}$  (3)  $15^\circ\text{C}$  (4)  $20^\circ\text{C}$

**Q.45** Eight identical cells each of potential E and internal resistance r are connected in series to form a closed circuit. An ideal voltmeter connected across 2 cells will read-

- (1) 13 E (2) zero (3) 2 E (4) 10 E

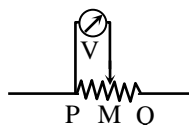**Q.46** P, Q is a uniform wire of resistance  $2000\Omega$  and M the mid point of PQ. A voltmeter of resistance  $1000\Omega$  is connected between P and M. The reading of the voltmeter, when, the potential difference applied between PQ is 150 volt will be -




- (1) 150 V (2) 100 V (3) 75 V (4) 50 V

**Q.47** Two rods A and B made up of same metal have same length. The ratio of their resistances is 1 : 2. If these rods are immersed in water then loss in weight will be -

- (1) more in A (2) more in B  
 (3) same in A and B (4) in the ratio 1 : 2

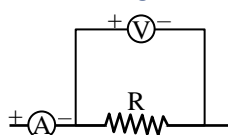**Q.48** A student connects a voltmeter, ammeter and resistance according to the circuit given. If the voltmeter reading is 20 V and ammeter reading is 4 A, then the resistance will be -




- (1) equal to  $5\Omega$   
 (2) more than  $5\Omega$   
 (3) less than  $5\Omega$   
 (4) more or less depending on the material of wire

- Q.49** A potentiometer wire of 10 m length and having a resistance of 1 ohm/m is connected to an accumulator of emf 2.2 volt and a high resistance box. To obtain a potential gradient of 2.2mV/m, the value of resistance used from the resistance box is -
- (1) 790 ohm                      (2) 810 ohm  
 (3) 990 ohm                      (4) 1000 ohm


- Q.50** For two wires A and B of same material and of same mass, the radius of A is double that of B. If the resistance of wire A is 34  $\Omega$ , then that of B will be -
- (1) 544  $\Omega$                       (2) 272  $\Omega$   
 (3) 68  $\Omega$                       (4) 17  $\Omega$

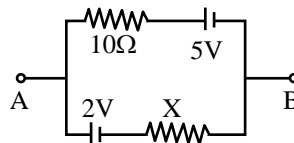- Q.51** In the following circuit if  $V_{AB} = 4V$ , then the value of resistance X in ohms will be -



- (1) 5            (2) 10            (3) 15            (4) 20

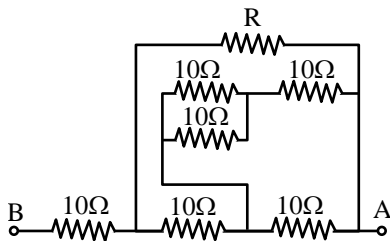- Q.52** For the network of resistance shown in the figure the equivalent resistance of the network between the points A and B is 18  $\Omega$ . The value of unknown resistance R is -




- (1) 8  $\Omega$                       (2) 10  $\Omega$   
 (3) 16  $\Omega$                       (4) 24  $\Omega$

- Q.53** When a potential difference is applied across the ends of a linear metallic conductor -
- (1) the free electrons are accelerated continuously from the lower potential end to the higher potential end of the conductor  
 (2) the free electrons are accelerated continuously from the higher potential end to the lower potential end of the conductor  
 (3) the free electrons acquire a constant drift velocity from the lower potential end to the higher potential end of the conductor  
 (4) the free electrons are set in motion from their position of rest

- Q.54** A current of 2A is flowing through a cell of e.m.f. 5 V and internal resistance 0.5 $\Omega$  from negative to positive electrode. If the potential of negative electrode is 10 V, the potential of positive electrode will be -
- (1) 5V                      (2) 14V  
 (3) 15V                      (4) 16V

- Q.55** 100 cells, each of e.m.f. 5V and internal resistance 1 $\Omega$ , are to be arranged so as to produce maximum current in a 25 $\Omega$  resistance. Each row is to contain equal number of cells. The number of rows should be -
- (1) 2                      (2) 4  
 (3) 5                      (4) 10

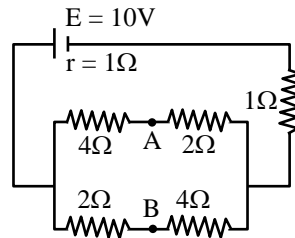- Q.56** In the circuit shown below, the cell has an e.m.f. of 10 V and internal resistance of 1 Ω. The other resistance are shown in the figure. The potential difference  $V_A - V_B$  is




- (1) 6V    (2) 4V    (3) 2V    (4) -2V

- Q.57** Two resistance  $R_1$  and  $R_2$  are made of different materials. The temperature coefficient of the material of  $R_1$  is  $\alpha$  and of the material of  $R_2$  is  $-\beta$ . The resistance of the series combination  $R_1$  and  $R_2$  will not change with temp., then ratio of resistance of two wire at  $0^\circ\text{C}$  will be -


- (1)  $\frac{\alpha}{\beta}$     (2)  $\frac{\alpha + \beta}{\alpha - \beta}$     (3)  $\frac{\alpha^2 + \beta^2}{\alpha\beta}$     (4)  $\frac{\beta}{\alpha}$

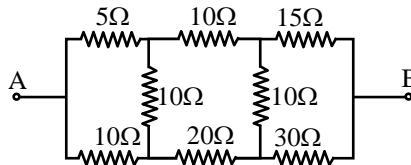- Q.58** In the arrangement of resistances shown below. The effective resistance between point A and B is -



- (1) 20 Ω    (2) 30 Ω  
(3) 90 Ω    (4) 110 Ω

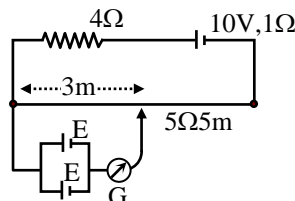- Q.59** A resistance of 4Ω and a wire of length 5 m and resistance 5Ω are joined in series and connected to a cell of e.m.f. 10V and internal resistance 1Ω. A parallel combination of two identical cells is balanced across 300 cm of the wire. The e.m.f. E of each cell is -



- (1) 1.5V    (2) 3.0V    (3) 0.67V    (4) 1.33V

- Q.60** The resistance of a galvanometer is 50Ω and the current required to give full scale deflection is 100μA. In order to convert it into an ammeter, reading upto 10A, it is necessary to put a resistance of -

- (1)  $5 \times 10^{-3} \Omega$  in parallel  
(2)  $5 \times 10^{-4} \Omega$  in parallel  
(3)  $10^5 \Omega$  in series  
(4) 99, 950 Ω in series


- Q.61** The resistivity of a wire depends on its -

- (1) length    (2) area of cross section  
(3) shape    (4) material

- Q.62** The conductivity of a super conductor is -

- (1) infinite    (2) very large  
(3) very small    (4) zero

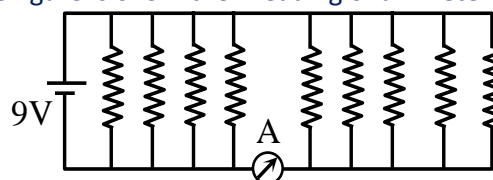
- Q.63** Electromotive force of a cell is basically a -  
 (1) force (2) power  
 (3) work (4) current capacity
- Q.64** A battery of 10V and internal resistance  $0.5\Omega$  is connected across a variable resistance R. The value of R for which the power delivered in its maximum state, is equal to -  
 (1)  $0.5\Omega$  (2)  $1\Omega$  (3)  $1.5\Omega$  (4)  $2\Omega$
- Q.65** A galvanometer has a resistance G and current  $i_a$  flowing in it, produces full scale deflection. If  $S_1$  is the value of shunt which converts it into an ammeter of range  $0 - i$  and  $S_2$  is the value of the shunt for the range  $0 - 2i$ . Then the ratio  $\frac{S_1}{S_2}$  will be -  
 (1) 1 (2) 2  
 (3)  $\frac{1}{2} \left( \frac{i - i_a}{2i - i_a} \right)$  (4)  $\left( \frac{2i - i_a}{i - i_a} \right)$
- Q.66** Constantan wire is used in making standard resistances, because its -  
 (1) specific resistance is low  
 (2) density is high  
 (3) temperature coeff. of resistance is negligible  
 (4) melting point is high
- Q.67** When a resistance of 2 ohm is connected across the terminals of a cell, the current is 0.5A. When the resistance is increased to 5 ohm, the current is 0.25A. The e.m.f. of the cell is -  
 (1) 1.0 V (2) 1.5 V  
 (3) 2.0 V (4) 2.5 V
- Q.68** Two non ideal batteries are connected in parallel consider the following statements:  
 (A) The equivalent emf is smaller than either of the two emfs  
 (B) The equivalent internal resistance is smaller than either of the two internal resistances  
 (1) both A and B are correct  
 (2) A is correct but B is wrong  
 (3) B is correct but A is wrong  
 (4) both A and B are wrong
- Q.69** Equivalent resistance of series combination -  
 (1) is equals to mean of individual resistors  
 (2) is less than the lesser one  
 (3) is in between the smaller and bigger resistors  
 (4) is sum of individual resistors
- Q.70** The net resistance of a voltmeter should be large to ensure that -  
 (1) it does not get over heated  
 (2) it does not draw excessive current  
 (3) it can measure large potential difference  
 (4) it does not appreciably change the potential difference to be measured
- Q.71** If each resistance in the figure is of  $9\Omega$  then reading of ammeter is -



- (1) 5A (2) 8A (3) 2A (4) 9A




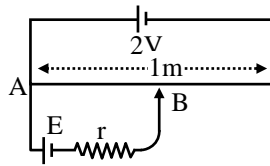- Q.72** In figure battery E is balanced on 55 cm length of potentiometer wire but when a resistance of  $10\ \Omega$  is connected in parallel with the battery then it balances on 50cm length of the potentiometer wire then internal resistance  $r$  of the battery is -



- (1)  $1\ \Omega$     (2)  $3\ \Omega$     (3)  $10\ \Omega$     (4)  $5\ \Omega$

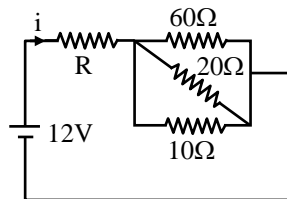- Q.73** If  $i = 0.25$  amp. in figure then value of  $R$  is -



- (1)  $48\ \Omega$     (2)  $12\ \Omega$   
(3)  $120\ \Omega$     (4)  $42\ \Omega$


- Q.74** A copper wire stretched so as to make it 0.1% longer. The percentage increase in the resistance of the wire is -

- (1) 1.0    (2) 2.0  
(3) 0.1    (4) 0.2

- Q.75** 10,000 electrons are passing per minute through a tube of radius 1 cm. The resulting current is -

- (1) 10,000 A    (2)  $0.25 \times 10^{-16}$  A  
(3)  $10^{-9}$  A    (4)  $0.5 \times 10^{-19}$  A

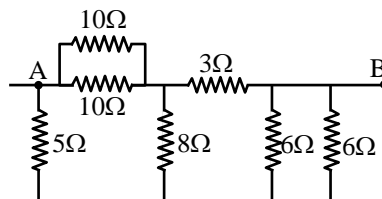- Q.76** Seven resistances are connected as shown in the figure. The equivalent resistance between A and B is -




- (1)  $3\ \Omega$     (2)  $4\ \Omega$   
(3)  $4.5\ \Omega$     (4)  $5\ \Omega$

- Q.77** At what temperature will the resistance of a copper wire become three times its value at  $0^\circ\text{C}$ ? [Temperature coefficient of resistance for copper =  $4 \times 10^{-3}$  per  $^\circ\text{C}$ ]

- (1)  $400^\circ\text{C}$     (2)  $450^\circ\text{C}$   
(3)  $500^\circ\text{C}$     (4)  $550^\circ\text{C}$

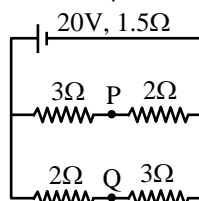
- Q.78** In the circuit shown below, the internal resistance of the battery is  $1.5\ \Omega$  and  $V_P$  and  $V_Q$  are the potentials at P and Q respectively. What is the potential difference between the points P and Q -



- (1) zero    (2) 4 volt ( $V_P > V_Q$ )  
(3) 4 volt ( $V_Q > V_P$ )    (4) 2.5 volt ( $V_Q > V_P$ )

- Q.79** A cylindrical wire is stretched such that its length gets doubled but volume remains same, the resistance of wire becomes -  
 (1) four times (2) remains same  
 (3) half (4) becomes double

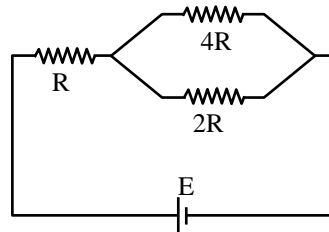
- Q.80** In a network as shown in the figure the potential difference across the resistance  $2R$  is (the cell has an emf of  $E$  and has no internal resistance) -



- (1)  $2E$  (2)  $4E/7$   
 (3)  $E/7$  (4)  $E$


- Q.81** There are  $8.4 \times 10^{22}$  free electrons per  $\text{cm}^3$  in copper. The current in the wire is  $0.21 \text{ A}$  ( $e = 1.6 \times 10^{-19} \text{ C}$ ). Then the drifts velocity of electrons in a copper wire of  $1 \text{ mm}^2$  cross section, will be -  
 (1)  $2.12 \times 10^{-5} \text{ m/s}$  (2)  $0.78 \times 10^{-5} \text{ m/s}$   
 (3)  $1.56 \times 10^{-5} \text{ m/s}$  (4) none of these

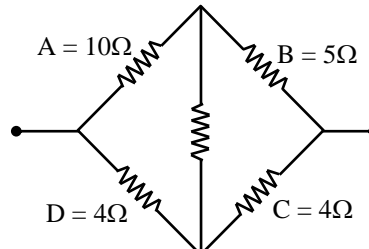- Q.82** In a typical wheatstone network the resistance in cyclic order are  $A = 10\Omega$ ,  $B = 5\Omega$ ,  $C = 4\Omega$  and  $D = 4\Omega$  for the bridge to be balanced -



- (a)  $10 \Omega$  should be connected in parallel with A  
 (b)  $10 \Omega$  should be connected in series with A  
 (c)  $5 \Omega$  should be connected in series with B  
 (d)  $5 \Omega$  should be connected in parallel with B  
 (1) a, b (2) b, c  
 (3) a, c (4) all

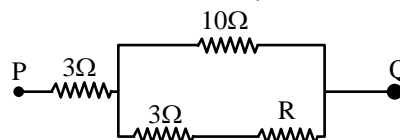
- Q.83** In the circuit shown here, what is the value of the unknown resistor  $R$  so that the total resistance of the circuit between points 'P' and 'Q' is also equal to  $R$  -




- (1)  $3 \Omega$  (2)  $\sqrt{39} \Omega$  (3)  $\sqrt{69} \Omega$  (4)  $10 \Omega$

- Q.84** A battery has e.m.f.  $4V$  and internal resistance ' $r$ '. When this battery is connected to an external resistance of  $2 \text{ ohms}$ , a current of  $1 \text{ amp}$ . flows in the circuit. How much current will flow if the terminals of the battery are connected directly ?  
 (1)  $1A$  (2)  $2A$   
 (3)  $4A$  (4) infinite

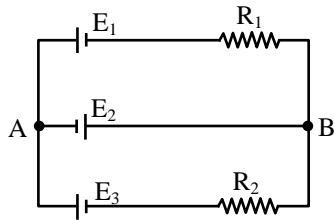- Q.85** In the circuit shown here,  $E_1 = E_2 = E_3 = 2V$  and  $R_1 = R_2 = 4$  ohms. The current flowing between points A and B through battery  $E_2$  is -



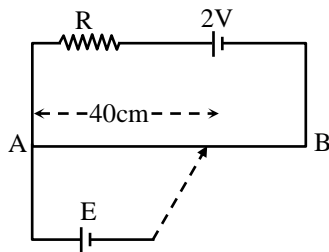
- (1) zero (2) 2 amp from A to B  
 (3) 2 amp from B to A (4) none of the above
- Q.86** AB is a potentiometer wire of length 100 cm and its resistance is 10 ohm. It is connected in series with a resistance  $R = 40$  ohm and a battery of e.m.f. 2V and negligible internal resistance. If a source of unknown e.m.f.  $E$  is balanced by 40 cm length of the potentiometer wire, the value of  $E$  is -



- (1) 0.8 V (2) 1.6 V (3) 0.08 V (4) 0.16 V
- Q.87** Three resistance of values  $2\Omega$ ,  $3\Omega$  and  $6\Omega$  are to be connected to produce an effective resistance of  $4\Omega$ . This can be done by connecting -
- (1)  $3\Omega$  resistance in series with the parallel combination of  $2\Omega$  and  $6\Omega$   
 (2)  $6\Omega$  resistance in series with the parallel combination of  $2\Omega$  and  $3\Omega$   
 (3)  $2\Omega$  resistance in series with the parallel combination of  $3\Omega$  and  $6\Omega$   
 (4)  $2\Omega$  resistance in parallel with the parallel combination of  $3\Omega$  and  $6\Omega$
- Q.88** A battery of electro motive force  $E$  is connected in series with a resistance  $R$  and a voltmeter. An ammeter is connected in parallel with the battery -
- (1) neither the ammeter nor the voltmeter will be damaged.  
 (2) both ammeter and voltmeter are likely to be damaged.  
 (3) only voltmeter is likely to be damaged  
 (4) only ammeter is likely to be damaged.
- Q.89** Two resistance wires on joining in parallel the resultant resistance is  $\frac{6}{5}$  ohm. One of the wire breaks, the effective resistance is 2 ohm. The resistance of the broken wire was -
- (1)  $\frac{3}{5}$  ohm (2) 2 ohm  
 (3)  $\frac{6}{5}$  ohm (4) 3 ohm
- Q.90** The temperature coefficient of resistance of a wire is 0.00125 per degree celcius. At 300 K its resistance is 1 ohm. The resistance of the wire will be 2 ohm at following temperature -
- (1) 1154 K (2) 1127 K  
 (3) 600 K (4) 1400 K


- Q.91** There is a current of 40 ampere in a wire of  $10^{-6} \text{ m}^2$  area of cross-section. If the number of free electron per  $\text{m}^3$  is  $10^{29}$ , then the drift velocity will be -  
 (1)  $1.25 \times 10^3 \text{ m/s}$  (2)  $2.50 \times 10^{-3} \text{ m/s}$   
 (3)  $25.0 \times 10^{-3} \text{ m/s}$  (4)  $250 \times 10^{-3} \text{ m/s}$
- Q.92** An ammeter and a voltmeter are joined in series to a cell. Their readings are A and V respectively. If a resistance is now joined in parallel with the voltmeter-  
 (1) both A and V will decrease  
 (2) both A and V will increase  
 (3) A will increase, V will decrease  
 (4) A will decrease, V will increase.
- Q.93** A cell supplies a current of 0.9 A through a  $2\Omega$  resistor and a current of 0.3 A through a  $7\Omega$  resistor. The internal resistance of the cell is -  
 (1)  $1.0 \Omega$  (2)  $0.5 \Omega$   
 (3)  $2.0 \Omega$  (4)  $1.2 \Omega$

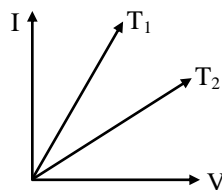- Q.94** The current voltage graph for a given metallic conductor at two different temperatures  $T_1$  and  $T_2$  are as shown in the figure. Then -



- (1)  $T_1 > T_2$   
 (2)  $T_1 = T_2$   
 (3) nothing can be said about  $T_1$  and  $T_2$   
 (4)  $T_1 < T_2$
- Q.95** A galvanometer of  $100\Omega$  resistance gives complete deflection on flowing 10 mA current. What should be the value of shunt so that it can measure 100 mA -  
 (1)  $11.11 \Omega$  (2)  $9.9 \Omega$   
 (3)  $1.1 \Omega$  (4)  $4.4 \Omega$
- Q.96** For changing the range of a galvanometer with G ohm resistance from V volt to nV, what will be the value of resistance connected in series to it -  
 (1)  $(n - 1)G$  (2)  $\frac{G}{n}$   
 (3)  $nG$  (4)  $\frac{G}{n - 1}$
- Q.97** N identical cells whether joined together in series or in parallel, give the same current, when connected to an external resistance of 'R'. The internal resistance of each cell is  
 (1)  $r = nR$  (2)  $r = R$   
 (3)  $r = \frac{R}{n}$  (4)  $r = n^2R$

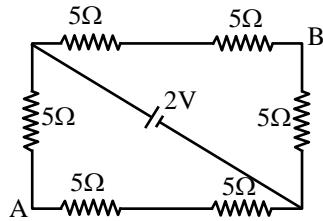**Q.98** The potential difference between the point A and B in the following circuit shown in the figure -



- (1)  $\frac{2}{3}$  volt                      (2)  $\frac{4}{5}$  volt  
 (3)  $\frac{8}{9}$  volt                      (4) 2 volt

**Q.99** In the potentiometer experiment if deflection in galvanometer is measured zero then current will become zero in

- (1) potentiometer wire  
 (2) galvanometer circuit  
 (3) main circuit  
 (4) cell


**Q.100** Length of a potentiometer wire is kept more and uniform to active -

- (1) uniform and more potential gradient  
 (2) non-uniform and more potential gradient  
 (3) uniform and less potential gradient  
 (4) non-uniform and less potential gradient


**Q.101** The balancing length is obtained at 78.4 cm length while measuring the potential difference at the ends of a resistance wire. When same potential difference is measured with a voltmeter, it shows 1.20 volt. If a standard cell of emf 1.018 volt is balanced at 63.2 cm, the error in voltmeter reading in volt will be -

- (1) - 0.06                      (2) + 0.06  
 (3) - 0.03                      (4) + 0.03

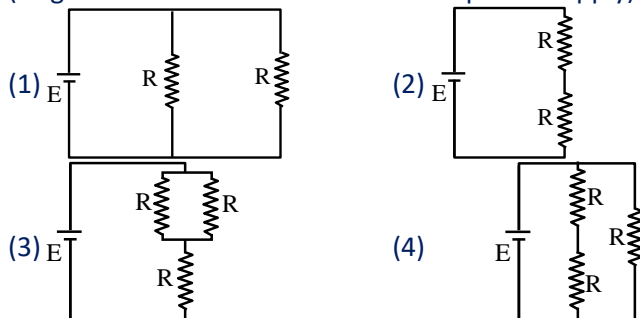**Q.102** Consider four circuits shown in the figure below. In which circuit power dissipated is greater (Neglect the internal resistance of the power supply) -



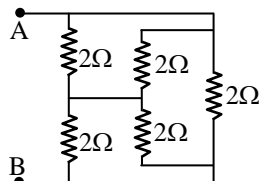**Q.103** The equivalent resistance across AB is-




- (1) 1Ω                      (2) 2Ω  
 (3) 3Ω                      (4) 4Ω

- Q.104** There are three voltmeters of the same range but of resistance  $10000\ \Omega$ ,  $8000\ \Omega$  and  $4000\ \Omega$  respectively. The best voltmeter among these is the one whose resistance is-
- (1)  $10000\ \Omega$
  - (2)  $8000\ \Omega$
  - (3)  $4000\ \Omega$
  - (4) all are equally good


- Q.105** When a voltmeter and an ammeter are connected respectively across the terminals of a cell, measures  $5\text{V}$  and  $10\text{A}$ . Now only a resistance of  $2\ \Omega$  is connected across the terminal of the cell. The current flowing through this resistance is-
- (1)  $7.5\ \text{A}$
  - (2)  $5.0\ \text{A}$
  - (3)  $2.5\ \text{A}$
  - (4)  $2.0\ \text{A}$

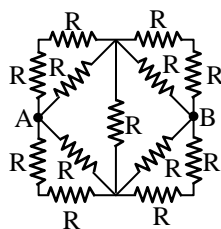- Q.106** Thirteen resistance each of resistance  $R$  ohm are connected in the circuit as shown in the figure. The effective resistance between A and B is-



- (1)  $\frac{4R}{3}\ \Omega$
- (2)  $2R\ \Omega$
- (3)  $R\ \Omega$
- (4)  $\frac{2R}{3}\ \Omega$

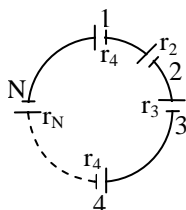- Q.107** A group of  $N$  cells whose emf varies directly with the internal resistance as per the equation  $E_N = 1.5 r_N$  are connected as shown in the figure. The current  $I$  in the circuit is-



- (1)  $5.1\ \text{A}$
- (2)  $0.51\ \text{A}$
- (3)  $1.5\ \text{A}$
- (4)  $0.15\ \text{A}$

- Q.108** A galvanometer has resistance  $36\ \Omega$ . If a shunt of  $4\ \Omega$  is added with this, then fraction of current that passes through galvanometer is-

- (1)  $\frac{1}{4}$
- (2)  $\frac{1}{9}$
- (3)  $\frac{1}{10}$
- (4)  $\frac{1}{40}$

- Q.109** If  $10^6$  electrons/s are flowing through an area of cross section of  $10^{-4}\ \text{m}^2$  then the current will be-
- (1)  $1.6 \times 10^{-7}\ \text{A}$
  - (2)  $1.6 \times 10^{-13}\ \text{A}$
  - (3)  $1 \times 10^{-6}\ \text{A}$
  - (4)  $1 \times 10^2\ \text{A}$

- Q.110** The terminal voltage is  $\frac{E}{2}$  when a current of  $2\text{A}$  is flowing through  $2\ \Omega$  resistance, then the internal resistance of cell is-
- (1)  $1\ \Omega$
  - (2)  $2\ \Omega$
  - (3)  $3\ \Omega$
  - (4)  $4\ \Omega$

**Q.111** A  $1\Omega$  voltmeter has range 1V. Find the additional resistance which has to join in series in voltmeter to increase the range of voltmeter to 100 V -

- (1)  $10\Omega$     (2)  $\frac{1}{99}\Omega$     (3)  $99\Omega$     (4)  $100\Omega$

**Q.112** The length of a given cylindrical wire is increased by 100%. Due to the consequent decrease in diameter the change in the resistance of the wire will be-

- (1) 300%    (2) 200%  
(3) 100%    (4) 50%


**Q.113** The length of a wire of a potentiometer is 100 cm, and the emf of its standard cell is E volt. It is employed to measure the e.m.f. of a battery whose internal resistance is  $0.5\Omega$ . If the balance point is obtained at  $\ell = 30$  cm from the positive end, the e.m.f. of the battery is-

- (1)  $\frac{30E}{100}$     (2)  $\frac{30E}{100.5}$   
(3)  $\frac{30E}{(100-0.5)}$     (4)  $\frac{30(E-0.5)}{100}$


**Q.114** Three unequal resistors in parallel are equivalent to a resistant 1 ohm. If two of them are in the ratio 1 : 2 and if no resistance value is fractional, the largest of the three resistance in ohms is-

- (1) 4    (2) 6  
(3) 8    (4) 12

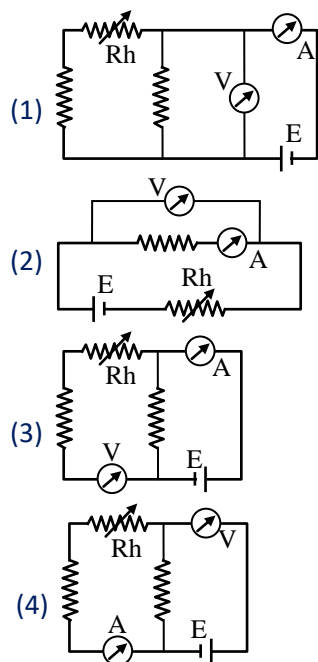**Q.115** Express which of the following setups can be used to verify Ohm's law-




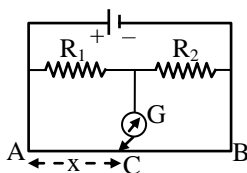**Q.116** In the shown arrangement of the experiment of the meter bridge if AC corresponding to null deflection of galvanometer is x, what would be its value if the radius of the wire AB is doubled-



- (1) x    (2)  $\frac{x}{4}$   
(3) 4x    (4) 2x

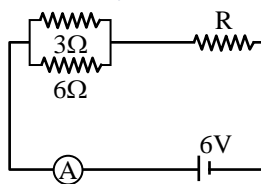**Q.117** If the ammeter in the given circuit reads 2A, the resistance R is-




- (1) 1 ohm  
 (2) 2 ohm  
 (3) 3 ohm  
 (4) 4 ohm

**Q.118** Resistance in the two gaps of a meter bridge are 10 ohm and 30 ohm respectively. If the resistances are interchanged the balance point shifts by -


- (1) 33.3 cm  
 (2) 66.67 cm  
 (3) 25 cm  
 (4) 50 cm

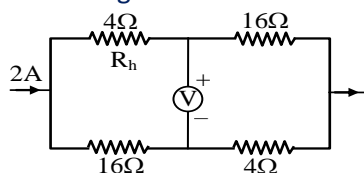**Q.119** In the circuit shown below. The reading of the voltmeter V is -



- (1) 12 V  
 (2) 8 V  
 (3) 20 V  
 (4) 16 V

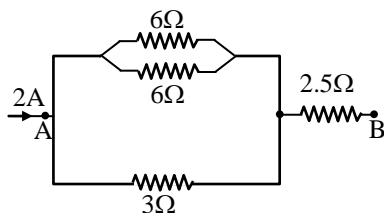**Q.120** The equivalent resistance and potential difference between A and B for the circuit is respectively-




- (1) 4Ω, 8V  
 (2) 8Ω, 4V  
 (3) 2Ω, 2V  
 (4) 16Ω, 8V

**Q.121** Resistance of an ideal voltmeter is -

- (1) zero  
 (2) less than 1 ohm  
 (3) more than 1 ohm  
 (4) infinite

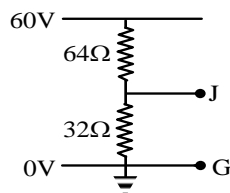**Q.122** Find potential of J with respect to G -



- (1) 40 V  
 (2) 60 V  
 (3) 20 V  
 (4) 30 V

**Q.123** In potentiometer experiment when terminals of the cell is at distance of 52 cm, then no current flows through it. When 5Ω shunt resistance is connected in it then balance length is at 40 cm. the internal resistance of the cell is -

- (1) 5  
 (2)  $\frac{200}{52}$   
 (3)  $\frac{52}{8}$   
 (4) 1.5

**Q.124** A potentiometer wire has resistance 40Ω and its length is 10m. It is connected by a resistance of 760 Ω in series. If emf of battery is 2V then potential gradient is -

- (1)  $0.5 \times 10^{-6}$  V/m  
 (2)  $1 \times 10^{-6}$  V/m  
 (3)  $1 \times 10^{-2}$  V/m  
 (4)  $2 \times 10^{-6}$  V/m



## IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 5

These questions of two statements each, printed as Assertion and Reason. While answering these Questions you are required to choose any one of the following four responses.

(A) If both Assertion & Reason are true & the Reason is a correct explanation of the Assertion.

(B) If both Assertion and Reason are true but Reason is not a correct explanation of the Assertion.

(C) If Assertion is true but the Reason is false.

(D) If Assertion & Reason both are false.

- Q.1** **Assertion:** The resistance of a copper wire varies directly as the length and diameter.  
**Reason :** Because the resistance varies directly the area of cross-section.  
(1) A (2) B (3) C (4) D
- Q.2** **Assertion :** When cells are connected in parallel to the external load, the effective e.m.f increases.  
**Reason :** Because effective internal resistance of cells decreases.  
(1) A (2) B (3) C (4) D
- Q.3** **Assertion :** The total resistance in series combination of resistors increases and in parallel combination of resistors decreases.  
**Reason :** In series combination of resistors, the effective length of resistors increases and in parallel combination of resistors, the area of cross-section of the resistors increases.  
(1) A (2) B (3) C (4) D
- Q.4** **Assertion :** In parallel combination of electrical appliance, total power consumption is equal to the sum of the powers of the individual appliances.  
**Reason :** In parallel combination, the voltage across each appliance is the same, as required for the proper working of electrical appliance.  
(1) A (2) B (3) C (4) D
- Q.5** **Assertion :** In series combination of electrical bulbs of lower power emits more light than that of higher power bulb.  
**Reason :** The lower power bulb in series gets more current than the higher power bulb.  
(1) A (2) B (3) C (4) D
- Q.6** **Assertion :** Each bulb in a frill of 20 bulbs in series when connected to supply voltage will emit more light than each bulb in frill of 19 bulbs in series when connected to same supply voltage.  
**Reason :** Each bulb in a frill of 20 bulbs in series will get less voltage than that in frill of 19 bulbs.  
(1) A (2) B (3) C (4) D
- Q.7** **Assertion:** When a wire is not connected to battery, then no current is flow.  
**Reason:** Electrons moves randomly or does not move in particular direction.  
(1) A (2) B (3) C (4) D
- Q.8** **Assertion:** Electric field inside a current carrying wire is zero.  
**Reason:** Net charge on wire is non zero.  
(1) A (2) B (3) C (4) D
- Q.9** **Assertion:** A voltmeter must be connected in parallel in a circuit and it should have a high resistance.  
**Reason:** The introduction of the voltmeter in the circuit must not effect the P.D. it is to measure.  
(1) A (2) B (3) C (4) D

- Q.10 Assertion:** For the same e.m.f. the availability of current from the secondary cell is greater as compared to the primary cell.  
**Reason:** Generally the resistance of secondary cell is less than of primary cell.  
(1) A (2) B (3) C (4) D
- Q.11 Assertion:** Electric field outside the wire due to steady current carrying wire is zero.  
**Reason:** Net charge present on current carrying wire is zero.  
(1) A (2) B (3) C (4) D
- Q.12 Assertion:** Kirchhoff's voltage law indicates that electro static field is conservative.  
**Reason:** Potential difference between two points in a circuit does not depends on path.  
(1) A (2) B (3) C (4) D
- Q.13 Assertion:** Terminal potential difference of a cell is always less than its emf.  
**Reason:** Potential drop on internal resistance of cell increases terminal potential difference.  
(1) A (2) B (3) C (4) D
- Q.14 Assertion:** When Wheatstone bridge is balanced then current through cell depends on resistance of galvanometer.  
**Reason:** At balanced condition current through galvanometer is non zero.  
(1) A (2) B (3) C (4) D
- Q.15 Assertion:** Potentiometer measures correct value of emf of a cell.  
**Reason:** Because no current flows through cell at null point.  
(1) A (2) B (3) C (4) D
- Q.16 Assertion:** When identical cells are connected in parallel to the external load, the effective e.m.f increases.  
**Reason:** All the cells will be sending unequal current to the external load in the same direction.  
(1) A (2) B (3) C (4) D
- Q.17 Assertion:** Potentiometer is an ideal instrument to measure the potential difference.  
**Reason:** Potential gradient along the potentiometer wire can be made very small.  
(1) A (2) B (3) C (4) D
- Q.18 Assertion:** An ammeter is always connected in series whereas a voltmeter is connected in parallel.  
**Reason:** An ammeter is a low-resistance galvanometer while a voltmeter is high-resistance galvanometer  
(1) A (2) B (3) C (4) D
- Q.19 Assertion:** The potentiometer wire is made of manganin.  
**Reason:** For manganin, the temperature coefficient of resistance is almost zero and its resistivity very less.  
(1) A (2) B (3) C (4) D
- Q.20 Assertion:** Current is a scalar quantity.  
**Reason:** Electric current arises due to continuous flow of charged particles or ions.  
(1) A (2) B (3) C (4) D
- Q.21 Assertion:** A larger dry cell has higher emf.  
**Reason:** The emf of a dry cell is proportional to its size.  
(1) A (2) B (3) C (4) D

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 1 (ANSWERS)**

<b>Q.No.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>
Ans.	3	3	4	1	3	2	2	4	4	2	4	1	3	2	4	1	2	2	1	3
<b>Q.No.</b>	<b>21</b>	<b>22</b>	<b>23</b>	<b>24</b>	<b>25</b>	<b>26</b>	<b>27</b>	<b>28</b>	<b>29</b>	<b>30</b>	<b>31</b>	<b>32</b>	<b>33</b>	<b>34</b>	<b>35</b>	<b>36</b>	<b>37</b>	<b>38</b>	<b>39</b>	<b>40</b>
Ans.	3	3	3	2	3	2	1	2	1	1	3	4	1	2	2	2	2	2	4	1
<b>Q.No.</b>	<b>41</b>	<b>42</b>	<b>43</b>	<b>44</b>	<b>45</b>	<b>46</b>	<b>47</b>	<b>48</b>	<b>49</b>	<b>50</b>	<b>51</b>	<b>52</b>	<b>53</b>	<b>54</b>	<b>55</b>	<b>56</b>	<b>57</b>	<b>58</b>	<b>59</b>	<b>60</b>
Ans.	3	3	1	2	3	1	3	1	1	3	3	4	3	2	1	2	3	3	3	3
<b>Q.No.</b>	<b>61</b>																			
Ans.	2																			

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 2 (ANSWERS)**

<b>Q.No.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>
Ans.	2	2	3	3	2	3	4	3	3	3	3	2	1	4	3	3	1	3	1	1
<b>Q.No.</b>	<b>21</b>	<b>22</b>	<b>23</b>	<b>24</b>	<b>25</b>	<b>26</b>	<b>27</b>	<b>28</b>	<b>29</b>	<b>30</b>	<b>31</b>	<b>32</b>	<b>33</b>	<b>34</b>	<b>35</b>	<b>36</b>	<b>37</b>	<b>38</b>	<b>39</b>	<b>40</b>
Ans.	2	1	3	4	3	2	1	1	3	3	4	4	2	3	4	2	1	4	1	3
<b>Q.No.</b>	<b>41</b>	<b>42</b>	<b>43</b>	<b>44</b>	<b>45</b>	<b>46</b>	<b>47</b>	<b>48</b>	<b>49</b>	<b>50</b>	<b>51</b>	<b>52</b>	<b>53</b>	<b>54</b>	<b>55</b>	<b>56</b>	<b>57</b>	<b>58</b>	<b>59</b>	<b>60</b>
Ans.	2	3	2	4	4	3	3	3	3	4	4	2	1	3	2	1	2	4	1	2
<b>Q.No.</b>	<b>61</b>	<b>62</b>	<b>63</b>	<b>64</b>	<b>65</b>	<b>66</b>	<b>67</b>	<b>68</b>	<b>69</b>	<b>70</b>	<b>71</b>	<b>72</b>	<b>73</b>	<b>74</b>	<b>75</b>	<b>76</b>	<b>77</b>	<b>78</b>	<b>79</b>	<b>80</b>
Ans.	2	1	4	3	3	3	3	3	3	3	2	3	4	1	2	3	2	3	3	3
<b>Q.No.</b>	<b>81</b>	<b>82</b>	<b>83</b>	<b>84</b>	<b>85</b>	<b>86</b>	<b>87</b>	<b>88</b>	<b>89</b>	<b>90</b>	<b>91</b>	<b>92</b>	<b>93</b>	<b>94</b>	<b>95</b>	<b>96</b>	<b>97</b>	<b>98</b>	<b>99</b>	
Ans.	1	4	2	4	3	4	4	3	1	4	4	3	3	2	1	3	2	2	2	

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 3 (ANSWERS)**

<b>Q.No.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>
Ans.	2	1	2	4	3	1	1	1	1	1	1	1	1	1	3	2	3	2	1	3
<b>Q.No.</b>	<b>21</b>	<b>22</b>	<b>23</b>	<b>24</b>	<b>25</b>	<b>26</b>	<b>27</b>	<b>28</b>	<b>29</b>	<b>30</b>	<b>31</b>	<b>32</b>	<b>33</b>							
Ans.	2	4	4	3	2	2	1	3	4	3	3	1	4							

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 4 (ANSWERS)**

<b>Q.No.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>
Ans.	2	4	1	3	2	1	1	4	2	2	1	3	1	3	3	2	2	4	4	2
<b>Q.No.</b>	<b>21</b>	<b>22</b>	<b>23</b>	<b>24</b>	<b>25</b>	<b>26</b>	<b>27</b>	<b>28</b>	<b>29</b>	<b>30</b>	<b>31</b>	<b>32</b>	<b>33</b>	<b>34</b>	<b>35</b>	<b>36</b>	<b>37</b>	<b>38</b>	<b>39</b>	<b>40</b>
Ans.	2	2	4	3	3	1	2	4	3	3	3	4	2	1	2	2	2	3	1	3
<b>Q.No.</b>	<b>41</b>	<b>42</b>	<b>43</b>	<b>44</b>	<b>45</b>	<b>46</b>	<b>47</b>	<b>48</b>	<b>49</b>	<b>50</b>	<b>51</b>	<b>52</b>	<b>53</b>	<b>54</b>	<b>55</b>	<b>56</b>	<b>57</b>	<b>58</b>	<b>59</b>	<b>60</b>
Ans.	1	1	2	4	2	4	1	2	3	1	4	3	3	2	1	4	4	1	2	2
<b>Q.No.</b>	<b>61</b>	<b>62</b>	<b>63</b>	<b>64</b>	<b>65</b>	<b>66</b>	<b>67</b>	<b>68</b>	<b>69</b>	<b>70</b>	<b>71</b>	<b>72</b>	<b>73</b>	<b>74</b>	<b>75</b>	<b>76</b>	<b>77</b>	<b>78</b>	<b>79</b>	<b>80</b>
Ans.	4	1	3	1	4	3	2	3	4	4	1	1	4	4	2	2	3	4	1	2
<b>Q.No.</b>	<b>81</b>	<b>82</b>	<b>83</b>	<b>84</b>	<b>85</b>	<b>86</b>	<b>87</b>	<b>88</b>	<b>89</b>	<b>90</b>	<b>91</b>	<b>92</b>	<b>93</b>	<b>94</b>	<b>95</b>	<b>96</b>	<b>97</b>	<b>98</b>	<b>99</b>	<b>100</b>
Ans.	3	3	3	2	2	4	3	4	4	2	2	3	2	4	1	1	2	1	2	3
<b>Q.No.</b>	<b>101</b>	<b>102</b>	<b>103</b>	<b>104</b>	<b>105</b>	<b>106</b>	<b>107</b>	<b>108</b>	<b>109</b>	<b>110</b>	<b>111</b>	<b>112</b>	<b>113</b>	<b>114</b>	<b>115</b>	<b>116</b>	<b>117</b>	<b>118</b>	<b>119</b>	<b>120</b>
Ans.	1	1	1	1	4	4	3	3	2	2	3	1	1	2	2	1	1	4	1	1
<b>Q.No.</b>	<b>121</b>	<b>122</b>	<b>123</b>	<b>124</b>																
Ans.	4	3	4	3																

**IMPORTANT PRACTICE QUESTION SERIES FOR IIT-JEE EXAM - 5 (ANSWERS)**

<b>Q.No.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>
Ans.	4	4	1	1	3	4	1	4	1	1	1	1	4	4	1
<b>Q.No.</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>	<b>21</b>									
Ans.	4	2	1	1	2	4									